



القسم... العام..... أسئلة الامتحان النهائي لمادة : دوائر كهربية 2  
لطلبة الفصل: ... الثاني... رمز المادة... EE102..... التاريخ 2022/ 04/ 10  
الفصل الدراسي خريف...-20222021..... اسم الأستاذ/المنسق : محمد الشاوش... ..الزمن...ساعتان.....  
اسم الطالب: ..... رقم القيد .....

المجموعات: 4+3+2+1


Q1)- complete the following {14 Marks}

- a)- The resistive circuit has .....power factor, because ..... {2 Marks}
- b)- The frequency is ..... {2 Marks}
- c)- Given that  $v(t) = 30\cos(377t - 60^\circ)$  and  $i(t) = 5\sin(377t + 60)$ , then the value of element or elements are .....because  $v$ ..... $i$ .....{3 Marks}
- d)- Two parallel impedances  $Z_1 = 4 + j6$  and  $Z_2 = 2 - j3$ , then  $Y_T = \dots\dots\dots(S)$ . {3 Marks}
- e)- Given  $i(t) = 50 \sin(2\pi 60 t + 20) A$   
Then the frequency is .....,the Period is .....,the average value is .....  
and the effective value is ..... {4 Marks}

Q2)- For the system shown {12Marks}

1- Draw the power triangle {8 Marks}

$$100 \angle 0^\circ V$$

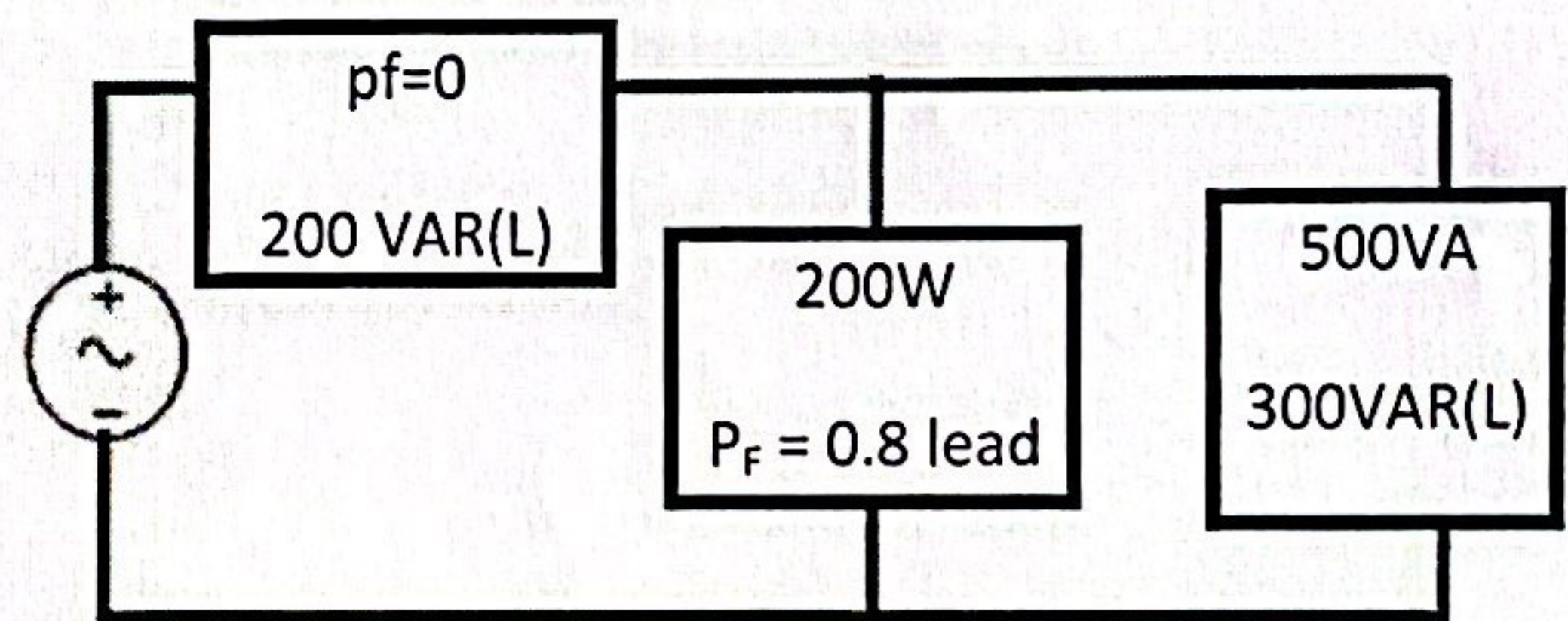


2- Determine the total current. {2 Marks}

3- Determine the total  $P_F$ . {2 Marks}

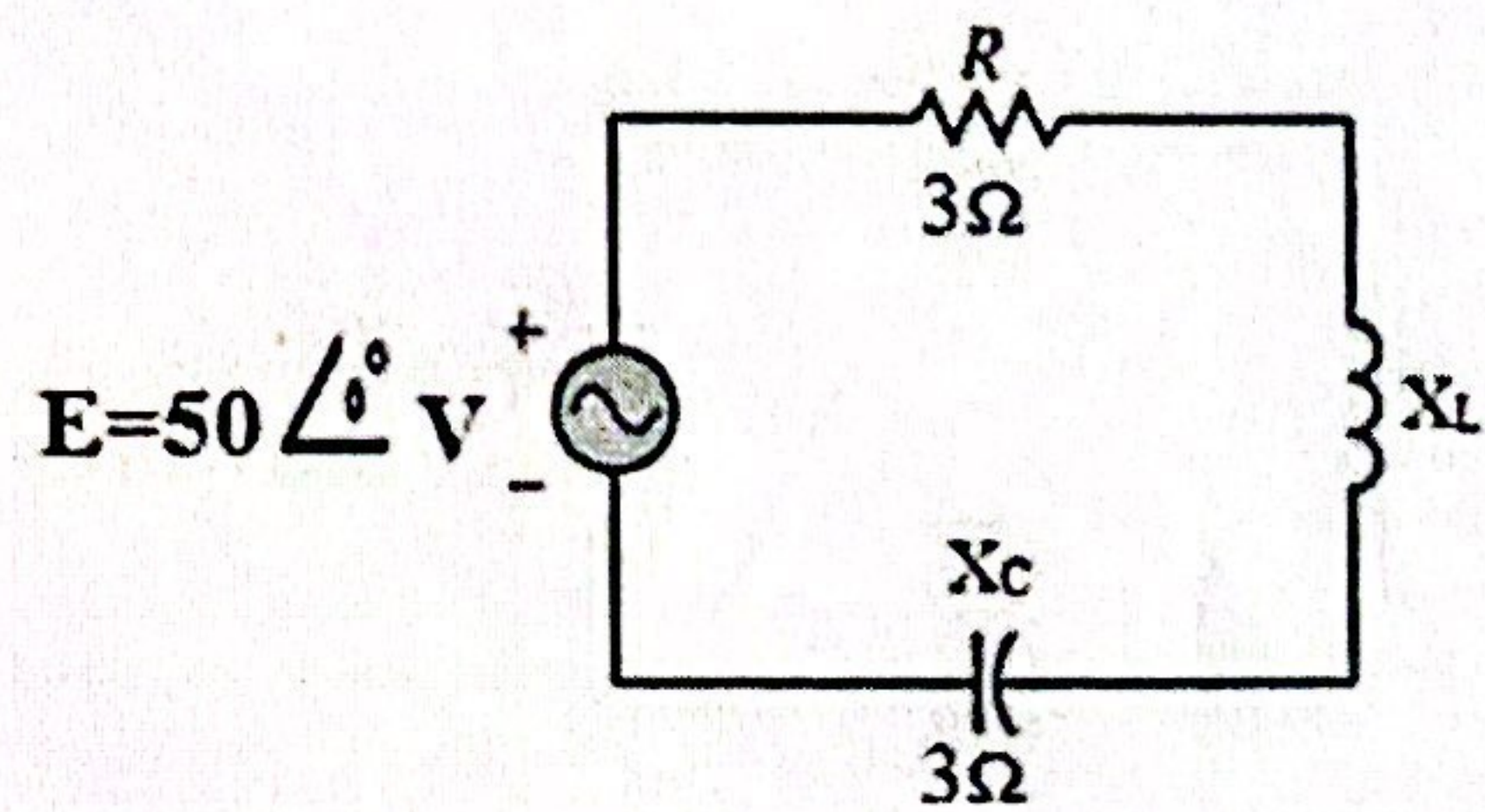Q3)- in the circuit shown, {12 Marks}

Given that:  $P_F = 0.6$  lagging,  
and the magnitude of  $Z_T = 5\Omega$ .

- a)- Determine the value of  $X_L$ . {4 Marks}
- b)- Draw the impedance diagram. {4 Marks}
- c)- Draw phasor diagram. {4 Marks}



Q4)- For the circuit {12 Marks}

shown in the figure.

$$Z_1 = 2 + j2, Z_2 = 2 \Omega,$$

$$Z_3 = -j2 \text{ and } Z_4 = 2 + j4$$

- a)- Determine the value of  $Z_L$  for maximum power to the Load. {5 Marks}
- b)- Find  $P_{max}$ . {7 Marks}

