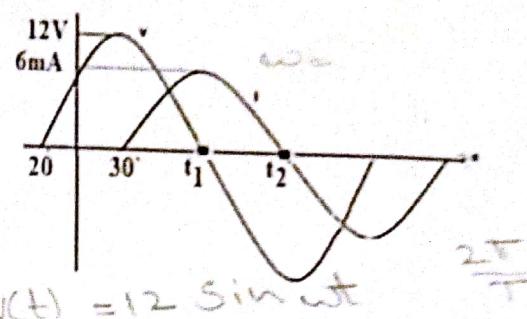


Q1)-

The waveforms of a series AC circuit are shown in the figure.

- Write the mathematical expressions for $v(t)$ and $i(t)$ if the frequency is 60HZ.
- What is the power factor of this circuit?
- Determine the type and value of the elements..



Q2)-

a)-The sinusoidal waveform is $v(t)=60 \sin (377t +20^\circ)$ V , sketch the waveform , and determine

- Average power.
- Effective value.
- The magnitude of the waveform at $t= 6ms$


Q3)-

For the circuit shown in the figure.

$$Z_1=4-J6, Z_2=-J6,$$

$$Z_3=J4 \text{ and } Z_4=2 \Omega$$

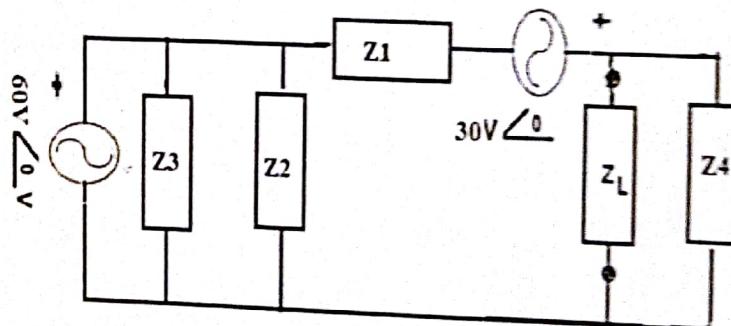
Determine the value of Z_L for maximum power to the Load, and find P_{max} .



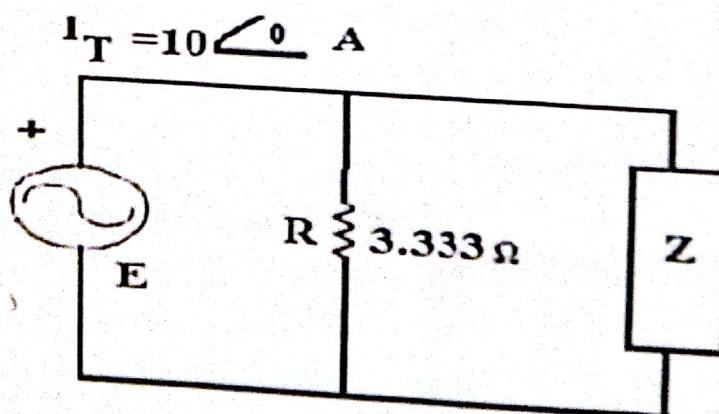Q4)-

For the circuit shown in the figure, the total current leads the source voltage E by 53.13°

- Determine the value of the unknown element.
- find E



Q1

Q1 At first we have to determine ω

$$\omega = 2\pi f$$

$$\omega = 2 \times 3.14 \times 60$$

$$\omega = 376.8 \text{ rad/s}$$

$$v(t) = 12 \sin(376.8t + 2^\circ) \quad \checkmark$$

$$i(t) = 6m \sin(376.8t - 3^\circ) \quad \checkmark$$

b] $P_f = \cos(\theta_v - \theta_i)$

$$= \cos 120 + 30^\circ$$

$$= \cos 50^\circ$$

$$P_f = 0.642 \text{ lagging} \quad \checkmark$$

c] $E_{\text{eff}} = \frac{V_m}{\sqrt{2}} = \frac{12}{\sqrt{2}} = 8.485 \angle 120^\circ \text{ V}$

$$I = \frac{I_m}{\sqrt{2}} = \frac{6 \times 10^{-3}}{\sqrt{2}} = 4.242 \angle -30^\circ \text{ mA}$$

$$Z_t = \frac{E}{I} = \frac{8.485 \angle 120^\circ}{4.242 \text{ mA} \angle -30^\circ} = 2k \angle 50^\circ \Omega$$

$$2 \angle 50^\circ = 1.285 \text{ k}\Omega + j1.532 \text{ k}\Omega \quad \checkmark$$

\therefore the elements are $1.285 \text{ k}\Omega$ resistor
and $1.532 \text{ k}\Omega$ inductor


$$L = ?$$

Q2

Q3

(1A)

Q3

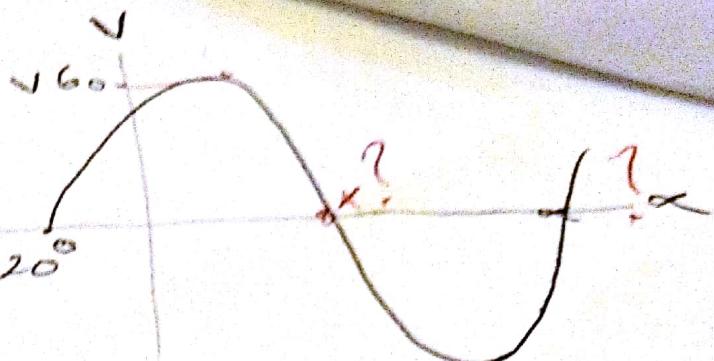

1] the average value

= zero because ✓

the sin wave is identical
wave.

$$V_{\text{eff}} = \frac{V_m}{\sqrt{2}} = \frac{60}{\sqrt{2}} = 42.426 \text{ V}$$

$$3] v(t) = 60 \sin(377t + 20^\circ) \text{ V}$$

$$v(6 \text{ ms}) = 60 \sin(377 \times 6 \times 10^{-3} + 20^\circ) \text{ V}$$


$$= 60 \sin(2.262 \times \frac{180^\circ}{\pi} + 20^\circ) \text{ V}$$

$$= 60 \sin(129.66^\circ + 20^\circ) \text{ V}$$

$$= 60 \sin(149.66^\circ) \text{ V}$$

$$\therefore v(6 \text{ ms}) = 30.3 \text{ V}$$

Q5

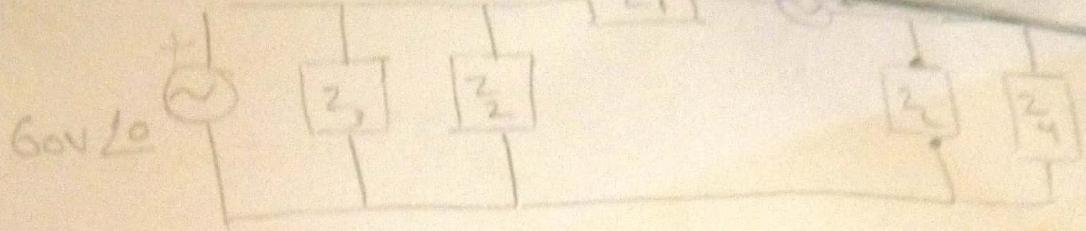

$$Z_1 = 4 - j6 = 7.211 \angle -56.309^\circ$$


$$Z_2 = -j6 = 6 \angle -90^\circ$$

$$Z_3 = j4 = 4 \angle 90^\circ$$

$$Z_4 = 2 = 2 \angle 0^\circ$$

by using thevenin's theory

$$Z_{th} = Z_1 \parallel Z_4$$

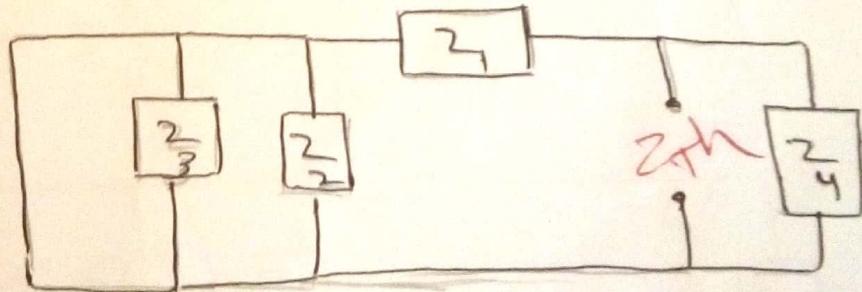

$$Z_{th} = \frac{7.211 \angle -56.309^\circ \times 2}{6 - j6} = \frac{14.422 \angle -56.309^\circ}{8.485 \angle -45^\circ}$$

$$Z_{th} = 1.699 \angle -11.309^\circ \Omega = 1.666 - j0.333 \Omega$$


~~$$Z_1 = Z_{th}^* = 1.699 \angle 11.309^\circ \Omega = 1.666 + j0.333 \Omega$$~~

E_{th}

30 L^o V Source active E'_{th}

$$E''_{th} = E_{24}$$


by using VDR

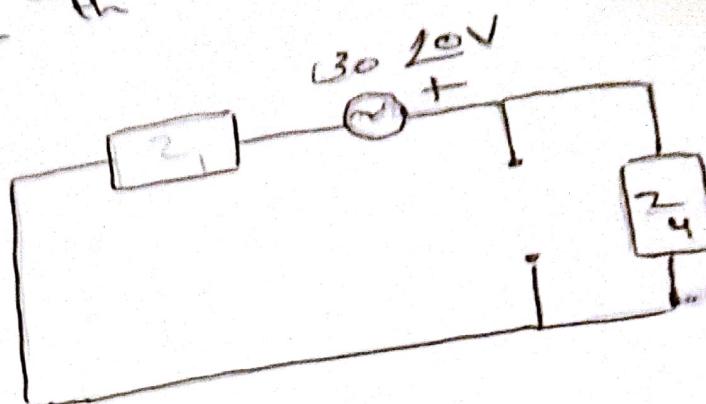

$$E''_{th}^+ = \frac{30 L^o \times 2}{8.485 L^{-45}} = 7.071 \angle 145^\circ V = 5 + j 5 V$$

60 L^o Source active E''_{th}^+

$$E''_{th}^- = E_{24}$$

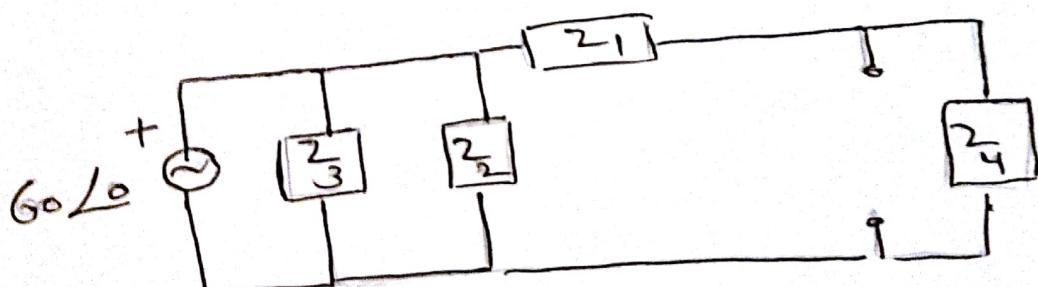

$$E(Z_1 + Z_4) = E_{source}$$

$$E''_{th}^+ = \frac{60 L^o \times 2}{8.485 L^{-45}} = \frac{60 L^o \times 2}{8.485 L^{-45}}$$

$$E''_{th}^- = 14.142 \angle 145^\circ V = 10 + j 10 V$$

$$E_{th} = E_m + E_m'$$

$$= 15 + 15 = 21.213 \text{ J/s}$$

$$P_{max} = \frac{E_{th}^2}{4R_{th}} = \frac{(21.213)^2}{4 \times 1.699} = 66.214 \text{ watt}$$

Qu

$$I = 10 \angle 0^\circ A$$

$$E = E \angle 53.13^\circ$$

$$P_f = \frac{G}{Y_t}$$

because 2 contains a single element
and the circuit has capacitive
effect

$$\cos 53.13 = \frac{0.3}{Y_t}$$

$$Y_t = \frac{0.3}{0.6} = 0.5$$

$$Y_t = 0.5 \angle 53.13$$

$$Y_t = 0.3 + j0.399$$

$$Y_t = 0.3 + j0.4$$

$$Y_t = \frac{3\Omega}{R} + \frac{2.5\Omega}{jX_C}$$

$$E = \frac{I}{Y_t} = \frac{10}{0.5} = 20 V$$

the unknown element is a capacitor with a value of
 2.5Ω