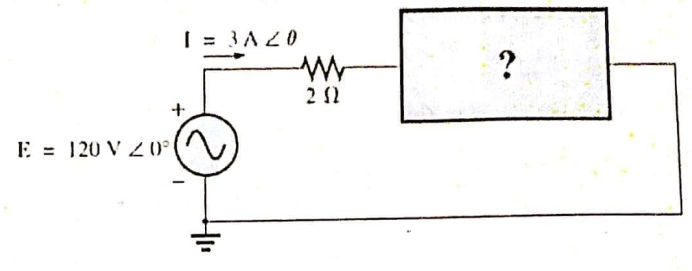


Answer all the questions

Q1A- 6 درجات

Find the series element or elements in the circuit shown that must be in the enclosed container to satisfy the following conditions.


- a- Average power of the circuit is = 300 W
- b- The circuit has a lagging power factor



Q1B- 9 درجات


For the network circuit shown Find

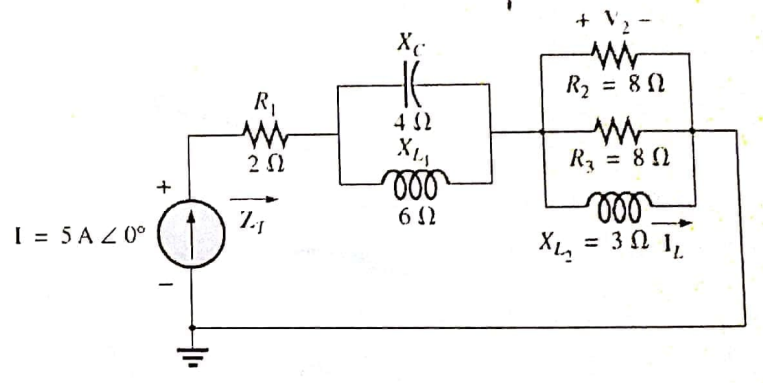- a) The current I_L .
- b) Voltage V_2 .
- c) The average power delivered to the network.



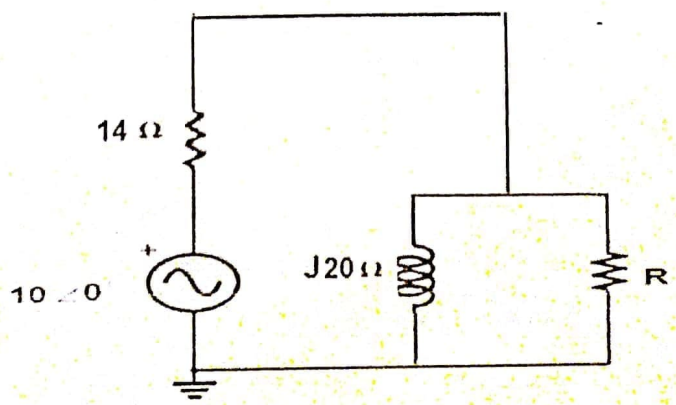Q2- 15 درجة


For the circuit shown , find the value of R to produce maximum power in the 14 Ω resistor, Calculate the value of this maximum power P_{max}





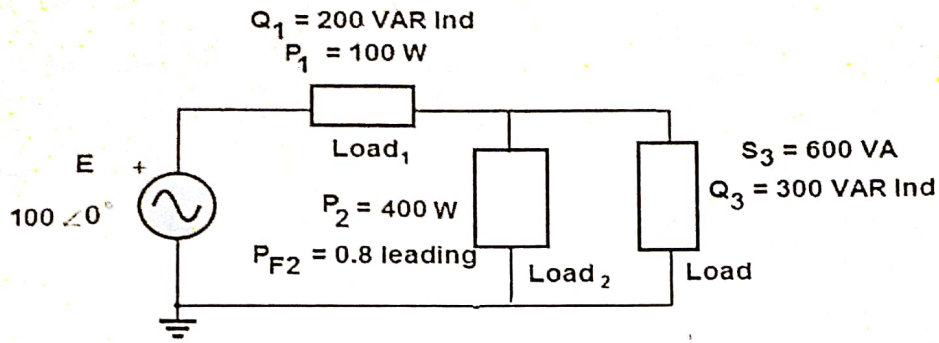Q3- 15 درجة

The Circuit shown consists of three loads in a series - parallel connection , with each of the load is deified as indicted. Find the overall complex power of the circuit , its overall Pf, and the phasor from of the source current I




Q4A 8 درجات

If A series resonant circuit will resonate at a frequency of 1 MHz with a fractional bandwidth of 0.2 Hz the quality factor of the coil at resonance is 12.5 and its inductance is 100 mH, determine the following:


- The resistance of the coil.
- The required value of capacitance

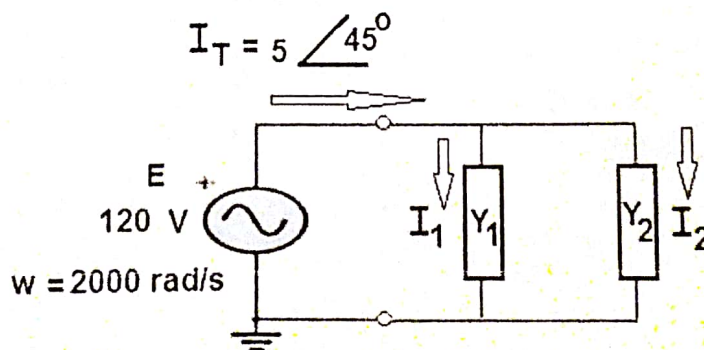Q4B- 7 درجات

Y1 and Y2 Contain a single element each. The current I1 is in phase with E and equal to 6A. The source voltage E leads It. Find the value of each element



Q11

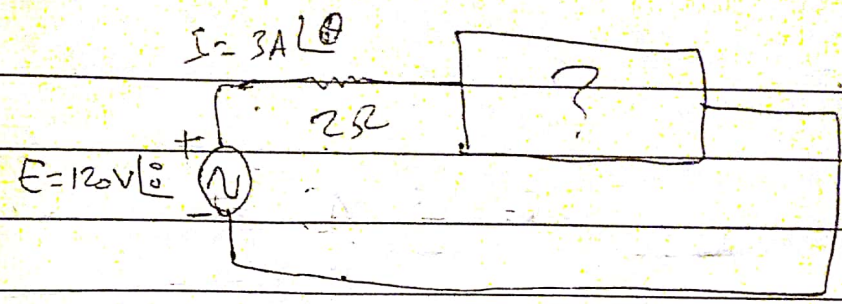

$$P = IV \cos \theta$$

$$300 = (3)(120) \cos \theta$$

$$\cos \theta = \frac{300}{(3)(120)} = 0.833$$

$$\theta = \cos^{-1} 0.833 = 33.59^\circ$$

$$\theta = 33.59^\circ$$

$$V = 120V \angle 0^\circ$$

$$I = 3A \angle -33.59^\circ$$


$$Z_T = \frac{V}{I} = \frac{120 \angle 0^\circ}{3 \angle -33.59^\circ} = 40 \Omega \angle 33.59^\circ$$

$$Z_T = 40 \Omega \angle 33.59^\circ = 33.34 + j22.10 \Omega$$


$$R_T = 33.34 \Omega = 2R + R$$

$$R = 33.34 - 2 = 31.34 \Omega$$

$$R = 31.34 \Omega$$

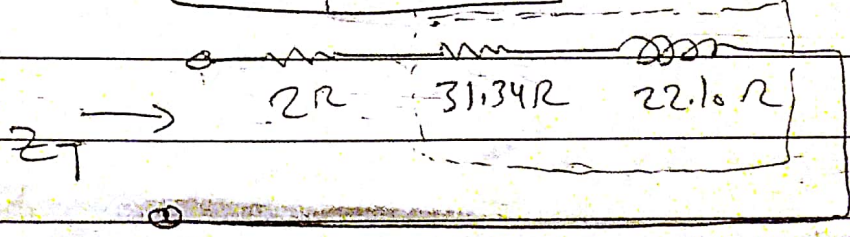

Q1B

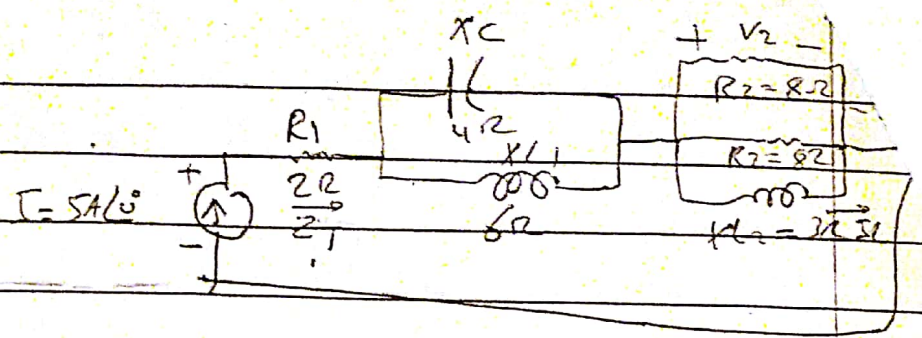

$$Z_T = 2\Omega + \frac{(4\angle -90^\circ)(6\angle 90^\circ)}{-j4 + j6} + \frac{(4\angle 0^\circ)(8\angle 0^\circ)}{4 + j3}$$

$$= 2 + 24\angle 0^\circ \frac{2\angle 90^\circ}{5\angle 36.87^\circ}$$

$$= 2 + 12\angle -90^\circ + 2.4\angle 53.13^\circ$$

$$Z_T = 3.44\Omega - j10.08\Omega$$

$$Z_T = 10.65\Omega \angle -71.16^\circ$$

$$V_2 = 2.4\angle 53.13^\circ \text{ V} = 2.4\angle 53.13^\circ \times 5\angle 0^\circ$$

$$V_2 = 12\angle 53.13^\circ \text{ V}$$

$$I_L = \frac{(4\angle 0^\circ) \text{ V}}{4 + j3} = \frac{(4\angle 0^\circ)(5\angle 0^\circ)}{5\angle 36.87^\circ} = 4\text{ A} \angle -36.87^\circ$$

$$I_L = 4\angle -36.87^\circ$$

$$FP = \frac{R}{Z_T} = \frac{3.44}{10.65} = 0.323 \text{ (Leading)}$$

$$P = EI \cos \theta$$

$$P = 53.25 \times 5 \times \cos(-71.16) = 53.25 \times 5 \times 0.323$$

$$P = 85.97 \text{ W}$$

$$\therefore S = 1039 = EI$$

2
A3

$$\therefore I = \frac{1039}{100} = 10.39 \text{ A}$$

Since it's inductive load \Rightarrow that
E lead I

$$\therefore I = 10.39 \angle -11.1^\circ \text{ A}$$

A3

A4B

Since I_1 in Y_1 is in phase with E $\Rightarrow Y_1$ is R
 \therefore E lead $I_T \Rightarrow$ ckt is inductive $\therefore Y_2$ must
be inductor then I_2 must lag E by
 90°

$$I_T^2 = I_1^2 + I_2^2$$

$$I_2 = \sqrt{5^2 - 3^2} = 4 \text{ A}$$

$$R = \frac{E}{I_1} = \frac{120}{3} = 40 \Omega$$

$$X_L = \frac{E}{I_2} = \frac{120}{4} = 30 \Omega = \omega L$$

$$\therefore L = \frac{30}{3000} = 10 \text{ mH}$$

$$E = 120 \angle 45^\circ + 53.1^\circ = 120 \angle 98.1^\circ \text{ V}$$

A2
 To find this max power

$$P_{142} = P_{max} = I^2 (14)$$

$$\text{but } I = \frac{E}{Z_T} = \frac{10 \angle 0^\circ}{Z_T}$$


$$\text{and } Z_T = 14 + \frac{19.6(\angle 20^\circ)}{19.6 + j20} = \frac{392 \angle 90^\circ}{2.8 \angle 45.58^\circ}$$

$$Z_T = 14 \angle 44.42^\circ$$

$$I = \frac{10 \angle 0^\circ}{14 \angle 44.42^\circ} = 0.714 \angle -44.42^\circ$$

$$P_{max} = (0.714)^2 (14) = 9.99 \approx 10 \text{ Watt}$$

4B
 Phasor diagram for Q4B

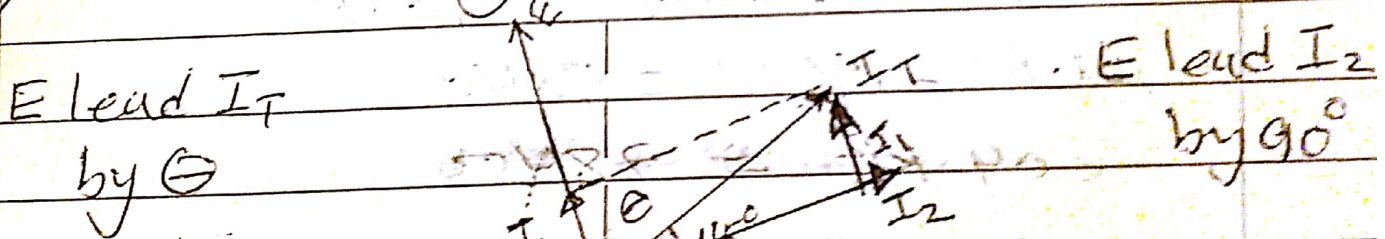

from figure

$$I_1 = I_T \cos \theta$$

$$\cos \theta = \frac{I_1}{I_T} = \frac{3}{5} = 0.6 \quad I_1^2 + I_2^2 = I_T^2$$

$$\theta = 53.1^\circ$$

د. محمد رفیق

D3

$$S = S_1 + S_2 + S_3$$

$$S_1 = 100 + j200 = 223.6 \angle 63.4^\circ \text{ VA}$$

For load 2

$$P_{F2} = 0.8 \text{ leading (capacitive load)}$$
$$= \frac{P_2}{S_2} = \cos \theta_2$$

$$\therefore |S_2| = \frac{P_2}{P_{F2}} = \frac{400}{0.8} = 500 \text{ VA}$$

$$\theta_2 = -36.9^\circ$$

Thus

$$S_2 = 500 \angle -36.9^\circ \text{ VA} = 400 - j300 \text{ VA}$$

For load 3

$$Q_3 = S_3 \sin \theta_3$$

$$\sin \theta_3 = \frac{Q_3}{S_3} = \frac{300}{600} = 0.5$$

$\therefore \theta_3 = 30^\circ \Rightarrow$ inductive load

$$S_3 = 600 \angle 30^\circ = 519.6 + j300 \text{ VA}$$


$$S = (100 + j200) + (400 - j300) + (519.6 + j300)$$
$$= 1019.6 + j200 = 1039.1 \angle 11.1^\circ \text{ VA}$$

The overall load is inductive with

$$P_F = \cos 11.1^\circ = 0.981 \text{ lagging}$$

Q2


To Transfer Max. power to 14Ω

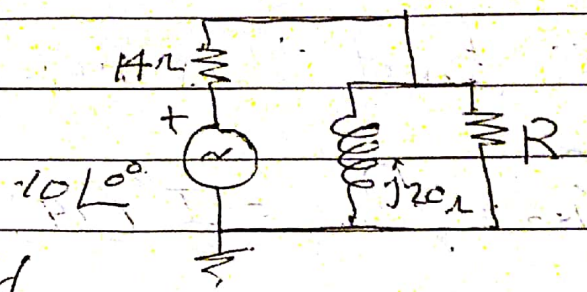

We need to find

Thevenin circuit out of 14Ω as follow
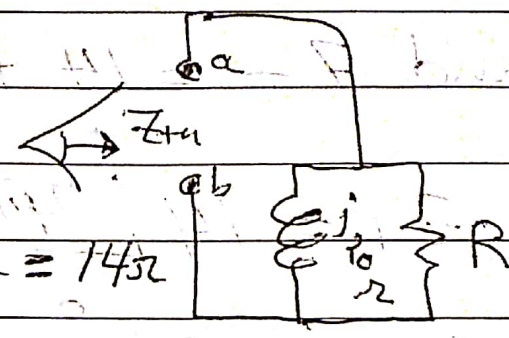
$$Z_{th} = \frac{j20 \times R}{R + j20}$$



$$\left| \frac{j20R}{R + j20} \right| = \frac{20R}{\sqrt{R^2 + 400}} = 14\Omega$$

Z_{th} must equal to 14Ω to insure a max power transfer. Square both sides

$$\frac{400R^2}{R^2 + 400} = 196$$

$$196(R^2 + 400) = 400R^2$$

$$196R^2 + 78400 = 400R^2$$

$$400R^2 - 196R^2 = 78400$$

$$204R^2 = 78400$$

$$R^2 = \frac{78400}{204} = 384.31\Omega$$

$$R = \sqrt{384.31} \Rightarrow 19.6\Omega$$

$$Q_L = \frac{X_L}{R_L} \Rightarrow R_L = \frac{X_L}{Q_L} = \frac{2\pi fL}{Q_L}$$

$$R_L = \frac{2\pi (1 \times 10^6) \times 100 \times 10^{-3}}{12.5} = 50.27 \text{ k}\Omega$$

$$\frac{P_o - P_i}{P_i} = \frac{L}{Q_S} = 0.2$$

$$Q_S = \frac{1}{0.2} = 5 = \frac{X_L}{R} = \frac{2\pi fL}{R} = \frac{2\pi \times 1 \times 10^6 \times 100 \times 10^{-3}}{R}$$

$$R = \frac{628.32 \times 10^3}{5} = 125.66 \text{ k}\Omega$$

$$R = R_d + R_L$$

$$125.66 \text{ k}\Omega = R_d + 50.27 \text{ k}\Omega$$

$$R_d = 125.66 \text{ k}\Omega - 50.27 \text{ k}\Omega$$

$$R_d = 75.39 \text{ k}\Omega$$

$$X_C = \frac{1}{2\pi fC} = X_L$$

$$C = \frac{1}{2\pi fX_C} = \frac{1}{2\pi \times 1 \times 10^6 \times 628.32 \times 10^3}$$

$$C = 253.3 \text{ nF}$$



Q1)- {15 Marks}

a)- Given $\omega = 314 \text{ rad/s}$, determine how long it will take the sinusoidal waveform to pass through an angle of 90°

$$\frac{90 \times \frac{\pi}{180}}{2\pi} \alpha = \omega t \quad \frac{\pi}{2} = \frac{314 \times \pi}{180} t$$

{7Marks}

b)- The current through a 0.2-H coil is provided. Find the sinusoidal expression for the voltage across the coil.



Sketch the v and i curves
 $i(t) = 7 \sin(377t - 70^\circ)$

{8Marks}

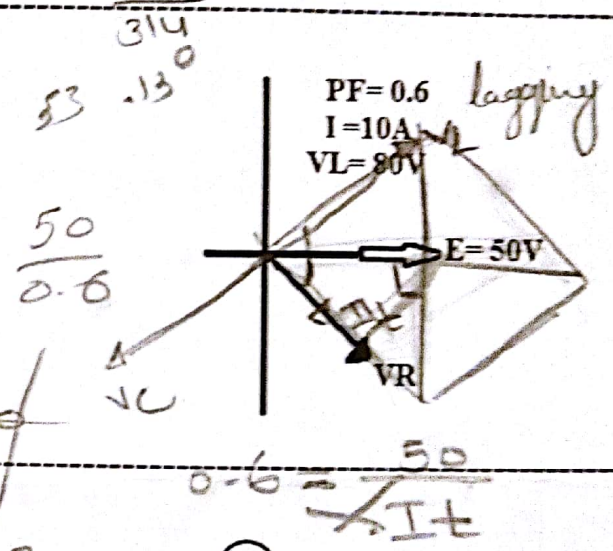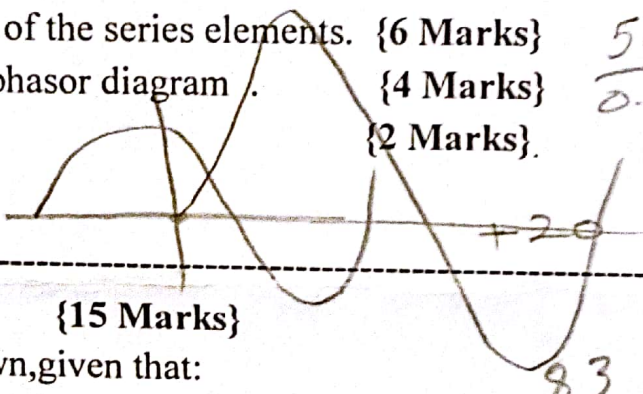Q2)- {15 Marks}

The phasor diagram of Series RLC circuit is shown in the fig:

- 1- Find The value of the series elements. {6 Marks}
- 2- Complete the phasor diagram. {4 Marks}
- 3- Determine P_{av} {2 Marks}.




Q3)- {15 Marks}

In the circuit shown, given that:

$Z_1 = 3 - j4$, $Z_2 = 4.426 + j4.426$, and $Z_3 = 2 - j3$

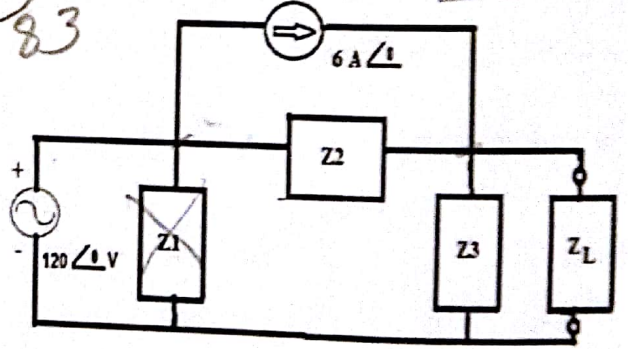
- a)- Determine the value of Z_L for maximum power to the load. {6 Marks}
- b)- Find P_{max} {9 Marks}



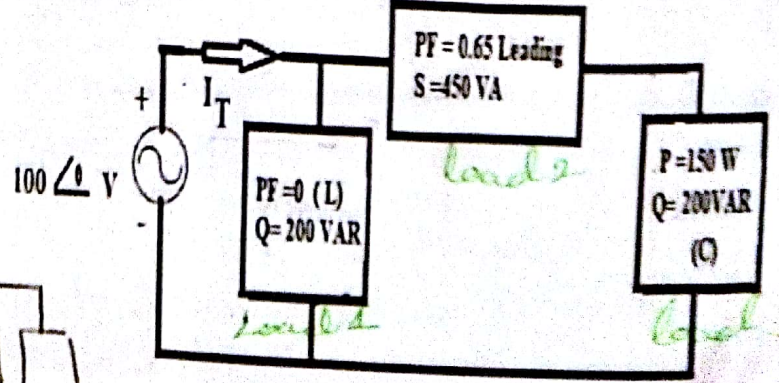Q4)- {15 Marks}

For the System shown:

- a)- Draw the power triangle. {9 Marks}
- b)- Find total power factor. {3 Marks}
- c)- Determine the total current I_T . {3 Marks}



تمنيتي للجميع بالتوفيق
أسئلة المادة