




اسئلة الامتحان النصفى الأول لمادة دوافر كهربائية 2

Answer all the following Questions

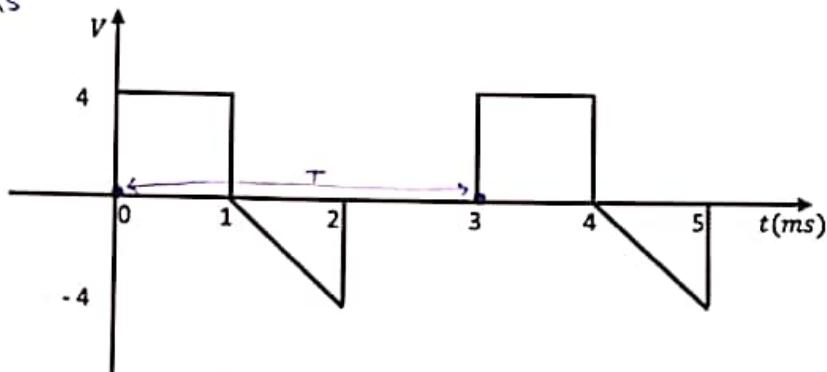
Q1- For the given periodic waveform, find:

- ✓ (i) The period (T)? 3 ms
- ✓ (ii) The frequency (f)?
- ✓ (iii) The average value?
- ✓ (iv) The RMS value?



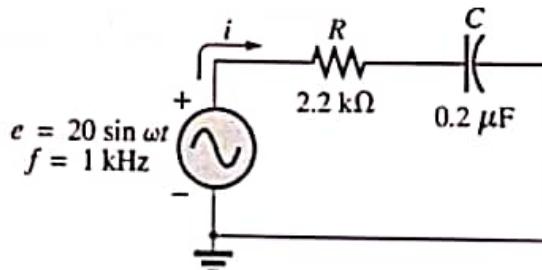Q2 For the given network:

- ✓ (i) Determine Z_T .
- ✓ (ii) Calculate V_C .
- ✓ (iii) Draw the phasor diagram.



Q3 Find the element or elements that must be in Z to satisfy power factor $P_f = 0.83$ (leading).

