



atzman... ساعة ونصف

أستاذ المادة / د. محمد ناجي الرقيعي

المجموعة:

رقم القيد:

اسم الطالب:

- ✓ Q1- (A) If the current through a capacitor $C = 50 \mu F$ is given by $i(t) = 5 \cos(2000t)$ A the voltage then is equal to..... [1.0 marks]

$P_f = \frac{Z}{Z+R}$ (B) If $\cos \theta = Z/R$ then the circuit is totally R and P_f is 1 and the phase angle between V and I is 90° in phase. and average power is.... $P = I^2 R$ and θ_Z is 0 [2.0 marks]

As P_f reaches zero level, the load reaches..... $Z = \infty$ [1.0 marks]

(C) If V leads I by 90 degree in series single element cct, the Impedance Z is equal to $Z = jX_L$ [1.0 marks]


(D) If the Load power factor is 1 , this means cct is R $\cos \theta_Z = 1$ $\theta_Z = 0$ [2.0 marks]

(E) $X_L = 0$ at frequency $f = 0$ & when $X_C > X_L$ in series cct means it leads V [1.0 marks]

(F) At what angle is $P_f = V/I$, The angle between I_L and I_C in parallel cct is 180° [1.0 marks]

(g) Phasor diagram shown is representing parallel circuit and the value of θ_L is $180^\circ - 45^\circ = 135^\circ$ [1.0 marks]

$$I^2 R = V^2 L$$

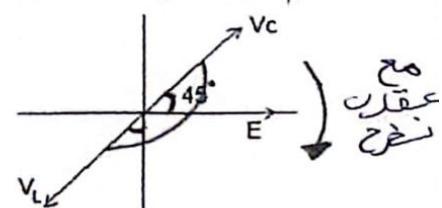


Q2.

$e_1(t) = 8 \sin(1000t + 15)$ v and $e_2(t)$ has RMS value of 5.66 v and leads $e_1(t)$ by 60 degree, if the current in the circuit is given by $i(t) = 2 \cos(1000t - 135)$ find

A) Nature and value of the single element load Z [6.0 marks]

b) Power dissipated in the circuit and P_f [2.0 marks]

c) Draw phasors diagrams [2.0 marks]

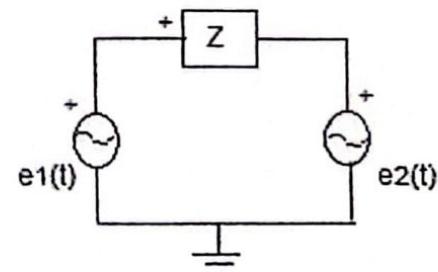

Q3.


In the cct shown $E = 1000$ v and the current i_1 lead E where E is reference signal [5]

$$i_1(t) = 158.1 \cos(1000t + 26.2)$$
 A [2.0 marks]

$$i_3(t) = 100 \sin(1000t + 135)$$
 A find

A) The phase between E and i_2 [4.0 marks]

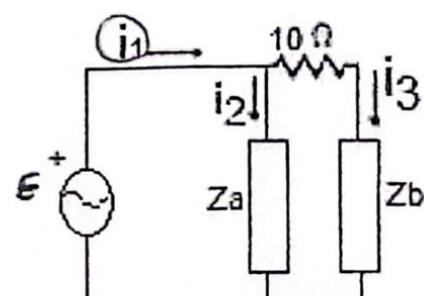b) The nature and values of Z_a and Z_b [6.0 marks]



Z_a Z_b are single elements

معروض
 $Z_C > X_L$
 $\theta_Z = -90^\circ$