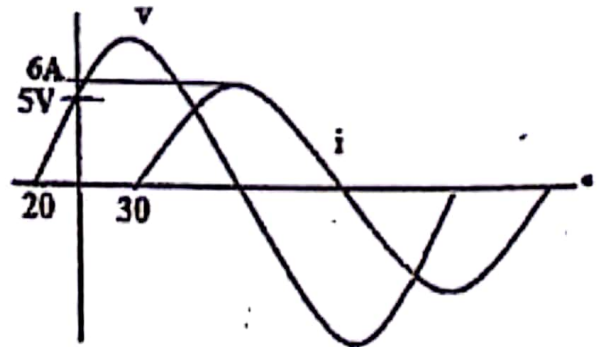


Q1)- {8 Marks}

The waveform of a parallel AC circuit are shown in the figure.

- Write the mathematical expressions for $v(t)$ and $i(t)$.
- Determine the average power (P_{av}) and Pf.
- Determine the type and value of the element or elements.




Q2)- {8 Marks}

For the circuit shown in the figure.

$$Z_1 = 2 + j2, Z_2 = -j2, Z_3 = 3 - j4$$

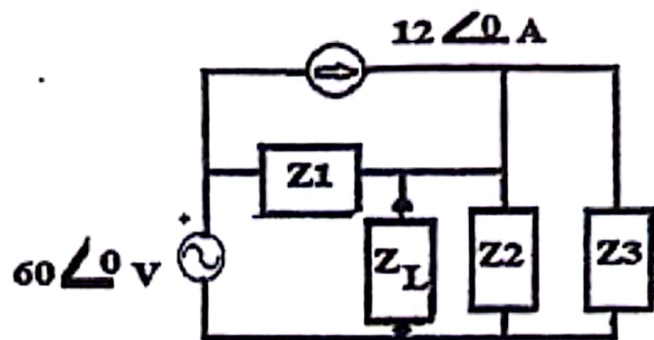Determine the value of Z_L for maximum power to the Load, and find P_{max}




Q3)- Complete {6 Marks}

If $i(t) = 10 \sin(2\pi 60t)$, then the frequency isHz, the average value is, the effective value is and the magnitude of the waveform at $t = 10 \text{ ms}$ is

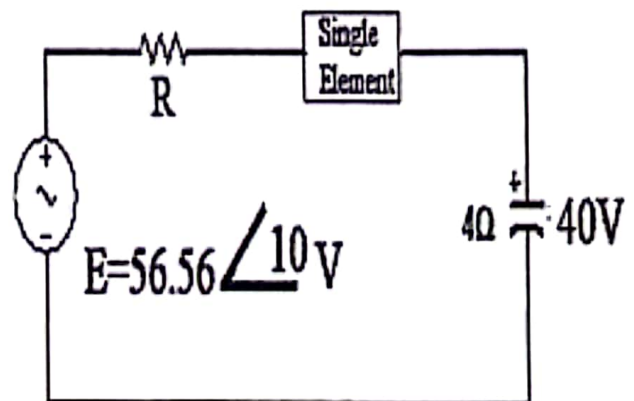Q4)- {8 Marks}

AC Series circuit shown in the fig, and the circuit has 0.707 Lagging Pf

- Determine R and the unknown single element.
- Draw phasor diagram.
- Draw impedance diagram.
- Find P_{av} .



Q1) - 18

$$i(t) = 6 \sin(\omega t - 3^\circ) \text{ A} \quad (01)$$

$$v(t) = V_m \sin(\omega t + 2^\circ) \Rightarrow 5 = V_m \sin 2^\circ$$

$$v(t) = 14.619 \sin(\omega t + 2^\circ) \text{ V} \quad (02) \quad V_m = \frac{5}{\sin 2^\circ} = 14.619 \text{ V}$$

$$(L) \quad P_{av} = \frac{V_m I_m}{2} \cos \theta$$

$$P_{av} = \frac{14.619 \times 6}{2} \cos 5^\circ = 28.191 \text{ W} \quad (01)$$

$$P_f = \cos 5^\circ = 0.642 \text{ Laggy}$$


(C) Parallel AC circuit

$$Y_T = \frac{I_T}{E} = \frac{6/\sqrt{2} \angle -3^\circ}{14.619/\sqrt{2} \angle 2^\circ} = 0.410 \angle -5^\circ \text{ (S)}$$

$$Y_T = \underbrace{0.2635}_G - j \underbrace{0.3141}_{BL}$$

$$R = \frac{1}{G} = \frac{1}{0.2635} = 3.7951 \, \Omega \quad (02)$$
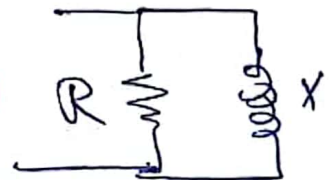
$$X_L = \frac{1}{BL} = \frac{1}{0.3141} = 3.1837 \, \Omega \quad (02)$$




Q2) / 8

$$Z_1 = 2 + j2 = 2.828 \angle 45^\circ \Omega$$

$$Z_2 = -j2 = 2 \angle -90^\circ \Omega$$
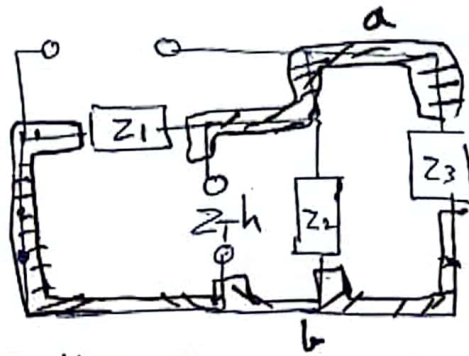
$$Z_3 = 3 - j4 = 5 \angle -53.13^\circ \Omega$$





$$Z_{Th} = Z_1 \parallel Z_2 \parallel Z_3 = 1.8115 \angle -48^\circ$$

$$= 1.2121 - j1.346 \quad \text{(01)}$$

$R_{Th} \qquad X_{Th}$

For max Power to the Load
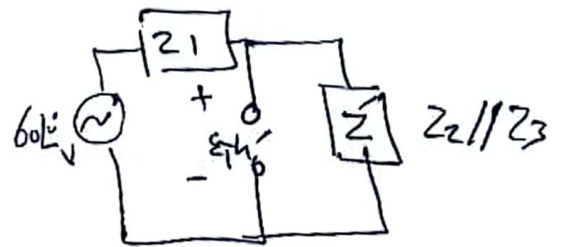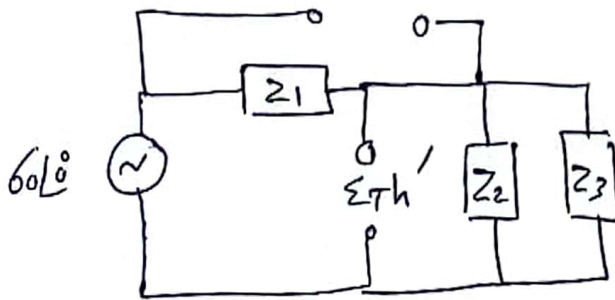
$$Z_L = 1.2121 + j1.346 \quad \Omega \quad \text{(02)}$$



$$E_{Th}' = V Z' \quad \text{using VDR}$$


$$E_{Th}' = \frac{60 \angle 0^\circ \times Z'}{Z' + Z_1} = \frac{60 \angle 0^\circ \times 1.491 \angle -79.57^\circ}{0.27 - j1.466 + 2 + j2} \quad \text{(01)}$$

$$E_{Th}' = \frac{89.46 \angle -79.57^\circ}{2.27 + j0.534} = \frac{89.46 \angle -79.57^\circ}{2.332 \angle 13.23^\circ} = 38.362 \angle -92.73^\circ \text{ V}$$

$$E_{Th}'' = V(Z' \parallel Z_1)$$

$$= 12 \angle 0^\circ \times 1.8115 \angle -48^\circ \quad \text{(01)}$$

$$= 21.738 \angle -48^\circ \text{ V}$$

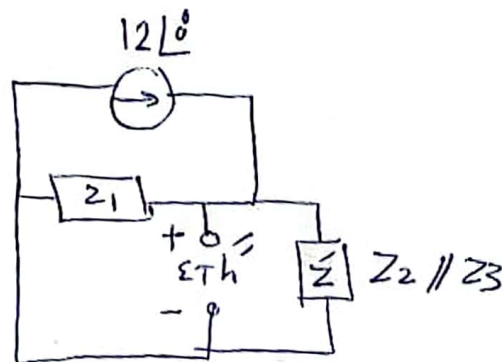

$$E_{Th} = E_{Th}' + E_{Th}''$$

$$= 38.362 \angle -92.73^\circ + 21.738 \angle -48^\circ$$

$$= 55.787 \angle -76.822^\circ \text{ V} \quad \text{(01)}$$

$$P_{max} = \frac{E_{Th}^2}{4R_{Th}} = 642 \text{ W} \quad \text{(02)}$$

15) - /6

if $i(t) = 10 \sin(2\pi 60t)$, then the frequency is 60 Hz , (01)

the average value = 2.88 A , (01) the effective value is 7.07 A (01)

and the magnitude of the waveform at $t = 10 \text{ ms}$ is 5.877 A (03)

Q4) - /8

(a)

$P_f = 0.707$ Lagging $\Theta = \cos^{-1} 0.707 = 45^\circ$

$I = \frac{V_c}{X_c} = \frac{40}{4} = 10 \text{ A}$

$I = 10 \angle -35^\circ \text{ A}$

$Z_T = \frac{E}{I} = \frac{56.56 \angle 10^\circ}{10 \angle -35^\circ}$

$Z_T = 5.656 \angle 45^\circ$

$= 4 + j4$
 R X_T

$Z_T = R + \text{single element} - j4$

$4 + j4 = R + \text{single} - j4$


$R + \text{single element} = 4 + j8$

$R = 4 \Omega$ single element = $j8$


d) - $P_{av} = E \cdot I \cos \Theta$

$= I^2 R$

$= (10)^2 \times 4 = 400 \text{ W}$ (01)

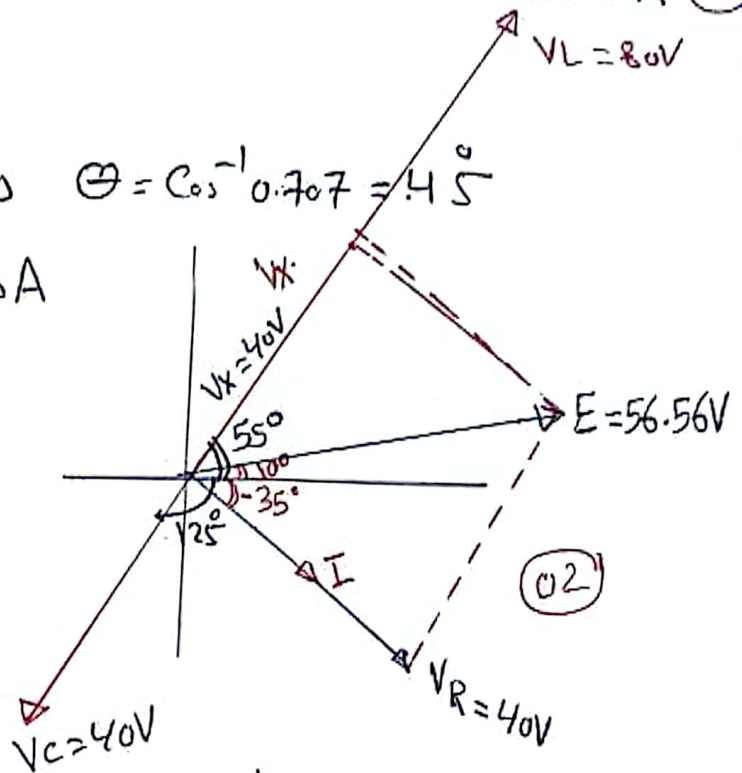

(b) Phasor Diagram

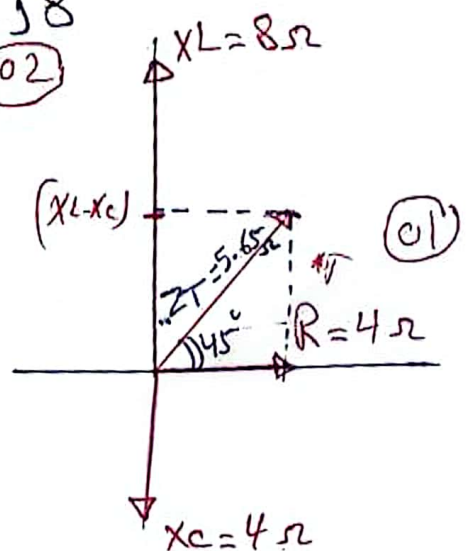

(c) Impedance Diagram