



القسم... العام..... أسئلة الامتحان النهائي لمادة : دوائر كهربية 2  
لطلبة الفصل:..... الثاني..... رمز المادة..... التاريخ 2019/ 09/ 18

لفصل الدراسي ربيع..... 2019..... اسم الأستاذ/المنسق :..... محمد الشاوش..... الزمن..... ساعتان.....  
اسم الطالب:..... رقم القيد..... المجموعات: الجميع

**Q1)- {15 Marks}**

a)- Given  $\omega = 314$  rad/s, determine how long it will take the sinusoidal waveform to pass through an angle of  $90^\circ$




b)-The current through a 0.2-H coil is provided. Find the sinusoidal expression for the voltage across the coil. Sketch the v and i curves

$i(t) = 7 \sin(377t - 70^\circ)$

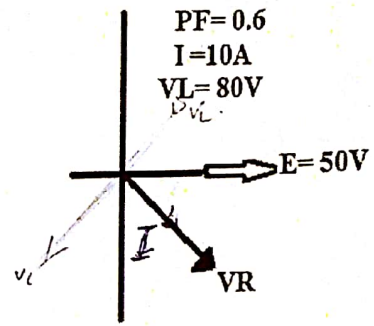**Q2)- {15 Marks}**

The phasor diagram of Series RLC circuit is shown in the fig:

- 1- Find The value of the series elements. {6 Marks}
- 2- Complete the phasor diagram . {4 Marks}
- 3- Determine  $P_{av}$  {2 Marks}




12

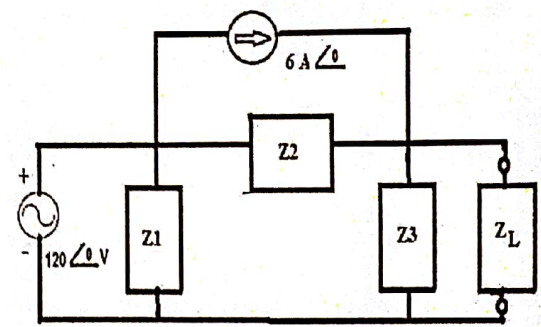**Q3)- {15 Marks}**

In the circuit shown, given that:  
 $Z_1 = 3 - j4$ ,  $Z_2 = 4.426 + j4.426$ , and  
 $Z_3 = 2 - j3$


- a)- Determine the value of  $Z_L$  for maximum power to the load. {6 Marks}
- b)- Find  $P_{max}$  {9 Marks}



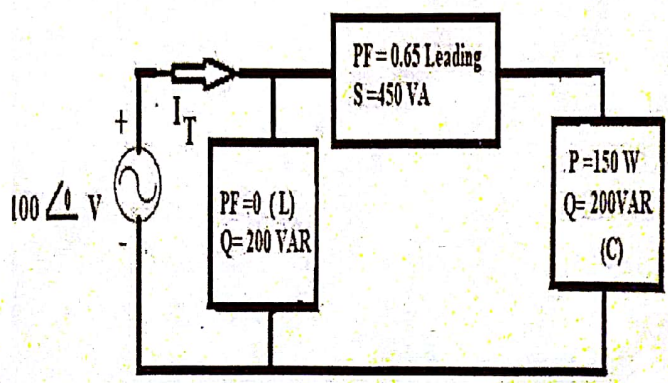**Q4)- {15 Marks}**

For the System shown:

- a)- Draw the power triangle. {9 Marks}
- b)- Find total power factor. {3 Marks}
- c)- Determine the total current  $I_T$ . {3 Marks}





(1)


Q1)  $\omega = 314 \text{ rad/s}$

$\alpha = 90^\circ$

$\alpha = \omega t \Rightarrow t = \frac{\alpha}{\omega} = \frac{90^\circ \times \frac{\pi}{180^\circ} \text{ rad}}{314 \text{ rad/s}} = 5 \text{ ms}$

II ω φ

(L)

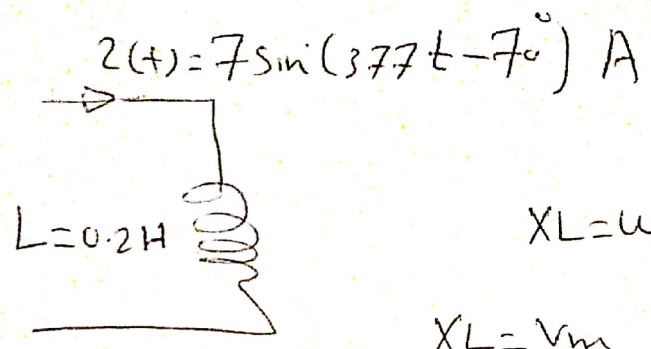


$X_L = \omega L = 377 \times 0.2 = 75.4 \Omega$

$X_L = \frac{V_m}{I_m}$


$V_m = I_m \times X_L = 7 \times 75.4 = 527.8 \text{ V}$

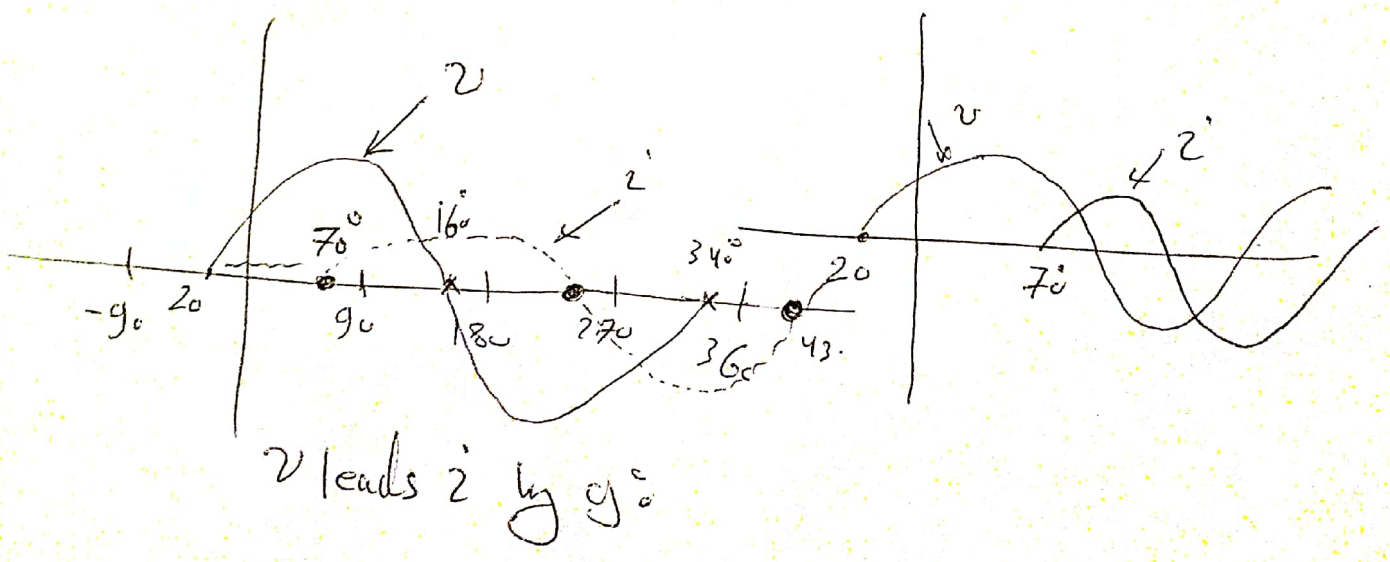$v(t) = 527.8 \sin(377t + 20^\circ) \text{ V}$






Q2) -

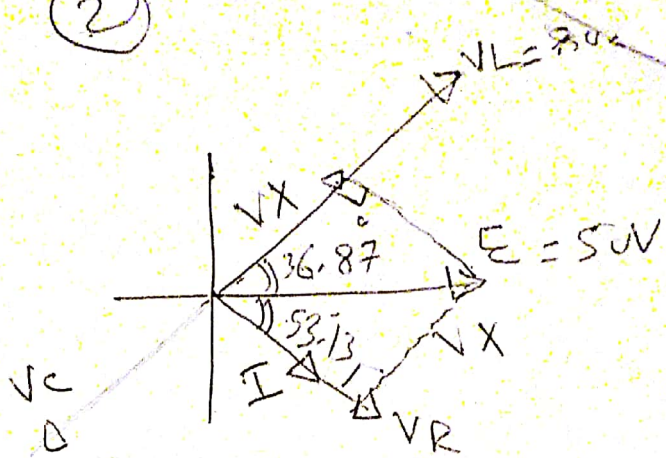

$$\textcircled{1} \quad \cos \theta = \frac{V_R}{E}$$
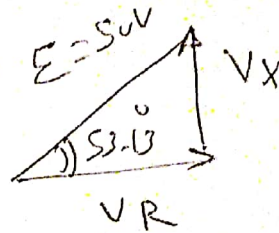
$$V_R = E \cos \theta = 50 \times 0.6 = 30V$$



$$\sin \theta = \frac{V_X}{E} \Rightarrow V_X = E \sin \theta = 50 \times \sin 53.13^\circ = 40V$$

$$V_X = V_L - V_C \\ V_C = 80V - 40V = 40V$$

$$R = \frac{V_R}{I} = \frac{30}{10} = 3 \Omega$$

$$X_L = \frac{V_L}{I} = \frac{80}{10} = 8 \Omega$$

$$X_C = \frac{V_C}{I} = \frac{40}{10} = 4 \Omega$$

$$\textcircled{3} \quad P_{av} = I^2 R = (10)^2 \times 3 = 300W$$

$$P_{av} = E \cdot I \cos \theta = 50 \times 10 \times 0.6 = 300W$$

Since  $V_L = 80V$   
 $I = 10A$   
 $X_L = \frac{80}{10} = 8 \Omega$   
 $Z_T = \frac{E}{I} = \frac{50 \angle 0^\circ}{10 \angle -53.13^\circ} = 5 \angle 53.13^\circ = 3 + j4$   
 $3 + j4 = R + j8 + \overset{R}{\cancel{j8}} + \overset{X_T}{\cancel{-j4}}$   
 $R = 3 \Omega \quad +j4 = +j8 + Z$   
 $Z = +j4 - j8 = -j4 = \underline{\underline{X_C}}$




Q3)

$$Z_1 = 3 - j4 = 5 \angle -53.13^\circ \Omega$$

$$Z_2 = 4.426 + j4.426 = 6.2593 \angle 45^\circ \Omega$$

$$Z_3 = 2 - j3 = 3.605 \angle -56.31^\circ \Omega$$
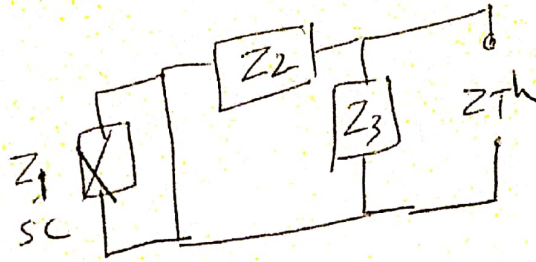
$$Z_{Th} = Z_2 \parallel Z_3 = \frac{Z_2 Z_3}{Z_2 + Z_3}$$




$$Z_{Th} = \frac{6.2593 \angle 45^\circ \times 3.605 \angle -56.31^\circ}{6.582 \angle 12.511^\circ} = 3.428 \angle -23.821^\circ \Omega = 3.1359 + j1.3845$$

For max Power to the Load

$$Z_L = 3.1359 + j1.3845$$
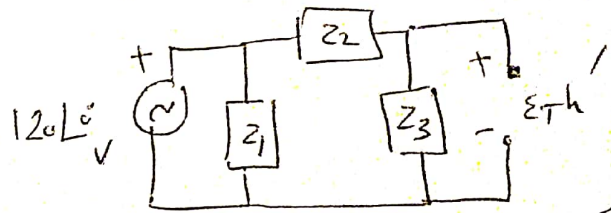
$$\begin{aligned} \mathcal{E}_{Th}' &= V_{Z_3} = \frac{120 \angle 0^\circ \times 3.605 \angle -56.31^\circ}{6.582 \angle 12.511^\circ} \\ &= 65.724 \angle -68.641^\circ \text{ V} \end{aligned}$$




$$\mathcal{E}_{Th} = 23.937 - j61.226$$

$$P_{max} = \frac{\mathcal{E}_{Th}^2}{4R_{Th}} = \frac{(80.9235)^2}{4 \times 3.1359} = 522.211 \text{ W}$$

$$I_x = \frac{6 \angle 0^\circ \text{ A}}{6.582 \angle 12.511^\circ} = 0.911 \angle -12.511^\circ \text{ A}$$

$$\begin{aligned} \mathcal{E}_{Th}'' &= V_{Z_3} = 0.911 \angle -12.511^\circ \times 3.605 \angle -56.31^\circ \\ &= 3.285 \angle -68.821^\circ \end{aligned}$$

$$\mathcal{E}_{Th} = 18.035 - j7.962$$

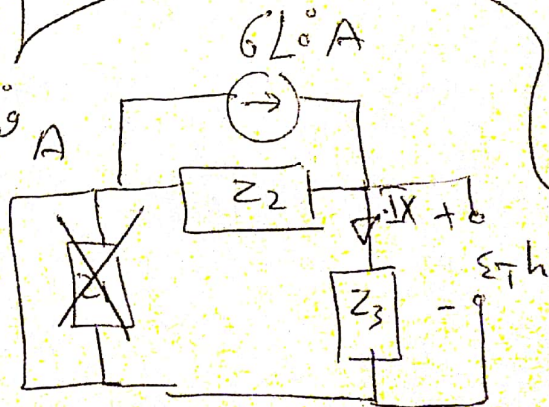

$$\mathcal{E}_{Th} = \mathcal{E}_{Th}' + \mathcal{E}_{Th}'' = 41.972 - j69.188 = 80.9235 \angle -58.757^\circ \text{ V}$$



Q.4)

Load # 1  $P_f = 0(L)$   $S_1 = 0 + j200$

$Q = 200 \text{ VAR}$

Load # 2

$P_{f2} = 0.65$  Leading

$\theta_2 = \cos^{-1} 0.65$

$\theta = 49.45^\circ$

$S_2 = 450 \text{ VA}$

$S_2 = 450 \angle -49.45^\circ$

$= 292.5 - j341.968$

Load # 3

$P_3 = 1500 \text{ W}$

$S_3 = 150 - j200$

$Q_3 = 200 \text{ VAR (C)}$

$S_T = (0 + j200) + (292.5 - j341.968) + (150 - j200)$

$= (442.5 - j341.97)$

$= 559.24 \angle -37.63^\circ \text{ VA}$

$P_{fT} = \cos 37.63 = 0.792$  Leading

$S_T = E \cdot I_T^*$

$I_T^* = \frac{S_T}{E} = \frac{559.24 \angle -37.63^\circ}{100 \angle 0^\circ}$

$I_T^* = 5.5924 \angle -37.63^\circ \text{ A}$

$I_T = 5.5924 \angle 37.63^\circ \text{ A}$

