

Answer the following questions:

Q:[16 Marks]

1- For the circuit shown in figure 1, $\omega L > R$, $R=10\Omega$, and $\alpha=30^\circ$.

- Draw v_s , v_o , v_R , v_L , i_s , i_o , i_L , and i_{D4} .
- Find the average value of v_o , and i_o .
- Find the rms value of i_s , i_L , and i_{D4} .
- Find P_L , PF , f_o , γ .

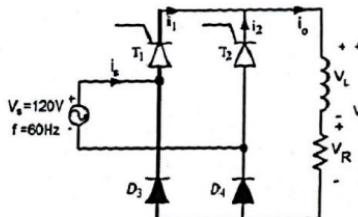


Fig. 1

Q2:[11 Marks]

For the circuit shown in figure 2, $v_i = 150 \sin 2\pi 50t$ [V], $R=10\Omega$, and $\alpha=60^\circ$.

- Draw v_s , v_o , v_T , i_s , i_o , and i_T .
- Find the average value of v_o , and i_o .
- Find the average and rms value of i_T .
- Find P_L , f_o , and PIV for each thyristor.
- Draw the same circuit type using 2 diodes and 2 thyristors.

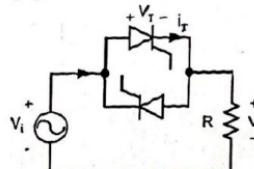


Fig. 2

Q3:[13 Marks]

a-For the circuit shown in figure 3, $V_s = 200V$, $R=50\Omega$, $T=20msec$, and the voltage drop on MOSFET $V_d = 3V$. Find the efficiency η .

b- If the output power $P=194W$, find k , T_{on} , draw v_G , and find the average value of I_Q .

c- Draw the circuit of the single phase bridge inverter.


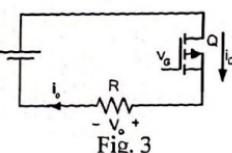


Fig. 3

Q1:

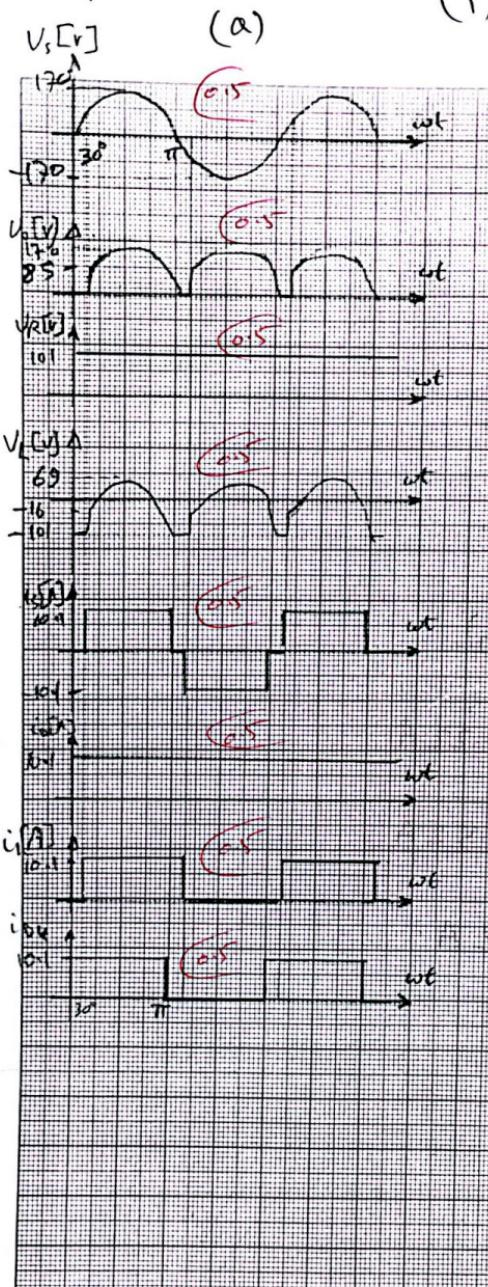

(1)

$$V_m = 120\sqrt{2} \approx 170 \text{ V}$$

$$\text{b) } V_{o,\text{av}} = \frac{V_m}{\pi} (1 + \cos 30^\circ) \quad (1)$$

$$= \frac{120}{\pi} (1 + \cos 30^\circ) \approx 101 \text{ V}$$

$$i_{\text{load}} = \frac{V_{o,\text{av}}}{R} = \frac{101}{10} = 10.1 \text{ A}$$

$$\text{c) } i_{\text{series}} = \sqrt{\frac{1 - \alpha}{\pi}} \times 10.1 \approx 9.21 \text{ A}$$

$$i_{\text{rms}} = \sqrt{\frac{1 - \alpha^2}{2\pi}} \times 10.1 = 7.14 \text{ A}$$

$$i_{\text{D,rms}} = i_{\text{rms}} = 7.14 \text{ A}$$

$$\text{d) } P_L = (i_{\text{rms}})^2 R$$

$$(10.1)^2 \times 10 = 1020 \text{ watt}$$


$$\text{e) } \eta = \frac{P_F}{P_L} = \frac{1020}{1020 \times 9.21} = 0.922$$

$$\text{f) } f_D = 2 \cdot f_1 = 2 \times 60 = 120 \text{ Hz}$$

$$\text{g) } \gamma = \pi f_1 t = 180^\circ$$

Q.:

(2)

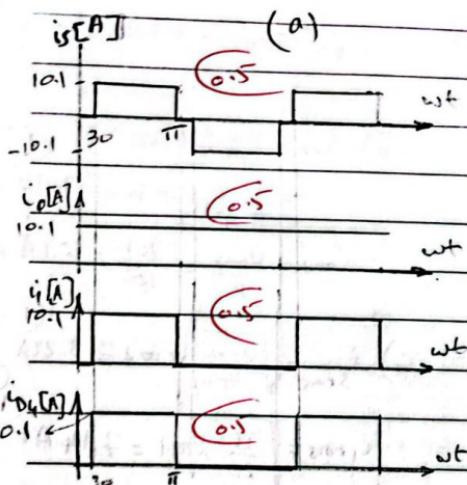


(b),

$$i_{srms} = \sqrt{\frac{\pi - \alpha}{\pi}} \times 10.1 = 9.22 \text{ A} \quad (1)$$

$$i_{srms} = \sqrt{\frac{\pi - \alpha}{2\pi}} \times 10.1 = 6.52 \text{ A} \quad (1)$$

$$i_{drms} = i_{rms} = 6.52 \text{ A} \quad (1)$$

Q 2:

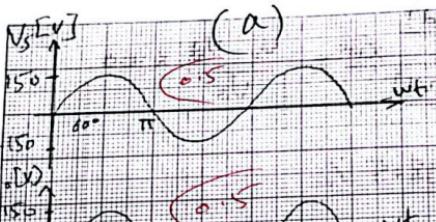

$$V_m = 150 \text{ V}, f = 50 \text{ Hz}$$

$$I_m = \frac{V_m}{R} = \frac{150 \text{ V}}{10 \Omega} = 15 \text{ A}$$

b - $V_{oav} = 0 \text{ V}$. (0.5)

$$I_{oav} = 0 \text{ A}. \quad \text{(0.5)$$


$$C - I_{oav} = \frac{I_m}{2\pi} (1 + \cos 60^\circ) \quad \text{span style="color:red">(1)}$$

$$= \frac{15}{2\pi} (1 + \cos 60^\circ) = 3.5 \text{ A}$$

$$I_{Trms} = \frac{I_m}{2} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin \alpha}{2\pi}}$$

$$= \frac{15}{2} \sqrt{1 - \frac{60}{180} + \frac{\sin 120}{2\pi}} \text{ A}$$
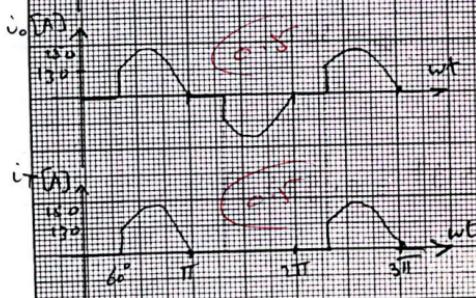
$$= 6.73 \text{ A} \quad \text{span style="color:red">(1)}$$



$$d) I_{Trms} = \frac{I_m}{\sqrt{2}} \sqrt{1 - \frac{\alpha}{\pi} - \frac{\sin \alpha}{2\pi}} \quad \text{span style="color:red">(1)}$$


$$= \sqrt{2} I_{Trms} = 9.52 \text{ A} \quad \text{span style="color:red">(1)}$$

$$P_L = (I_{Trms})^2 R$$

$$= (9.52)^2 \times 10 = 906 \text{ watt}$$

$$f_o = f_i = 50 \text{ Hz} \quad \text{span style="color:red">(0.5)}$$
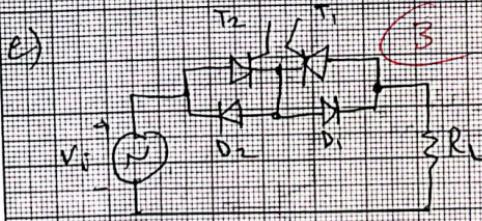
$$P.I.V = 150 \text{ V} = V_m \quad \text{span style="color:red">(0.5)}$$



Q3:


$$a) \eta = \frac{P_L}{P_S} \times 100 = \frac{k(V_S - V_D)^2}{R} \times 100 = \frac{k(V_S - V_D) \times 100}{V_S}$$

$$\eta = \frac{200-3}{200} \times 100 = 98.5\% \quad (2)$$

$$b) P_L = \frac{k(V_S - V_D)^2}{R} = \frac{k(200-3)^2}{50} = 194$$


$$K = \frac{194 \times 50}{(197)^2} = 0.25 \quad (2)$$
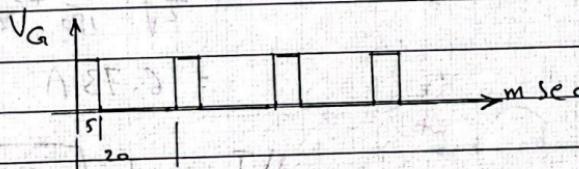
$$T_{on} = K T = 0.25 \times 20 \text{ msec} = 5 \text{ msec} \quad (2)$$



$$I_Q \text{ av} = \frac{k(V_S - V_D)}{R} = \frac{0.25 \times 197}{50} = 0.985 \text{ A} \quad (2)$$

C-

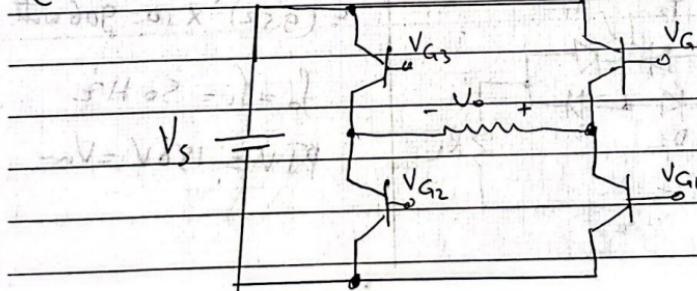

$$V_{G1} = V_{G2} = \bar{V}_{G3} = \bar{V}_{G4}$$

4/4