

Name:


Date: 26/3/2022

Time: 2 hour

Q1: Determine the voltage gain, input impedance, and output impedance with feedback for voltage (in put) current(out put) feedback having  $A= 100$ ,  $Z_{in}= 10\text{ k}\Omega$  ,  $Z_o= 20\text{ k}\Omega$  for feedback of  $\beta= 0.5$ . (6 Marks)


Q2: For the schmitt triger circuit shown:

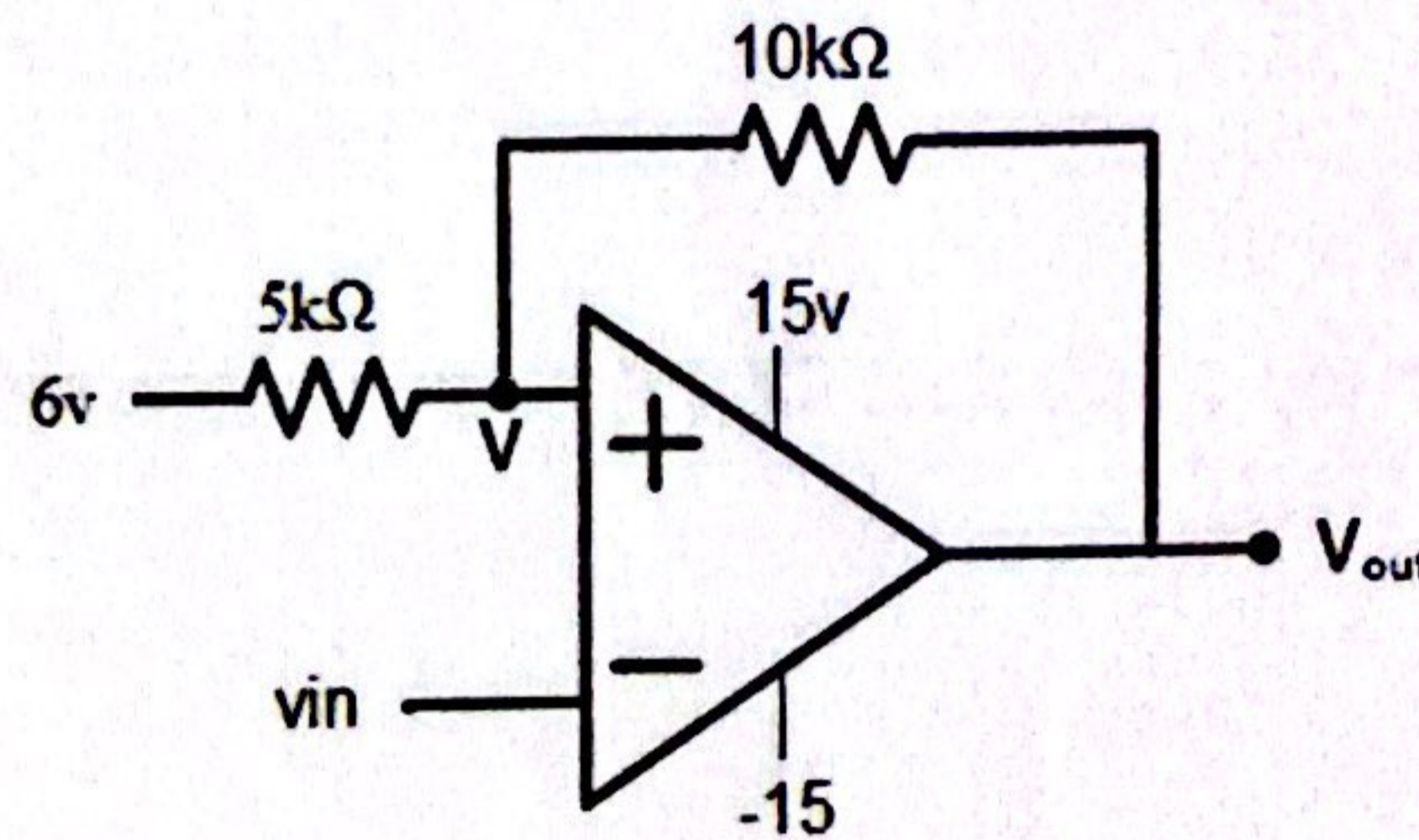- a) Find  $V_{HT}$ ,  $V_{LT}$  , hysteresis and draw the transfer characteristics
  - b) draw  $V_{out}$  if  $V_{in} = 12 \cos \omega t$
- (10 Marks)




Q3: Calculate the output voltage

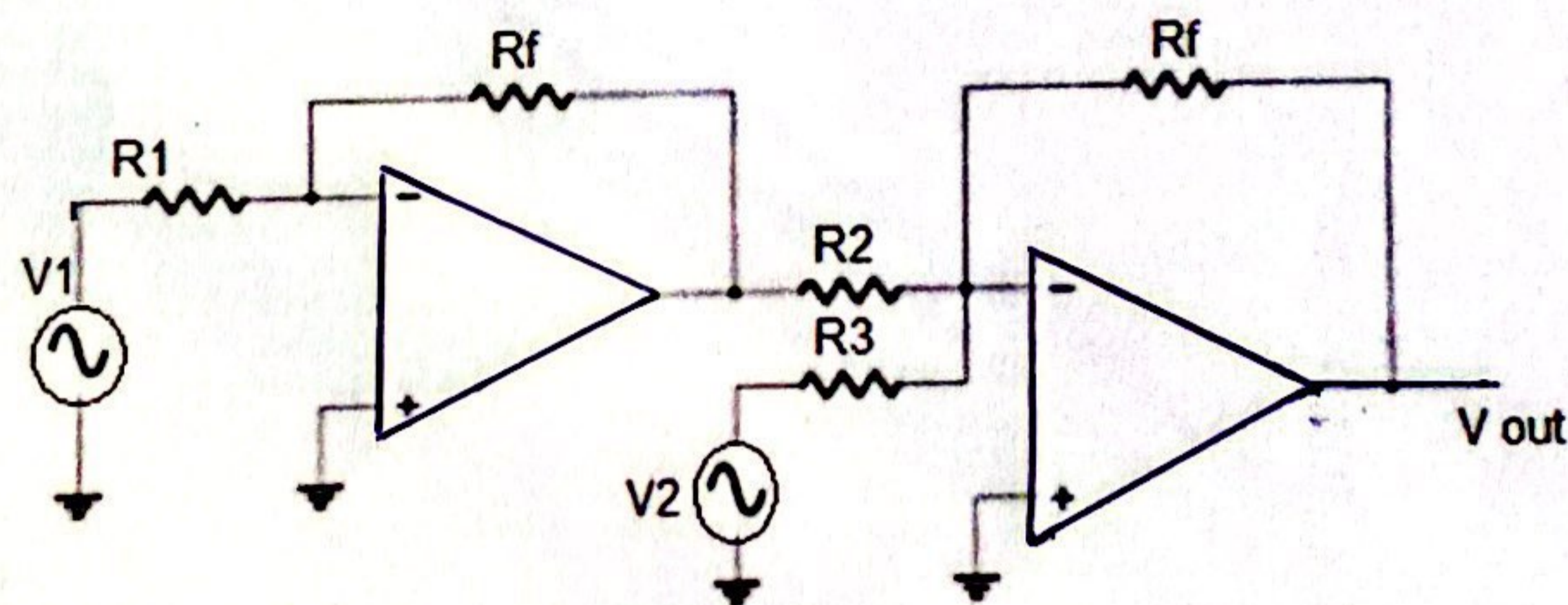- a)  $R_1=10\text{k}\Omega$  ,  $R_2=20\text{k}\Omega$  ,  $R_3=40\text{k}\Omega$  ,  $R_f=20\text{k}\Omega$   
 $V_1=0.5\sin \omega t$  ,  $V_2=2\cos \omega t$




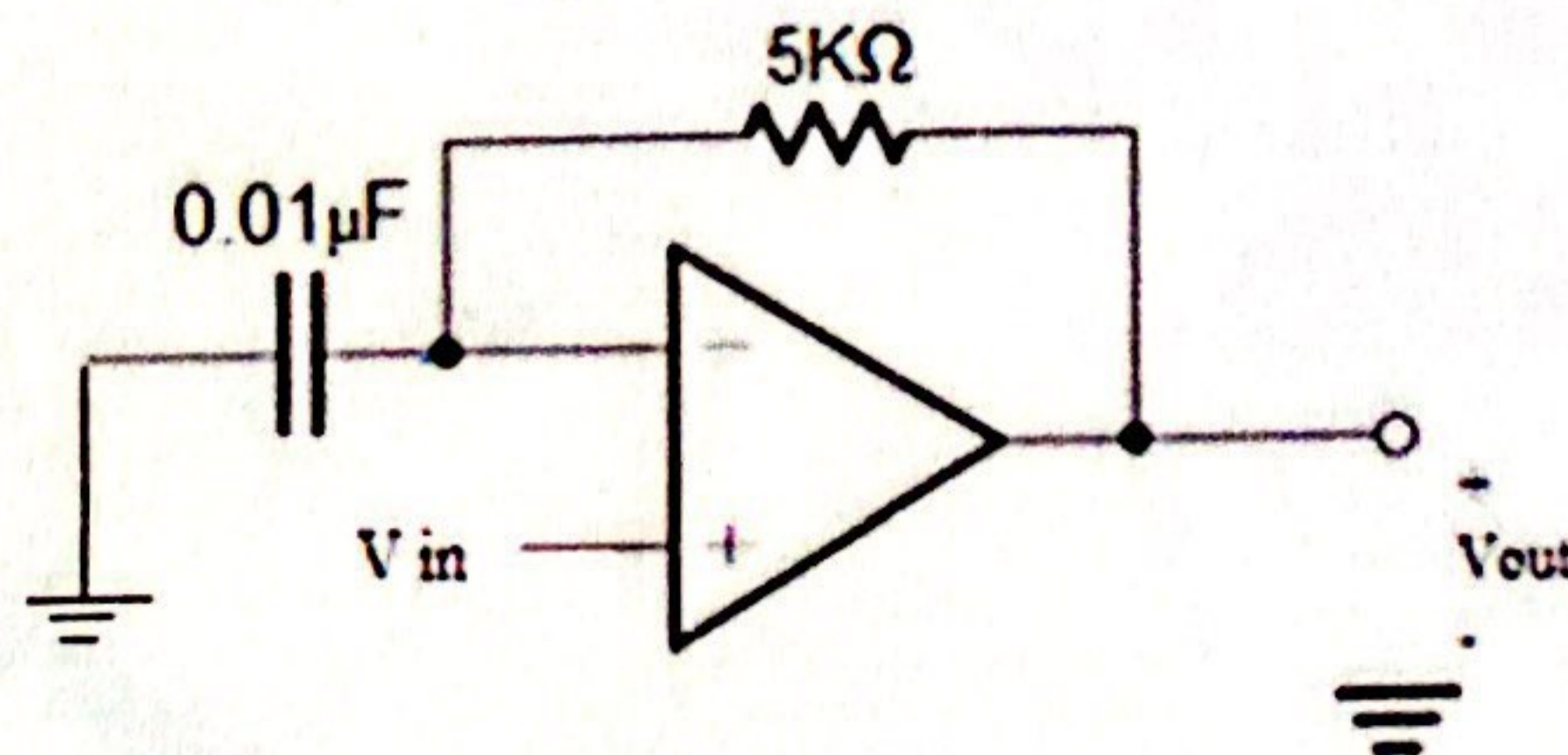- b)  $V_{in} = 2\cos \omega t$  ,  $\omega=20\text{ rad/sec}$



(10 marks)

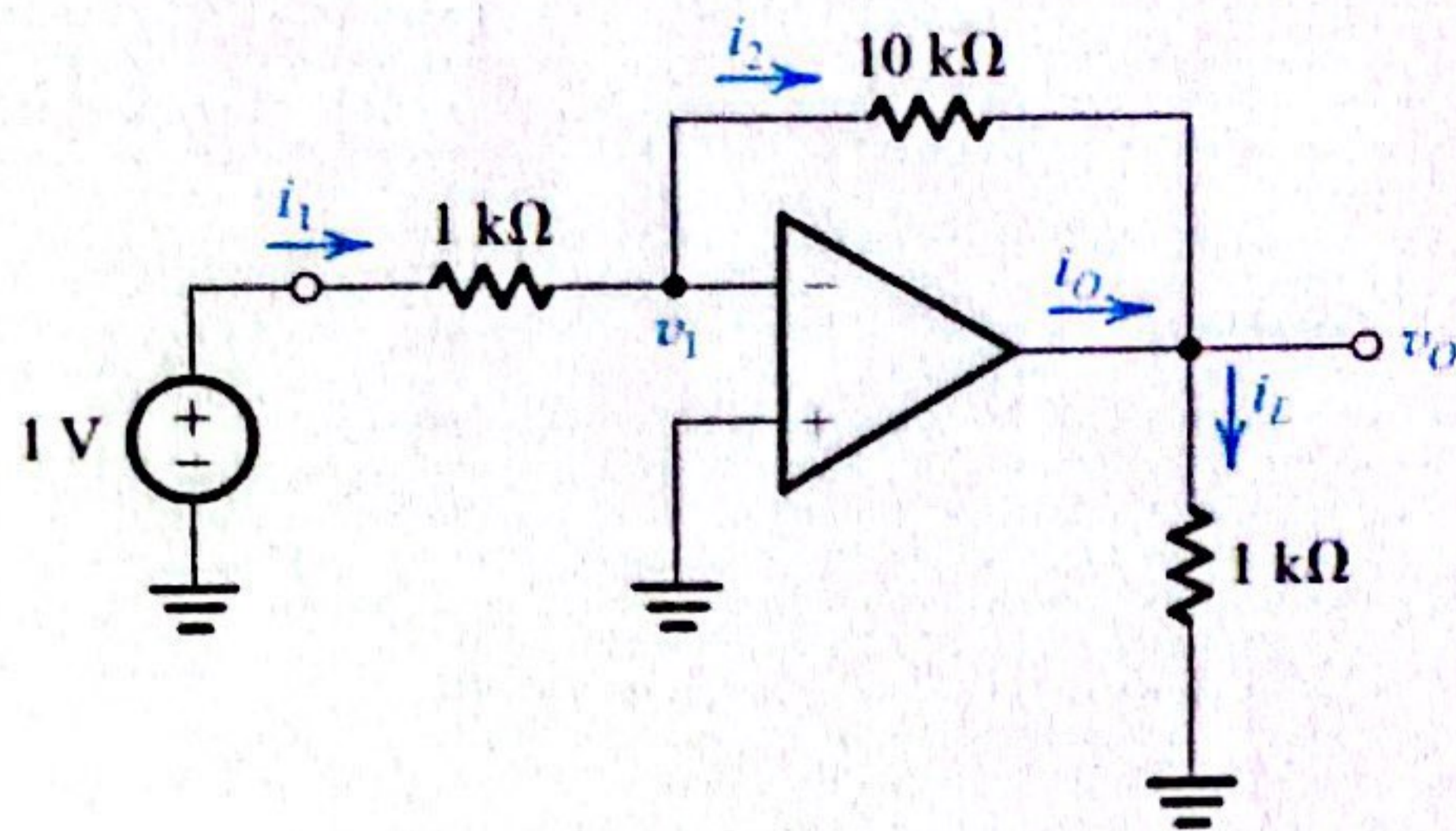Q4: For the circuit below determine the values of  $v_1$ ,  $i_1$ ,  $i_2$ ,  $v_o$ ,  $i_L$ , and  $i_o$ . Also determine the voltage gain, current gain, and power gain.



(7 Marks)

Q5: Design by using one op-amp circuit with inputs  $V_1, V_2$  such that  $V_{out} = 6V_2 - 10V_1$ , draw the circuit.

(7 Marks)

Good luck