

College of Electronic Technology / Tripoli

The final exam of electronic circuit III

Name:.....

Date: 30/10/2022

Time: 2 hours

Q1: [10Marks]

Design a First order HPF with cutoff frequency $f_c = 1\text{kHz}$, and maximum gain $A_v = 10$,

[Using only 10nF capacitors].

a) Draw the circuit.

b) Draw the frequency response.

c) Find v_o if $v_i = 0.2 \sin 2\pi 10kt$ [V].

$$25 \sin$$

d) Find v_i if $v_o = 5 \sin 2\pi 100kt$ [V].

$$0.5 \sin$$


Q2: [10Marks]

1) For the circuit shown find V_o if:

$$V_i = 50 \text{ mV}$$

$$\& V_2 = 10 \sin 2\pi 10^4 t \text{ (v)}$$

2) Find R_C

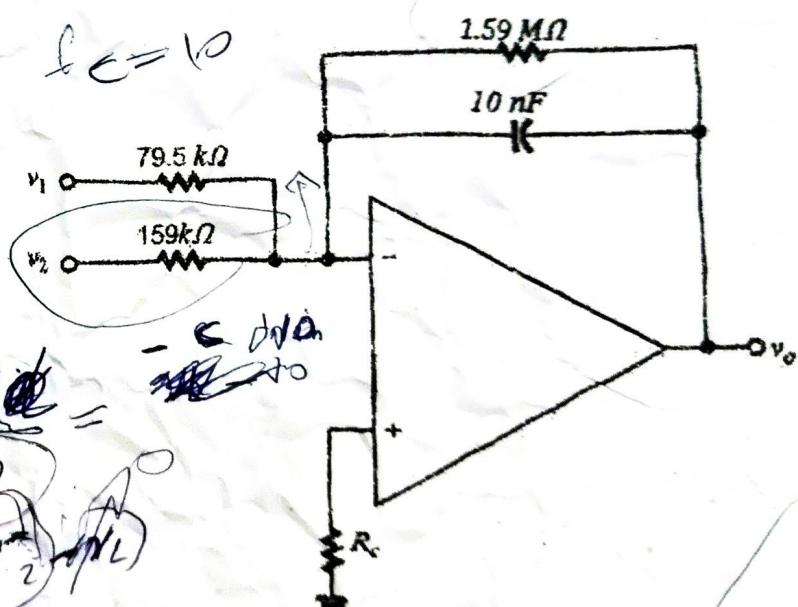


Q3: [10Marks]

For the circuit shown in figure :

- a- Draw the transfer characteristics.
- b- Find the hysteresis h.
- c- Draw v_o if i- $v_i = 5 \sin \omega t$ [V].

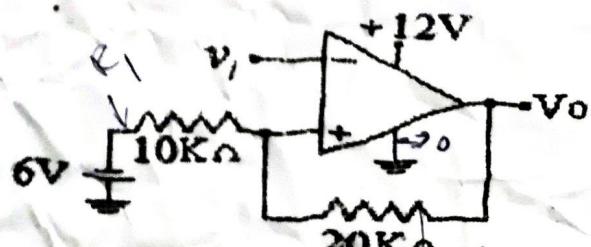
$$ii- v_i = -6 \cos \omega t \text{ [V]}$$



$$VR_C \frac{R_2}{R_1 + R_2} + b + \frac{1}{R_L} (R_L + R_2)$$

Q4: [10Marks]

For the circuit shown below :

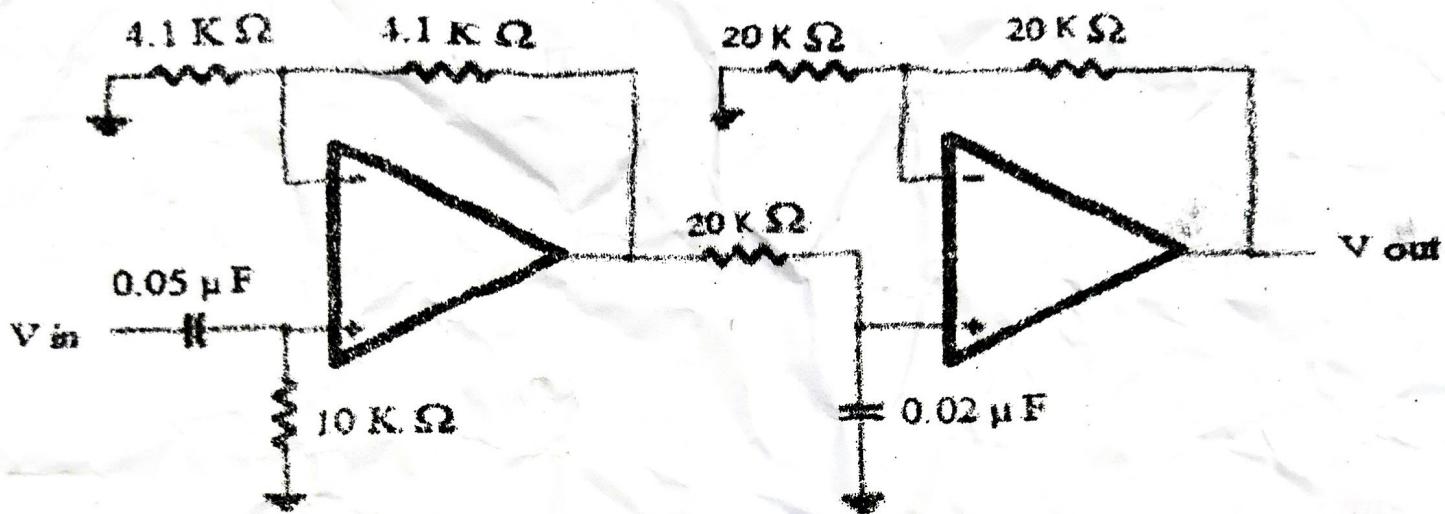

- What is the function of this circuit.
- Draw the frequency response .
- Find the gain at 31.8 HZ.

3 (8)

