

College of Electronic Technology / Tripoli

Date: ١٢ / ٣ / ٢٠٢٠


The midterm exam of electronic circuit III

inverting ~

Time: 2 hours

- 1) Calculate the voltage V_{o1} , V_{o2} and V_{oT} of the circuit.
(5 points)

$$-\frac{1}{CR} \int V_{in} dt$$

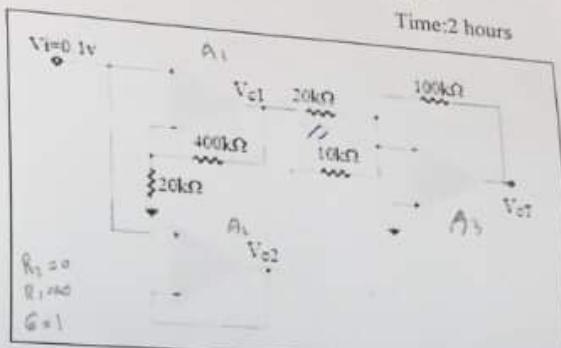



- 2) Use an ideal op amp to design an inverting integrator with an input resistance of $100\text{k}\Omega$ and an integration time constant of 10^{-3}s . Draw the circuit?
(5 points)

- 3) It is required to connect a 10V source with a source resistance of $100\text{k}\Omega$ to a $1\text{k}\Omega$ load. Find the load voltage, the load current and where does the load current come from in each case? (Draw the circuits)
 $\text{VL} = 1\text{V}$

- IF: (a) The source is connected directly to the load.
(2.5 points)


- (b) A unity-gain op-amp buffer is inserted between the source and the load.
(2.5 points)

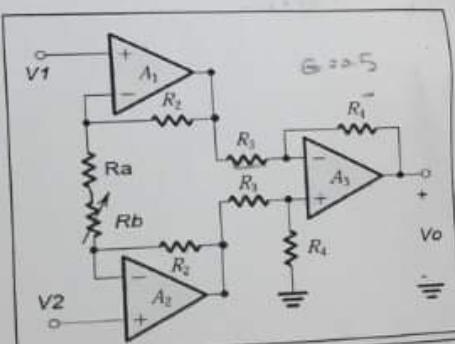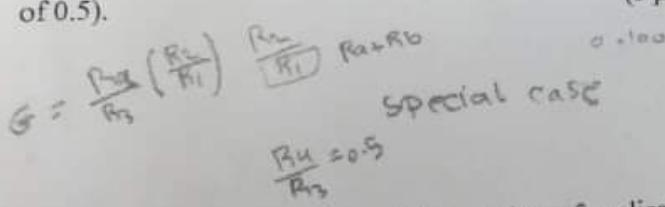- 4) Design the instrumentation-amplifier circuit of to realize a differential gain variable in the range 1 to 100, using a $100\text{k}\Omega$ pot as variable resistor. (Note: Design the second stage for a gain of 0.5).
(5 points)



- 5) The circuit can be configured for a variety of applications by the suitable connection of terminals A, B, C, D, and O. Avoid leaving a terminal open-circuit. Show how the circuit with gains and prove?
(note: single input single output)

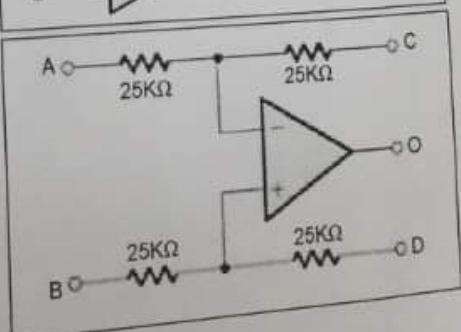- a) -1V/V (2.5 points)
b) $+1\text{V/V}$ (2.5 points)
c) $+2\text{V/V}$ (2.5 points)
d) $+0.5\text{V/V}$ (2.5 points)



good luck