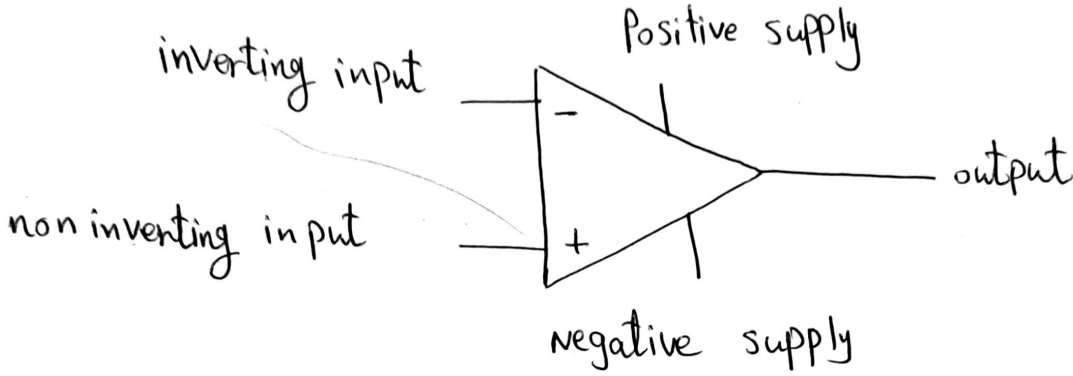



operational Amplifiers (op-amp)



input  $\rightarrow$   $X \rightarrow$   $\boxed{A}$   $\rightarrow$  out =  $X \cdot A$       فكرة عمل المكبر  $\Leftarrow$   
 Gain

\* المكبر هو قطعة الكترونية تستخدم لتكبير وتضخيم الجهود وبتأية تصميمها  
 كان لغرض القيام ببعض العمليات الحسابية وساعد كثيراً في عمليات  
 التكبير وبعض التطبيقات الأخرى مثل استخدامه في دوائر المقارنات و  
 المنظمات .

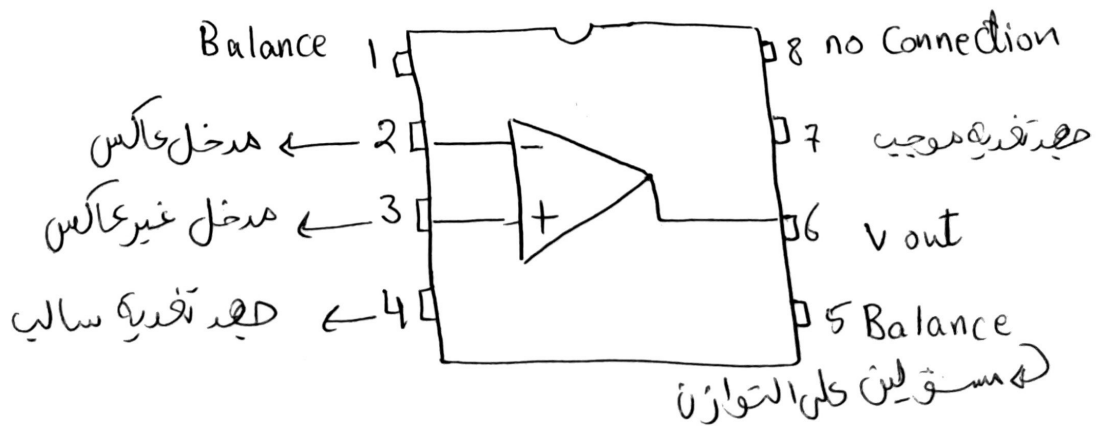لتنغيل المضخم تحتاج لمصدر جهد للتغذية قادر على اعطاء + و - (v)  
 بإمكان المكبر أن يكبر الإشارة و يعكس القطبية ويجعل كفلتر وكمقارن




# Ideal op-Amp


	قیمی	قیمی	
A	$10^5 \rightarrow 10^8$	$\infty$	] A <sub>OL</sub>
R <sub>i</sub>	$10^5 \rightarrow 10^8 (\Omega)$	$\infty$	
R <sub>o</sub>	$10 \rightarrow 100 (\Omega)$	0	

$\begin{matrix} + \\ - \end{matrix} V_{CC} \quad 5 \rightarrow 24 (V)$

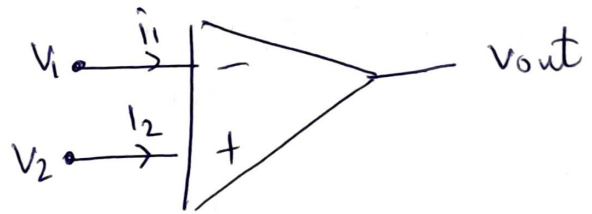$\therefore \begin{matrix} i_1 = 0 \\ i_2 = 0 \\ V_1 = V_2 \end{matrix}$



$R_0$

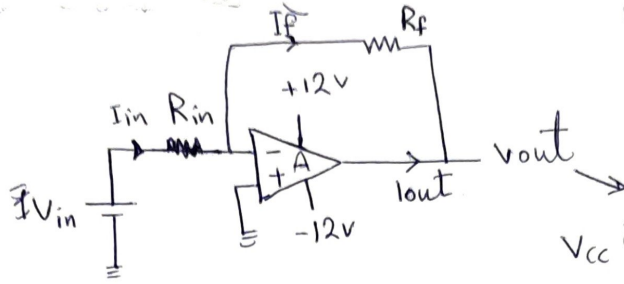

Close loop Gain  
Feedback هو مقدار  $\frac{V_o}{V_s}$  بوجود FB

لاذ م ما يكون التيارين  $V_{cc}$

\* inverting op-amp

$$V_{out} = A \cdot V_{d1} \Rightarrow A \cdot (V_2 - V_1)$$

$$V_d = V_2 - V_1$$


$$V_{out} = -\frac{R_f}{R_{in}} \times V_{in} \quad = \text{قانون التضخم العكس}$$

$$\text{Gain (Av)} = \frac{V_{out}}{V_{in}} = -\frac{R_f}{R_{in}}$$

$R_f \Rightarrow V_{out}$  هي المقاومة بين طرفين Inverting

$R_{in} \Rightarrow V_{in}$  هي المقاومة بين طرفين Inverting، والإشارة الداخلة  $V_{in}$

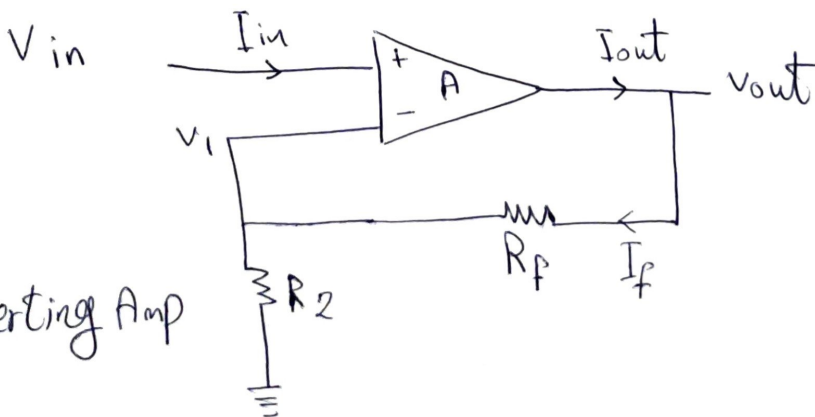Gain (Av): هو معامل تكبير الإشارة ويبدل على عدد مرات تكبير الإشارة الدخل



\* non Inverting Amp

$$A(v) = 1 + \frac{R_f}{R_2}$$

$$V_1 = \frac{R_2}{R_2 + R_f} \times V_{out}$$

Ideal summing point  $\Rightarrow V_1 = V_{in}$

Voltage Gain  $A(v)$  is equal to:  $\frac{V_{out}}{V_{in}}$


$$\text{Then: } A(v) = \frac{V_{out}}{V_{in}} = \frac{R_2 + R_f}{R_2}$$

$$A(v) = \frac{V_{out}}{V_{in}} = 1 + \frac{R_f}{R_2} \quad A \geq 1$$


مكبر مقارن Comparator Amp

الهدف منه مقارنته  $\rightarrow$  بين عند المبدئين وانتاج اسل وبتل على الحجة الأكبر


1) Non inv. Comparator

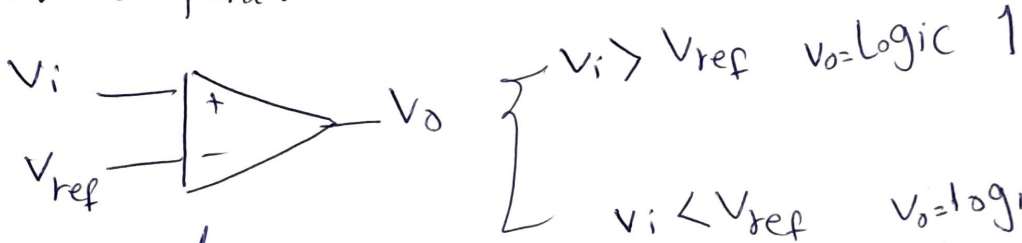

2) inv. Comparator

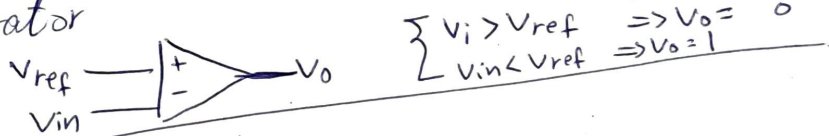

Voltage follower Buffer

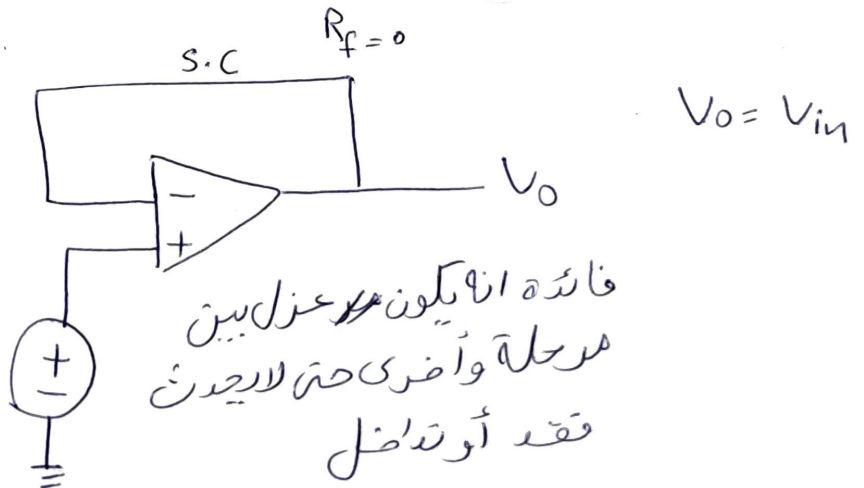


نستفاد من هذا النوع لما يكون عندنا اكثر من مرحلة تكبير خلية في الوسط حتى لا يحدث تداخل

فانده انما يكون عزولين مرحلة واضرر حدة لا يحدث فقد اوت تداخل

Ex :-

Inverting op-amp

1)

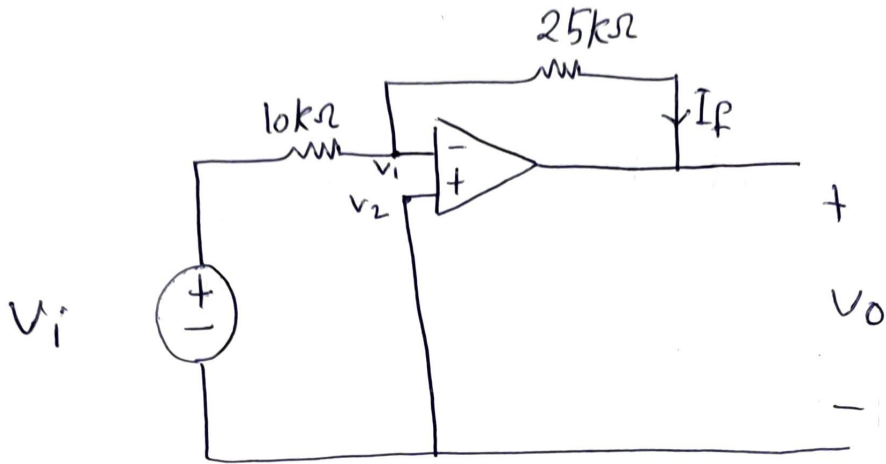

for  $V_i = 0.5V$  find :- 1)  $V_o$   
2)  $I_f$

$\therefore$  inverting op amp


1)  $\therefore V_{out} = -\frac{R_f}{R_{in}} \times V_{in}$

$$= \frac{-25k}{10k} \times 0.5V = -1.25 \text{ volt}$$

2)  $I_f = \frac{V_i - V_o}{R_f} \Rightarrow V_i = 0$

$$I_f = \frac{0 - (-1.25)}{25k\Omega} = 0.05 \text{ mA}$$

2)

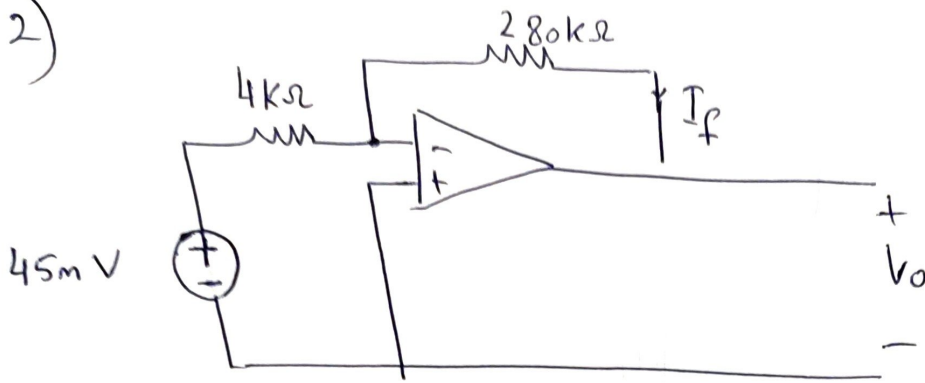

Ideal op-amp  
inverting op-amp

Find  $\frac{V_o}{V_i}$ ,  $V_o$  and  $i_f$

$$\frac{V_o}{V_i} = -\frac{R_f}{R_{in}}$$

Gain :-  $\frac{V_o}{V_i} = -\frac{280}{4} = -70$

$$V_o = \frac{-R_f}{R_{in}} \cdot V_i$$


$$= -70 \times 45\text{mV} = -3.15\text{ Volt}$$

$$i_f = \frac{V_i - V_o}{R_f} = \frac{0 - (-3.15)}{280\text{k}\Omega} = \frac{3.15}{280\text{k}\Omega} = 11.25\text{mA}$$

\* Non-inverting op-amp

Ex

find  $V_o$

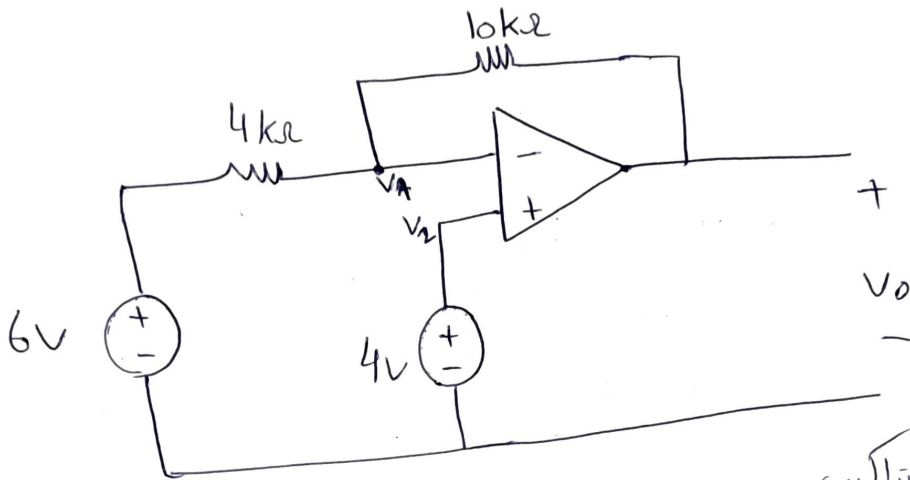

by using superposition theorem :- بواسطة نظرية التراكيب

A  $V_o = V_{o1} + V_{o2}$



6V effect  $\Rightarrow V_{o1} = -\frac{10}{4} \times 6$

$V_{o1} = -15V$

4V effect  $\Rightarrow V_{o2} = \left(1 + \frac{10}{4}\right) \times 4$

$= 14V$

$\Rightarrow V_o = -15 + 14 = -1V$

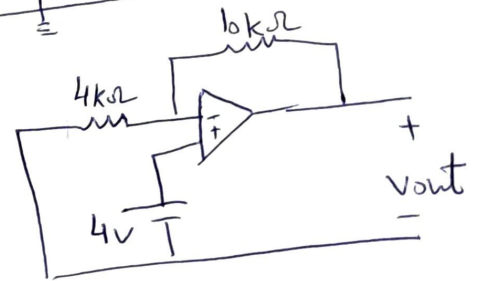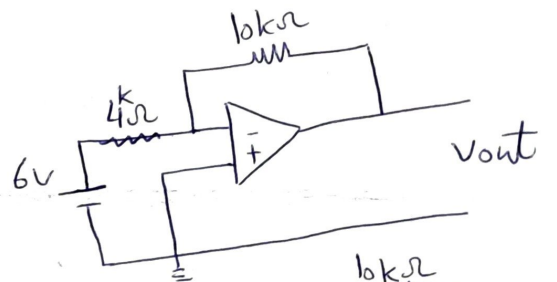

OR by using KCL  $\therefore \frac{6 - V_1}{4k\Omega} = \frac{V_1 - V_o}{10k\Omega}$

$\therefore V_1 = V_2 = 4$

$\frac{6 - 4}{4k\Omega} = \frac{4 - V_o}{10k\Omega}$

$\therefore V_o = -1V$

~~Find~~ Find  $v_o$  ① for  $\left. \begin{matrix} 741 \\ 351 \end{matrix} \right\} \begin{matrix} \text{logic 1} = +V_{CC} \\ \text{logic 0} = -V_{CC} \end{matrix}$



Comparator

② 710  $\Rightarrow$   $\begin{matrix} \text{logic 1} = 3.2V \\ \text{logic 0} = -0.6V \end{matrix}$

Ex:- find  $v_{out}$  assuming 710 comparator  
if  $v(t) = 10 \sin \omega t$

if  $v_i > v_{ref} \Rightarrow v_{out} = 3.2V$

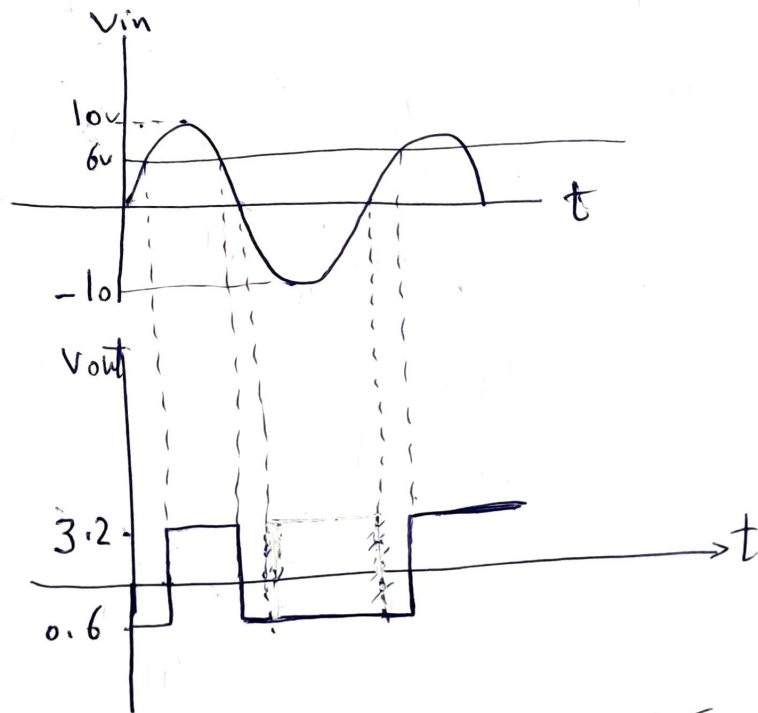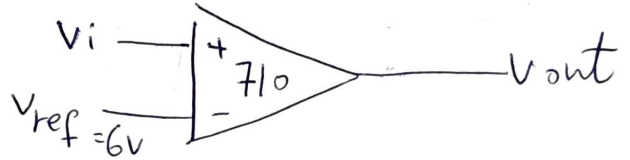
if  $v_i < v_{ref} \Rightarrow v_{out} = -0.6V$




حوالت اشارة الإخفاق من موجة جيبية إلى باس 0,1



open loop gain and close loop gain

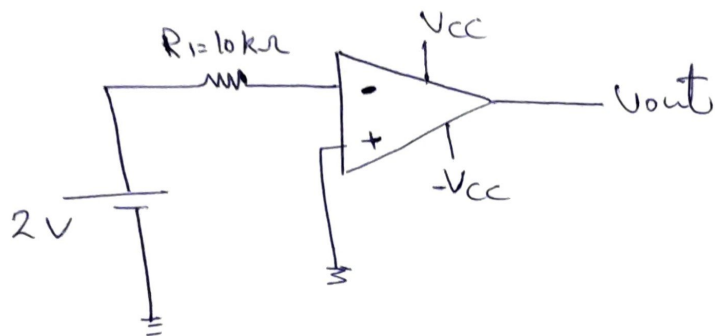

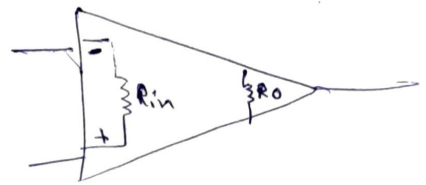1) find  $V_o$  when  $A = 2 \times 10^5$   
 $R_{in} = 2M\Omega$   
 $R_o = 50\Omega$



$$V_o = A_{OL} V_{in}$$

$$= (2 \times 10^5)(2) = 400000 \text{ V (saturated)} \quad V_o = V_{CC}$$


2) close loop gain when  $R_f = 20k\Omega$

$$A_{CL} = \frac{-R_f}{R_{in}} = \frac{-20k\Omega}{10k\Omega} = -2$$

$$V_o = -2(2) = -4 \text{ V}$$
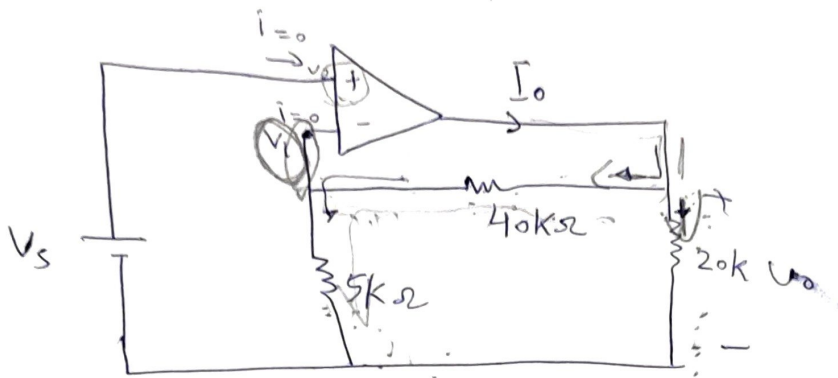
#

Ex 3- find  $\frac{V_o}{V_s}$  and  $I_o$  when  $V_s = 1$  volt



بیم آن لم جدید پارامتران :: تجربه مثالی  
و نقل

$i_1 = 0$       في المثالي  
 $i_2 = 0$

$$V_1 = V_2 = V_s \quad |$$

VDR

$$V_1 = \frac{V_o \times 5}{5 + 40}$$

$$V_s = V_o \frac{5}{45} \Rightarrow \frac{V_o}{V_s} = 9 \quad = \text{Close loop voltage gain}$$

$$V_s \cdot 45 = V_o \cdot 5$$

$$I_o = \frac{V_o}{(5+40)k} + \frac{V_o}{20}$$

$$V_s = 1 \text{ volt}$$

$$V_o = 9 \text{ V}$$

$$I_o = \frac{9}{45k} + \frac{9}{20k} = 0.657 \text{ mA}$$

Ex:-

Design an op-amp circuit that will produce the output

$$V_o = \sin \omega t \quad \& \quad V_{in} = 2 \sin \omega t$$


Solution :-

$$A = \frac{V_o}{V_{in}} = \frac{\sin \omega t}{2 \sin \omega t} = \frac{1}{2}$$

$$A = \frac{-R_f}{R_{in}} = \frac{1}{2}$$

$$R_{in} = 2 R_f$$
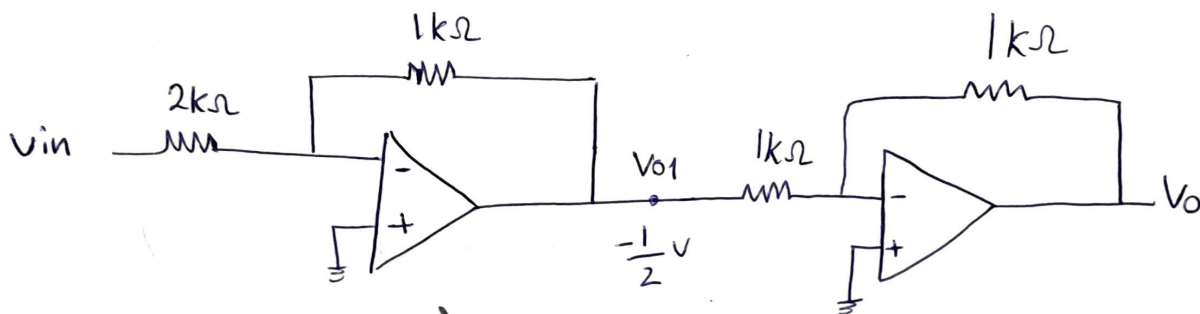
$$\text{let } R_f = 1k \quad \& \quad R_{in} = 2k$$




$$V_{01} = -\frac{1}{2} (2 \sin \omega t)$$

$$V_o = A \cdot V_{in}$$

$$= \frac{-1k\Omega}{1k\Omega} (-\sin \omega t) = \sin \omega t$$

$$\therefore V_o = \sin \omega t$$

Ex 8-

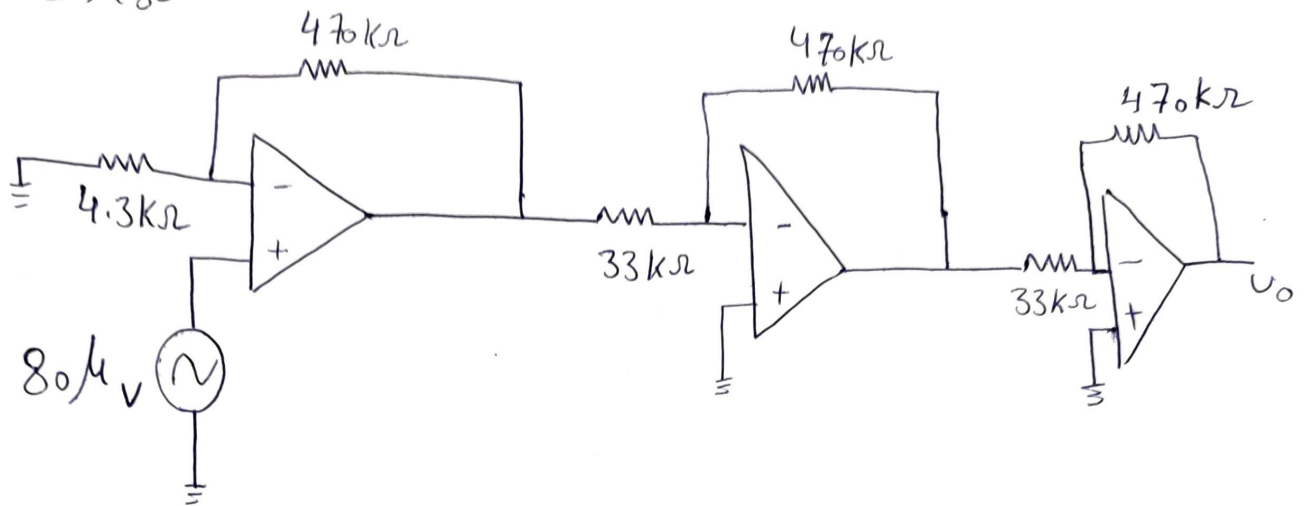

calculate the output voltage  
Solution:-

The amplifier gain is

$$A = A_1 A_2 A_3$$

$$= \left(1 + \frac{R_f}{R_i}\right) \left(-\frac{R_f}{R_2}\right) \left(-\frac{R_f}{R_3}\right)$$

$$= \left(1 + \frac{470 \text{ k}\Omega}{4.3 \text{ k}\Omega}\right) \left(\frac{-470 \text{ k}\Omega}{33 \text{ k}\Omega}\right) \left(\frac{-470 \text{ k}\Omega}{33 \text{ k}\Omega}\right)$$

$$= 22 \times 10^3$$

$$V_o = A V_i$$

$$= 22 \times 10^3 (80 \mu\text{V}) = 1.78 \text{V}$$

Ex :- Find  $v_o$  and  $i_o$

19/1/2022


الإحصاء - ١٠ - ٢٠٢٢

25/1/2022 الأوقات المتصلة ١١:٠٠

Summing Amplifier :-

"المكبر الجامع"

يقوم بجمع الجهود الموجودة عند الدخل

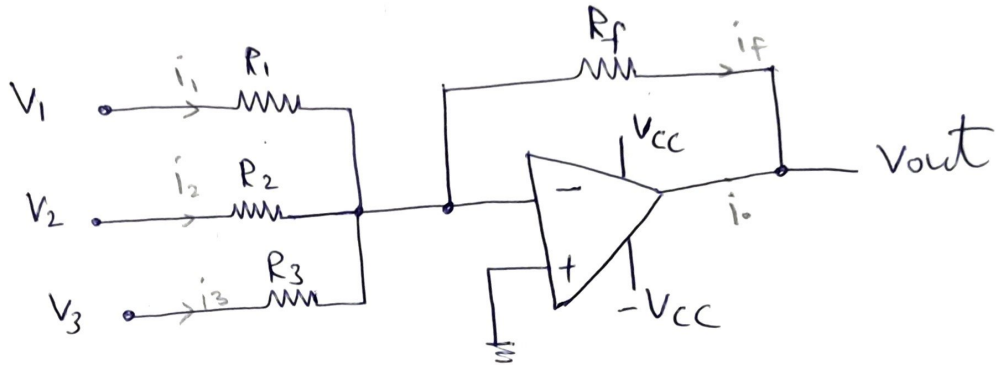

by using superposition theorem


$$\therefore V_{out} = A_{CLV1} \cdot V_1 + A_{CLV2} \cdot V_2 + A_{CLV3} \cdot V_3$$

$$A_{CLV1} = \frac{-R_f}{R_1}, \quad A_{CLV2} = \frac{-R_f}{R_2}, \quad A_{CLV3} = \frac{-R_f}{R_3}$$

$$\therefore V_{out} = -\frac{R_f}{R_1} (V_1) + -\frac{R_f}{R_2} (V_2) + -\frac{R_f}{R_3} (V_3)$$

$$* \quad V_{out} = -\left( \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$

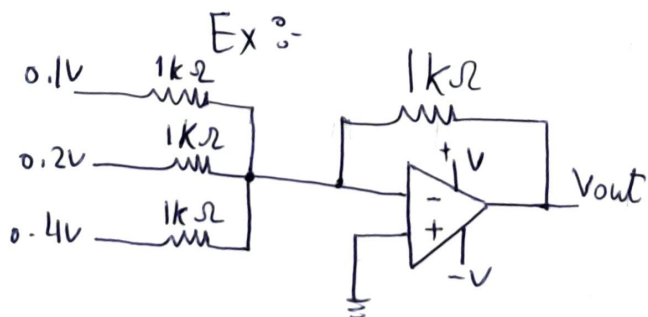
$$V_{out} = -(V_1 + V_2 + V_3) \quad \text{عندما } R_1 = R_2 = R_3 = R_f$$



find  $V_{out}$

$$\begin{aligned} \Rightarrow V_{out} &= -(V_1 + V_2 + V_3) \\ &= -(0.1 + 0.2 + 0.4) \\ &= -0.7V \end{aligned}$$

Ex:-

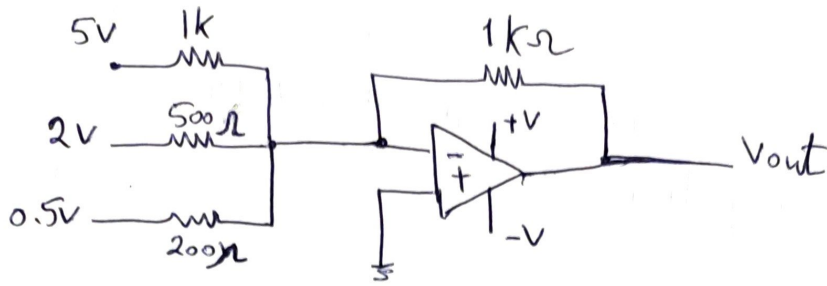


Find  $V_{out}$

$$V_{out} = - \left( \frac{R_f}{R_1} \cdot V_1 + \frac{R_f}{R_2} \cdot V_2 + \frac{R_f}{R_3} \cdot V_3 \right)$$

$$= - \left( \frac{1k}{1k} \times 5 + \frac{1k}{500} \times 2 + \frac{1k}{200} \times 0.5 \right)$$

$$= - (5V + 4V + 2.5V) = -11.5V$$

Ex:-

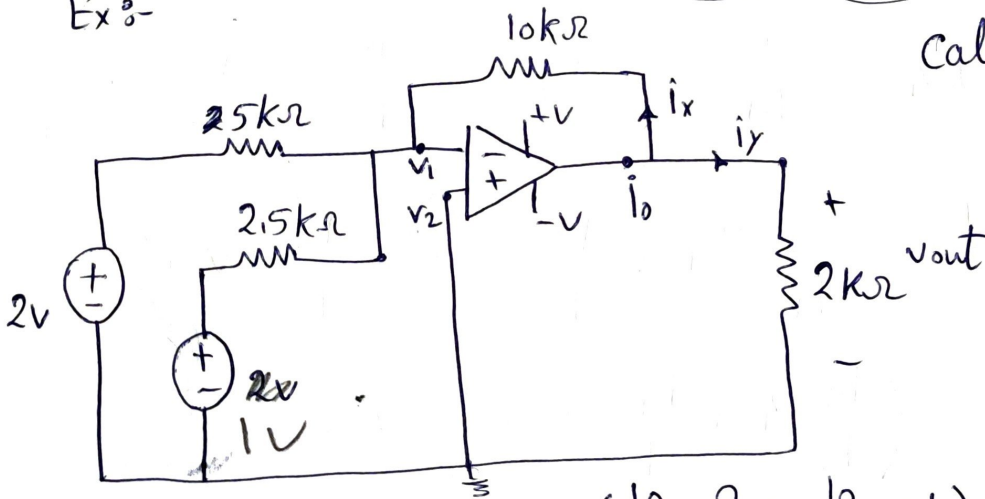


Calculate  $V_o$  &  $i_o$   
in the op-Amp circuit

$$V_o = - \left( \frac{10}{5} \times 2 + \frac{10}{2.5} \times 1 \right) = -8 \text{ volt}$$

$$i_o = \frac{V_o - V_1}{R_f} + \frac{V_o - 0}{R_{2k\Omega}}$$

$$= \frac{-8}{10k} + \frac{-8}{2k} = -4.8 \text{ mA}$$

Ex:- Find  $V_o$  and  $i_o$

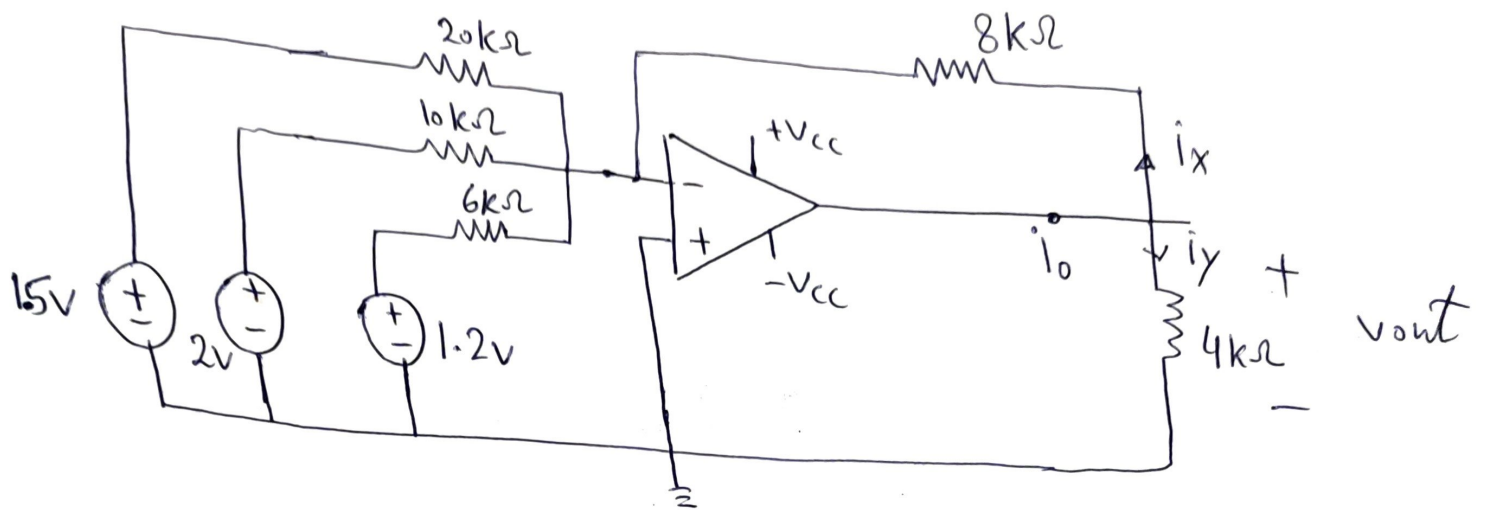

$$V_{out} = - \left( \frac{8k}{20k} \times 1.5 + \frac{8k}{10k} \times 2 + \frac{8k}{6k} \times 1.2 \right)$$

$$= - 3.8 \text{ V}$$

$$i_o = i_x + i_y$$

$$= \frac{V_o - 0}{8k\Omega} + \frac{V_o - 0}{4k\Omega}$$

$$= \frac{-3.8 \text{ V}}{8k\Omega} + \frac{-3.8 \text{ V}}{4k\Omega} = -1.425 \text{ mA}$$


$$\frac{0 - V_o}{8k\Omega} + \frac{V_o - 0}{4k\Omega}$$

$$\frac{3.8}{8k\Omega} + \frac{-3.8}{4k\Omega} = 0.475 - 0.95 = -0.475$$



# Subtraction op-Amp

المكبر الطرح

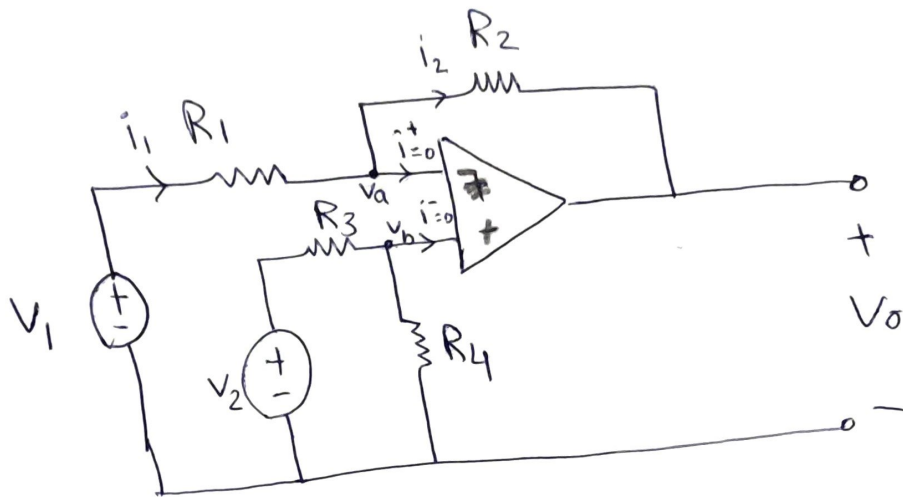

$$i^+ = i^- = 0$$

$$\hat{i}_1 = \hat{i}_2 = \frac{V_1 - V_a}{R_1} = \frac{V_a - V_o}{R_2}$$

$$R_1(V_a - V_o) = R_2(V_1 - V_a)$$

$$R_1 V_a - R_1 V_o = R_2 V_1 - R_2 V_a$$

$$R_2 V_1 - R_2 V_a - R_1 V_a = -R_1 V_o$$

$$- \frac{R_2 V_1}{R_1} + \frac{R_2 V_a}{R_1} + \frac{R_1 V_a}{R_1} = V_o$$

$$\left(1 + \frac{R_2}{R_1}\right) V_a - \frac{R_2}{R_1} V_1 = V_o$$

$$\therefore V_o = \left(1 + \frac{R_2}{R_1}\right) V_a - \frac{R_2}{R_1} V_1$$

$\therefore V_a = V_b$  for ideal op-Amp

$$V_b = V_{4\Omega}$$

$$V_a = V_b = V_2 \cdot \frac{R_4}{R_3 + R_4}$$

$$* \therefore V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) \cdot V_2 - \frac{R_2}{R_1} V_1$$

$$* V_o = \frac{R_2 (1 + R_1/R_2)}{R_1 (1 + R_3/R_4)} \cdot V_2 - \frac{R_2}{R_1} V_1$$

if:  $\frac{R_2}{R_1} = \frac{R_4}{R_3}$  or  $\frac{R_1}{R_2} = \frac{R_3}{R_4}$

$$= V_o = \frac{R_2}{R_1} \cdot V_2 - \frac{R_1}{R_2} \cdot V_1$$

$$V_o = \frac{R_2}{R_1} (V_2 - V_1)$$

$V_o = 0$  when  $V_1 = V_2$

$$R_2 = R_1 \quad \& \quad R_3 = R_4$$

Gain = 1 &  $V_0 = V_2 - V_1$  من أجل أن لا يحدث تكبير

Ex: 1

Design an op-Amp circuit with inputs  $V_1$  &  $V_2$  such that :  $V_0 = 3V_2 - 5V_1$

الحل : تصميم باستخدام مكبر واحد

$$V_0 = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_2 - \frac{R_2}{R_1} V_1$$

$$\frac{R_2}{R_1} = 5 \Rightarrow R_2 = 5R_1$$

نفرض :  $R_1 = 10k\Omega$   
 $\Rightarrow R_2 = 50k\Omega$

$$\frac{R_2}{R_1} = 5 \Rightarrow \left(1 + \frac{R_2}{R_1}\right) = 6$$

$$6 \left(\frac{R_4}{R_3 + R_4}\right) = 3$$

$$\frac{2}{3} R_4 = \frac{3R_3 + R_4}{3}$$

$$2R_4 = R_3 + R_4 \Rightarrow R_4 = R_3$$


$$2R_4 - R_4 = R_3 \Rightarrow R_4 = R_3$$

نفرض أن  $R_3 = 10k$

$$\therefore R_4 = 10k$$




الحل بطريقة أخرى

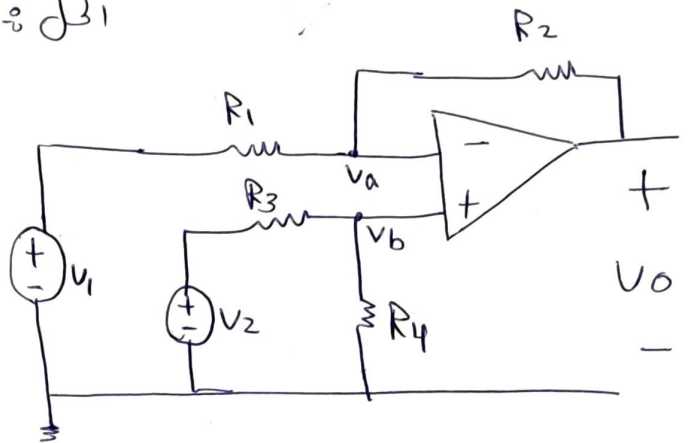

الحل باستخدام نوعين من المكبرات  
inverting amp

two input inverting summer

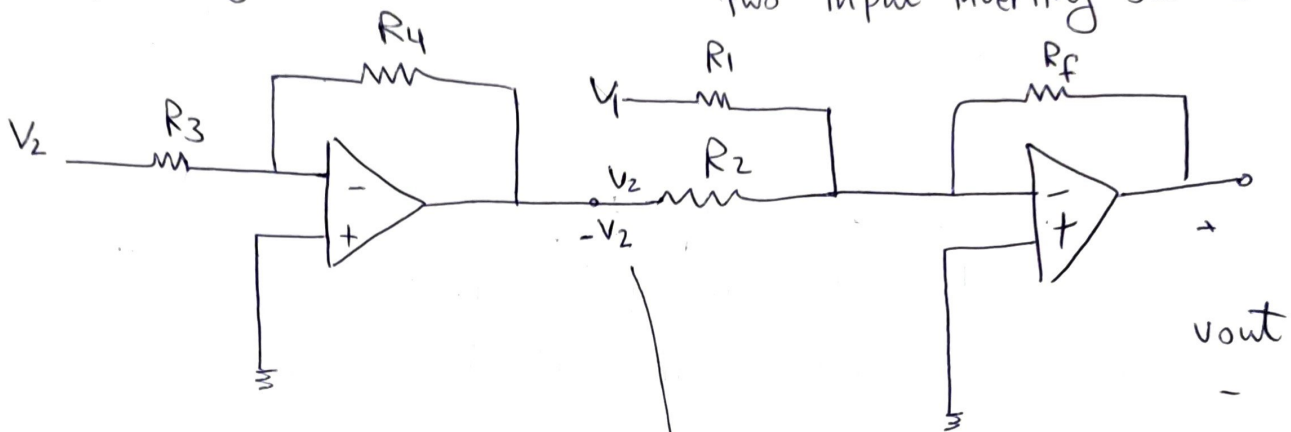

$$R_4 = R_3 = 10 \text{ k}\Omega$$

$$R_f = 15 \text{ k}\Omega$$

$$R_1 = 3 \text{ k}\Omega$$

$$R_2 = 5 \text{ k}\Omega$$

$$1) \quad v_{out} = \frac{-10 \text{ k}}{10 \text{ k}} \cdot V_2$$

$$v_{out} = -V_2$$

$$2) \quad v_{out} = -\frac{R_f}{R_2} \cdot (V_2) + \left(-\frac{R_f}{R_1}\right) V_1$$


$$= -\frac{15 \text{ k}\Omega}{5 \text{ k}\Omega} (-V_2) - \frac{15 \text{ k}\Omega}{3 \text{ k}\Omega} V_1$$

$$= 3V_2 - 5V_1$$

Ex 9:-

Find  $V_o$  if  $V_{in1} = 10 \sin(2\pi 60t) - 0.1 \sin(2\pi 1000t)$
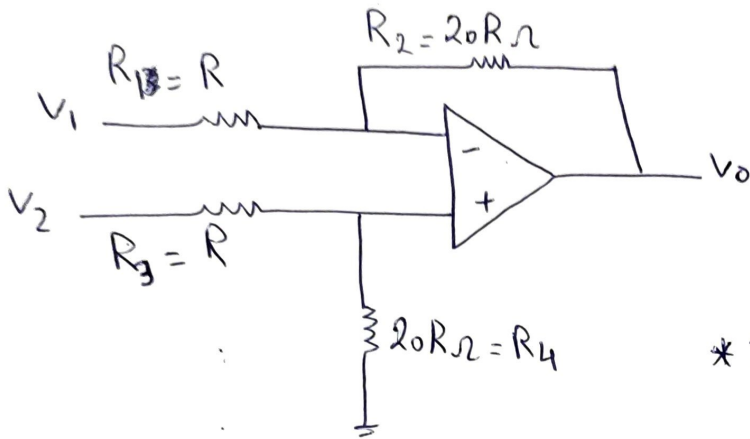
$$V_{in2} = 10 \sin(2\pi 60t) + 0.1 \sin(2\pi 1000t)$$



\* subtraction op amp

$$\therefore \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

$$\therefore V_o = \frac{R_2}{R_1} (V_2 - V_1)$$

$$= \frac{20R}{R} (10 \sin(2\pi 60t) + 0.1 \sin(2\pi 1000t) - 10 \sin(2\pi 60t) + 0.1 \sin(2\pi 1000t))$$

$$20 (0.2 \sin(2\pi 1000t)) = 4 \sin(2\pi 1000t)$$

Ex: 2

Design a difference amp with gain 5.

$$V_0 = 5(V_2 - V_1)$$

if  $R_1 = R_3$  ,  $R_2 = R_4$  ← مبالغة

$$V_0 = \frac{R_2}{R_1} (V_2 - V_1)$$

$$\therefore \frac{R_2}{R_1} = 5 \quad \therefore R_2 = 5 R_1$$

$$R_1 = 10 \text{ k}\Omega$$


$$\therefore R_2 = 50 \text{ k}\Omega$$

$$R_3 = 10 \text{ k}\Omega$$

$$\therefore R_4 = 50 \text{ k}\Omega$$

نقراض

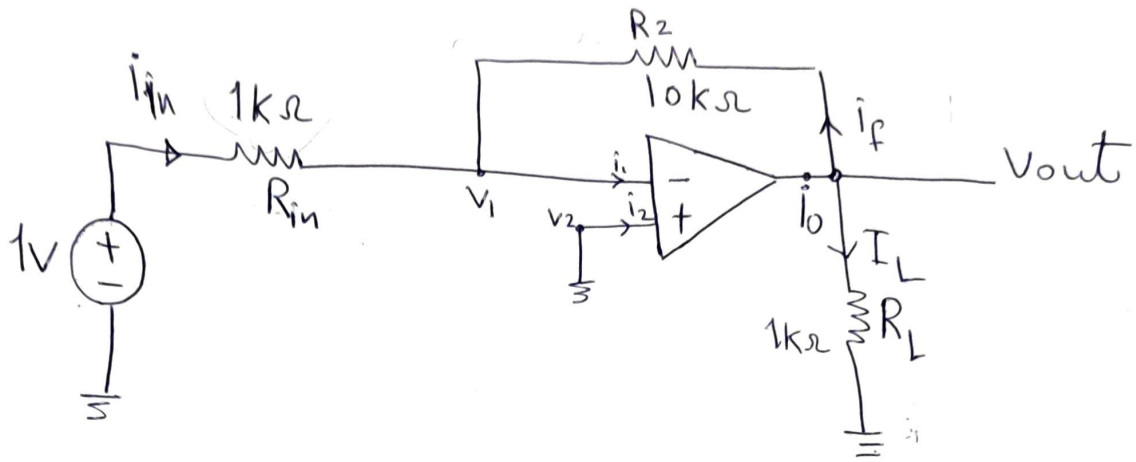في الدائرة مكبر التيارات المثالية في الشكل التالي أوجد :-  
 $V_o$  ،  $i_{in}$  ،  $i_o$  ،  $i_L$  ، الكسب في الجهد والتيار والقدرة ،



= Ideal op - Amp  $\Rightarrow i_1 = i_2 = 0$

$$* i_{in} = \frac{V_s - v_1}{R_{in}} = \frac{1V - 0}{1k\Omega} = 1mA$$

$v_1 = v_2 = 0$  ✓

$$* i_{in} = i_f = 1mA$$

$$* V_{out} = \frac{-R_f}{R_{in}} \cdot V_{in} = \frac{-10k}{1k} (1V) = -10V$$

$$* i_L = \frac{V_o}{R_L} = \frac{-10V}{1k\Omega} = -10mA$$

$$\begin{aligned} i_o &= i_f + i_L \\ &= 1mA + 10mA \\ &= 11mA \end{aligned}$$


$$A_V = \frac{V_o}{V_i} = \frac{-10V}{1V} = -10$$

$$A_{I_{in}} = \frac{i_o}{i_{in}} = \frac{-10mA}{1mA} = -10$$

$$A_P = \frac{P_L}{P_i} = \frac{(-10V)(-10mA)}{(1V)(1mA)} = 100$$

Exo-

find  $A_{CL}$ ,  $V_{out}$

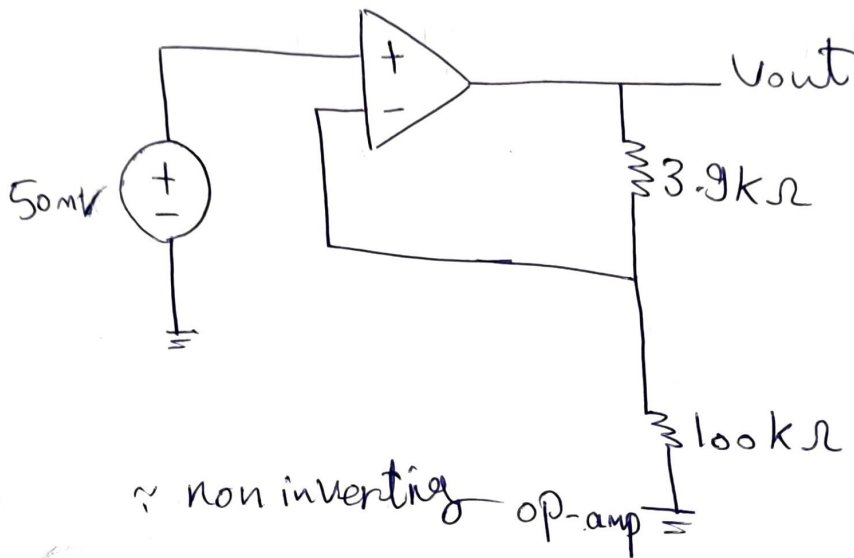

$$A_{CL} = \frac{R_f}{R_i} + 1$$

$$= \frac{3.9k\Omega}{100k\Omega} + 1$$

$$= 1.039$$


$$V_{out} = A_{CL} \cdot V_{in}$$

$$= 1.039 (50mV)$$

$$= 52mV$$

Ex 9-

gain = 26 dB

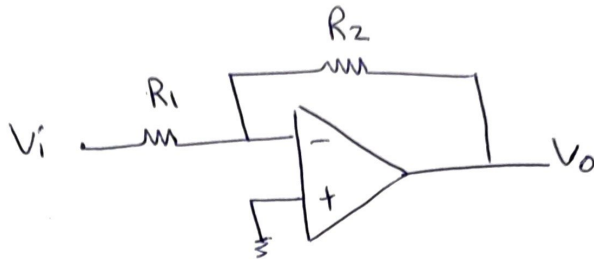

use resistors no larger than  $1M\Omega$  Design the circuit having the largest possible input resistor.

Solution:-

$$A = -\frac{R_2}{R_1}$$

$$26 \text{ dB} = 20 \log \left( -\frac{R_2}{R_1} \right)$$

$$\log \left( -\frac{R_2}{R_1} \right) = \frac{26}{20} = 1.3$$

$$-\frac{R_2}{R_1} = 10^{(1.3)} \Rightarrow \log^{-1}$$

$$-\frac{R_2}{R_1} = 19.95$$

$$-\frac{R_2}{R_1} \approx 20$$

$$\therefore R_2 = 20R_1$$

$$\text{let } R_2 = 1M\Omega$$

$$1M\Omega = 20R_1$$

$$\therefore R_1 = \frac{1M}{20} = \frac{1000k}{20} = 50k\Omega$$

$$\therefore R_2 = 1M\Omega \quad \& \quad R_1 = 50k\Omega$$




Exo -


Design an op amp circuit that will produce the output  $\Rightarrow V_o = -2V_1 + 3V_2 + 5V_3 - V_4 + V_5 - 0.5V_6 + \frac{1}{4}V_7$

b) Draw the output if  $V_1 = 1V$ ,  $V_2 = \sin \omega t (V)$ ,  $V_3 = 0.2V$   
 $V_4 = 2 \sin \omega t (V)$ ,  $V_5 = -2V$   
 $V_6 = -4V$  and  $V_7 = 4V$


Sol :-

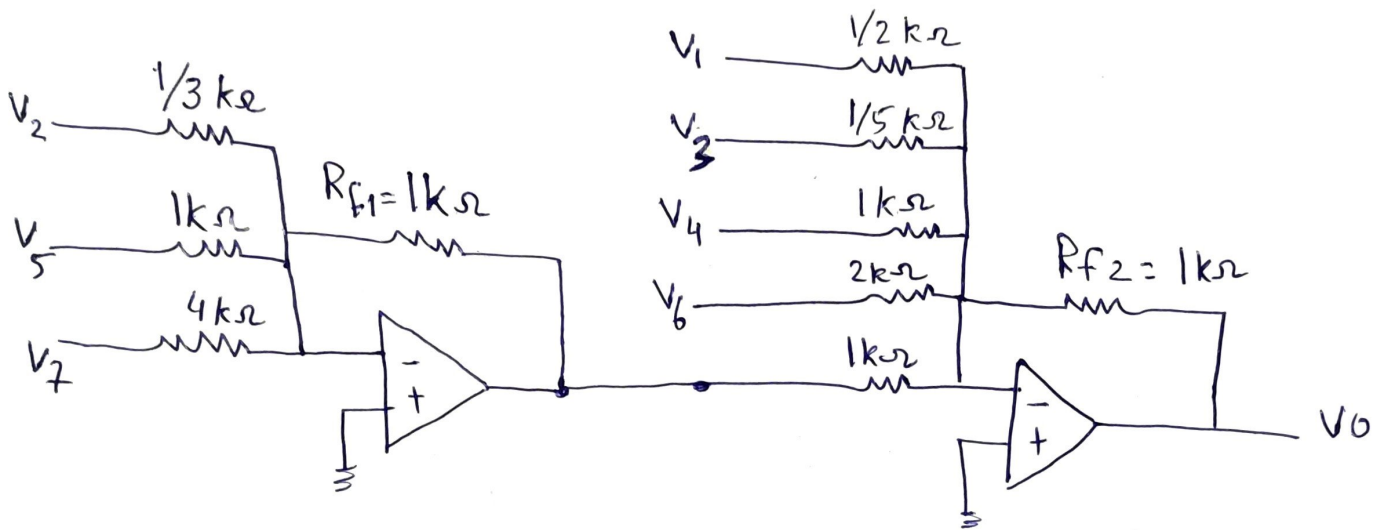
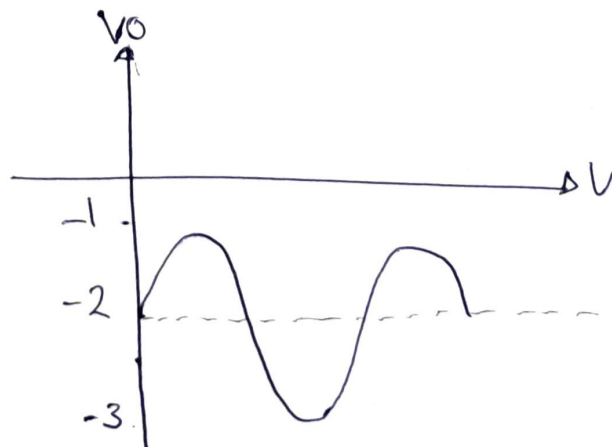
$$\begin{aligned}
 \text{b) } V_o &= -2(1) + 3(\sin \omega t) - 5(0.2) - (2\sin \omega t) + \\
 &\quad (-2) - 0.5(4) + 0.25(4) \\
 &= -2 + 3\sin \omega t - 1 - 2\sin \omega t - 2 + 2 + 1 \\
 \Rightarrow V_o &= \sin \omega t - 2
 \end{aligned}$$




find  $V_o(t)$

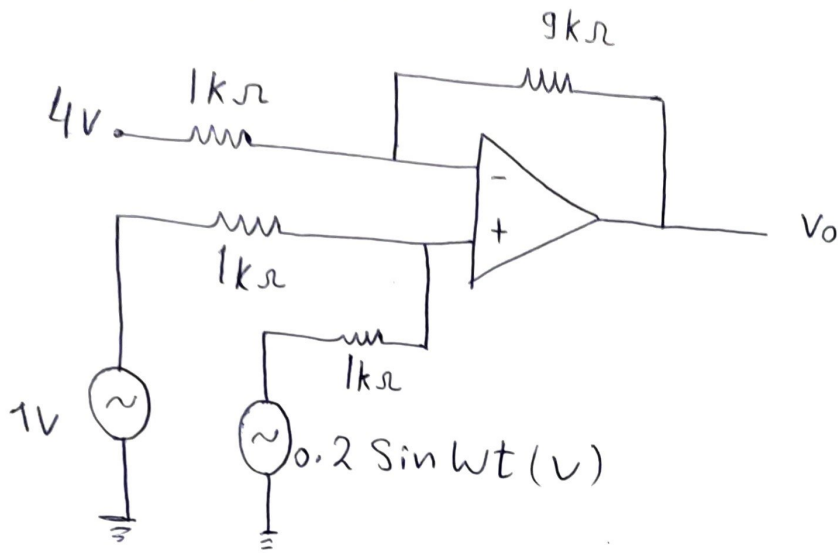

by using superposition


[A] for inverting mode  $\Rightarrow$  4V active
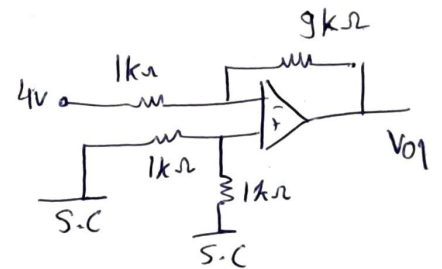
$$V_{o1} = \frac{-9k\Omega}{1k\Omega} (4V) = -36V$$



[B] for non inverting mode  $\Rightarrow$  1V active
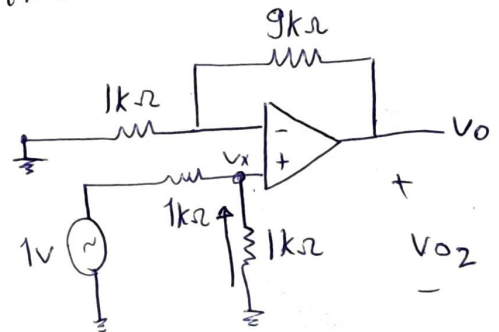
$$\begin{aligned} V_{o2} &= \left(1 + \frac{9k}{1k}\right) (V_x) \\ &= 10 V_x \quad \text{VDR} \\ &= 10 \left(1V \times \frac{1\Omega}{1+1\Omega}\right) V \\ &= 5V \end{aligned}$$




2)  $0.2 \sin \omega t$  active

$$V_{o3} = \left(1 + \frac{9k\Omega}{1k\Omega}\right) \cdot V_y$$

$$V_{o3} = 10 V_y \Rightarrow V_y = V_i \cdot \frac{1}{1+1} = \frac{1}{2} V_i$$
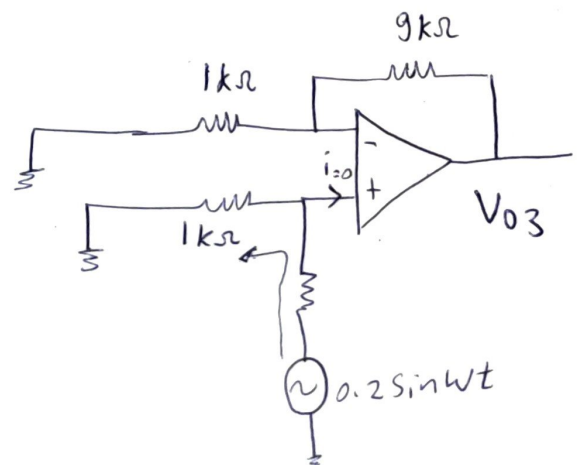
$$V_{o3} = 10 \left(\frac{1}{2} \times 0.2 \sin \omega t\right) = \sin \omega t$$



$$\therefore V_0 = V_{01} + V_{02} + V_{03}$$

$$= -36 + 5 + \sin \omega t$$

$$V_0 = -31 + \sin \omega t$$


---

2/2022

\* Instrumentation Amplifier (IA) operational:-


(IA) is an amp. of low level signal used in process control measurement applications system

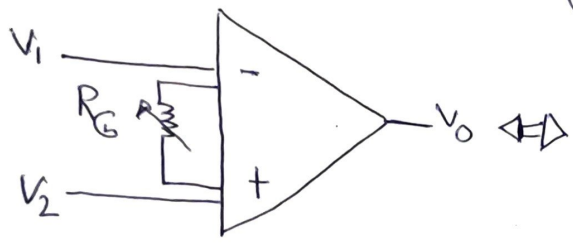يسمى صناعياً بـ كثره وهو موجود قطعه جاهزة ويستطيع ان يعمل باسئام 3 مكبرات



$$A_V = 1 + \frac{2R}{R_G}$$


$$V_0 = A_V (V_2 - V_1)$$

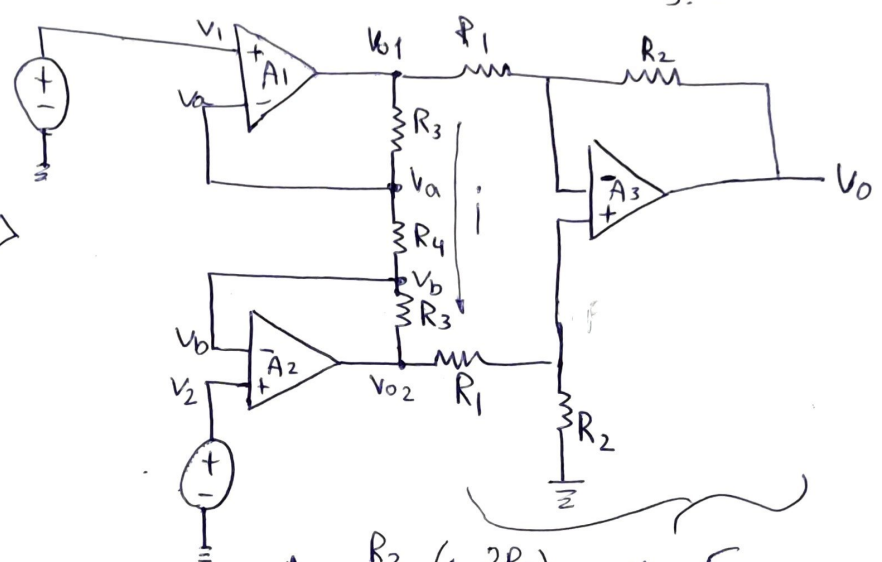

مكبر طارح،  $A_V = \frac{R_2}{R_1} \left(1 + \frac{2R_3}{A_1}\right)$

$$V_0 = \frac{R_2}{R_1} \left(1 + \frac{2R_3}{R_4}\right) (V_2 - V_1)$$

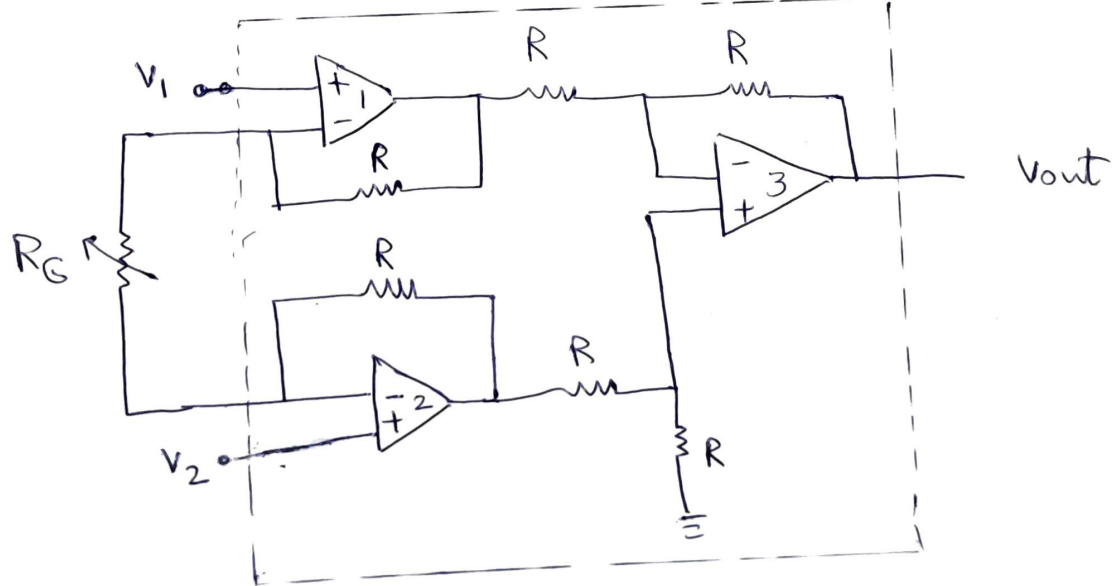$R_G$ : مقاومة متغيره بين طرفي ضبط الكسب مقاومه ضبط الكسب  
external gain setting resistor



\* The Gain Can be varied from 1 to 1000 by an external resistor whose value may vary from 100 to 10kΩ

\* استنتاج قانون (IA)

$$V_0 = \frac{R_2}{R_1} (V_{02} - V_{01})$$

$$\begin{aligned} V_{01} - V_{02} &= i (R_3 + R_4 + R_3) \\ &= i (2R_3 + R_4) \end{aligned}$$

$$\Rightarrow i = \frac{V_a - V_b}{R_4}$$

$$V_a = V_1, \quad V_b = V_2$$

$$\therefore i = \frac{V_1 - V_2}{R_4}$$

$$V_{01} - V_{02} = \left( \frac{V_1 - V_2}{R_4} \right) (2R_3 + R_4)$$

$$V_{01} - V_{02} = \left( \frac{2R_3 + 1}{R_4} \right) (V_1 - V_2)$$

(1-2)  $\Rightarrow V_{02} - V_{01}$   $\Rightarrow$   $V_2 - V_1$

$$-V_{01} + V_{02} = \frac{2R_3}{R_4} + 1 (-V_1 + V_2)$$

$$\therefore V_{02} - V_{01} = \frac{2R_3}{R_4} + 1 (V_2 - V_1)$$

$$\therefore V_0 = \frac{R_2}{R_1} \left( \frac{2R_3}{R_4} + 1 \right) (V_2 - V_1)$$

Exo-1

let  $R = 10k\Omega$ ,  $V_1 = 2.011V$  and  $V_2 = 2.017V$

if  $R_G$  is adjusted to  $500\Omega$  determine:-

- 1) the voltage gain
- 2) the output voltage

Solution:

$$1) A_V = 1 + \frac{2R}{R_G} = 1 + \frac{2 \times 10,000}{500} = 41$$

$$2) V_0 = A_V (V_2 - V_1) \\ = 41 (2.017 - 2.011) = 41(6)mV = 246mV$$


Exo-2


Determine the value of the  $R_G$  required for the IA in fig to produce a gain of 142 when  $R = 25k\Omega$

$$A_V = \left(1 + \frac{2R}{R_G}\right)$$

$$142 = \left(1 + \frac{2 \times 25000}{R_G}\right)$$

$$R_G = 354.6\Omega$$

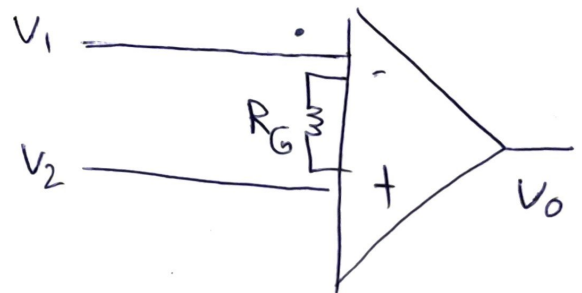

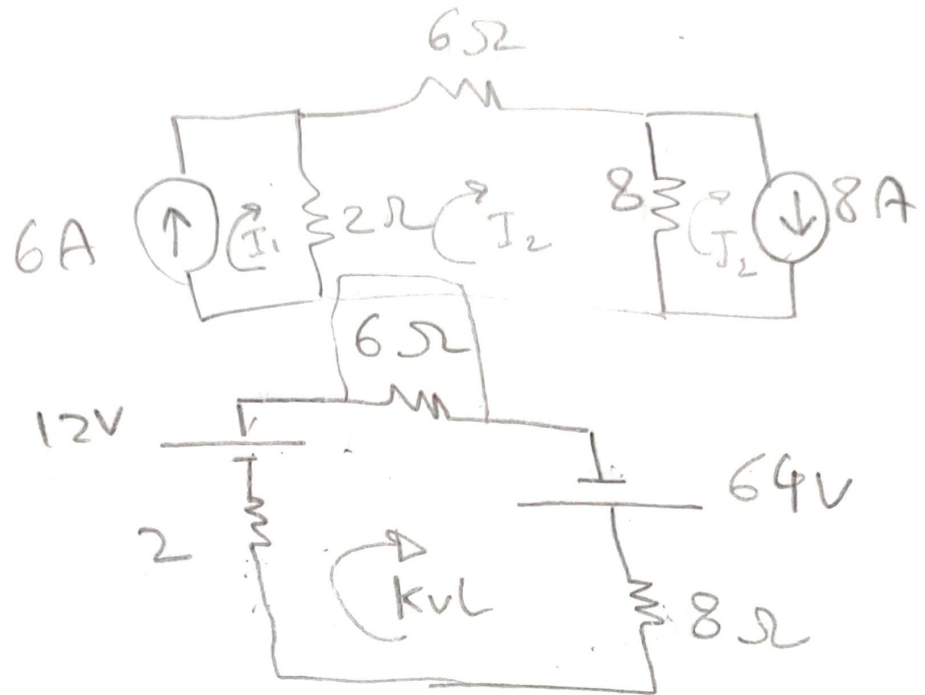

$$-2I + 12 - 6I_2 + 64 - 8I_2 = 0$$

$$-16I = -76$$

$$I = \frac{-76}{-16} = +$$


Roa Aburageba.

aburagebaroa@gmail.com

\* Practical op-amp  
 1) Frequency Response is the relation between freq- and gain.

\* open loop :-

$$f_t = A_{OL}(f_c)$$

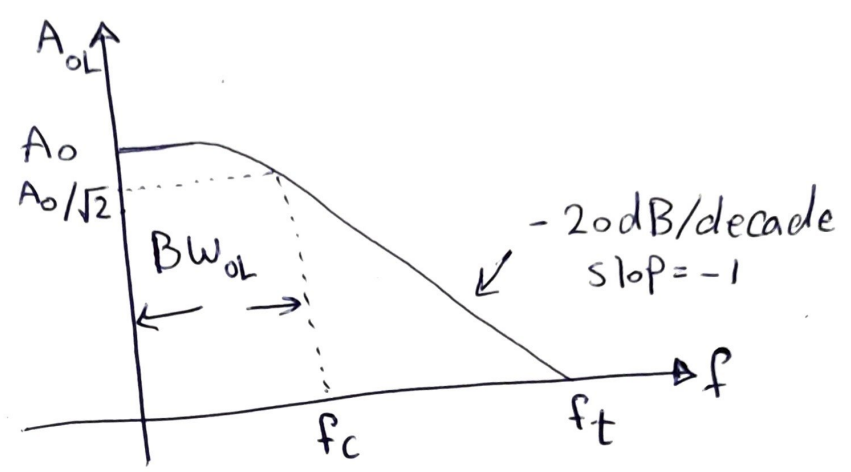


\* close loop :-

$A_{CL}$  = close loop gain

$$f_c(CL) = BW_{CL} = \text{closed loop bandwidth} \cdot \sqrt{2}$$

$$BW_{CL} = \beta f_t = A_{OL} f_c(OL)$$

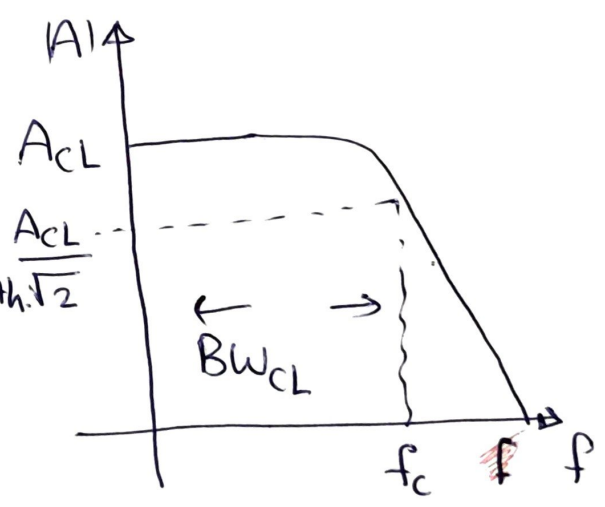

$\beta$  is feed back ratio  $\Rightarrow \beta = \frac{R_g}{R_g + R_f}$



For inverting and non inverting amplifier.



# frequency response

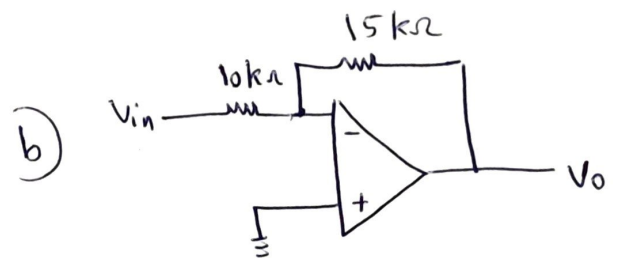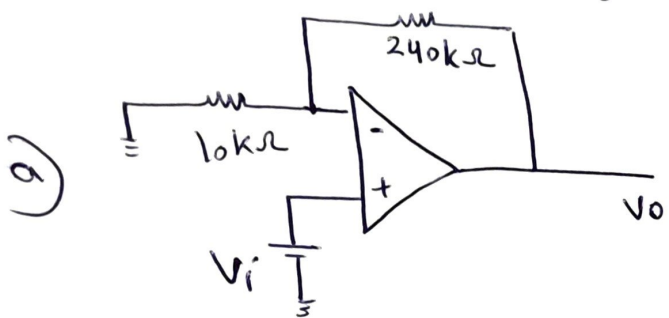Example:-

- Each of the amplifier shown has an open loop gain bandwidth product equal to 1MHz.
- 1) find the closed loop cutoff frequencies.
  - 2) Draw the frequency response of each circuit.



Sol :-

$$f_t = 1\text{MHz}$$

$$f_o(\text{cl}) = \text{BW}_{\text{cl}} = \beta f_t$$


$$\text{a) } \beta = \frac{10\text{k}\Omega}{10\text{k}\Omega + 240\text{k}\Omega} = \frac{1}{25} = 0.04$$

$$\text{BW}_{\text{cl}} = 0.04 \times 1\text{MHz} = 40\text{kHz}$$


$$\text{b) } \beta = \frac{10\text{k}\Omega}{10\text{k}\Omega + 15\text{k}\Omega} = \frac{10}{25} = 0.4$$

$$\text{BW}_{\text{cl}} = 0.4 \times 1\text{MHz} = 400\text{kHz}$$
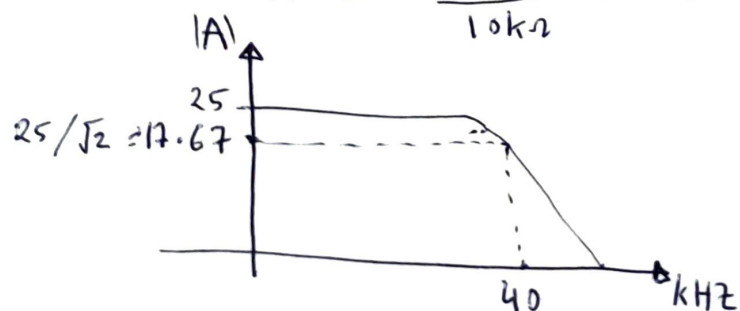
$$\text{2) a) } A = 1 + \frac{240\text{k}\Omega}{10\text{k}\Omega} = 25$$



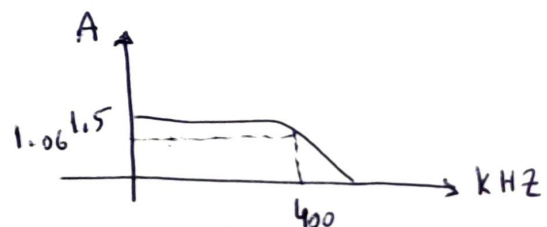
$$\text{b) } A = -\frac{15\text{k}\Omega}{10} = -1.5$$



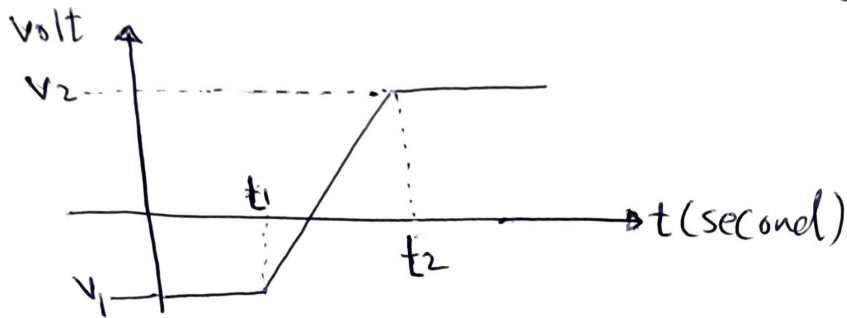
## Slew Rate

The slew rate is the maximum possible rate at which the op amp output voltage can change (V/s)




$$\begin{aligned} \text{rate change of op amp function} &= \frac{v_2 - v_1}{t_2 - t_1} \\ &= \frac{dv}{dt} \text{ V/s} \leq \text{SR} \quad [\text{For no distortion}] \end{aligned}$$
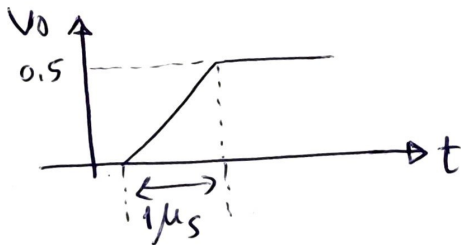
$$\text{SR} \Rightarrow \text{op amp 741} = 0.5 \text{ V}/\mu\text{sec}$$



\* Slew rate

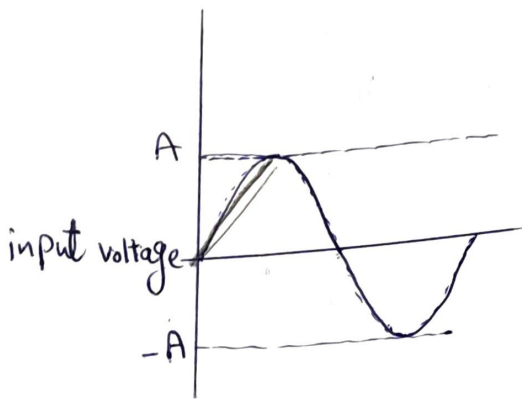


741

$$SR = 0.5 \text{ V}/\mu\text{s}$$

slope of midum. voltage


$$SR = \frac{dV_{out}}{dt}$$

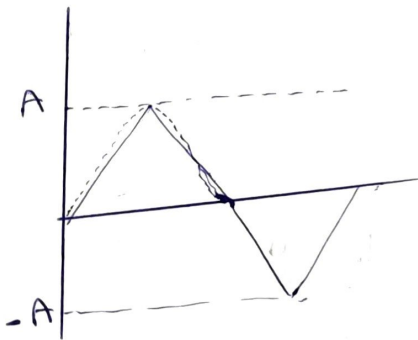

\* frequency response:

at 10V  $\Rightarrow P = \frac{V_{out}^2}{R} = 100\text{W}$

at 7V  $\Rightarrow P = 49\text{W}$

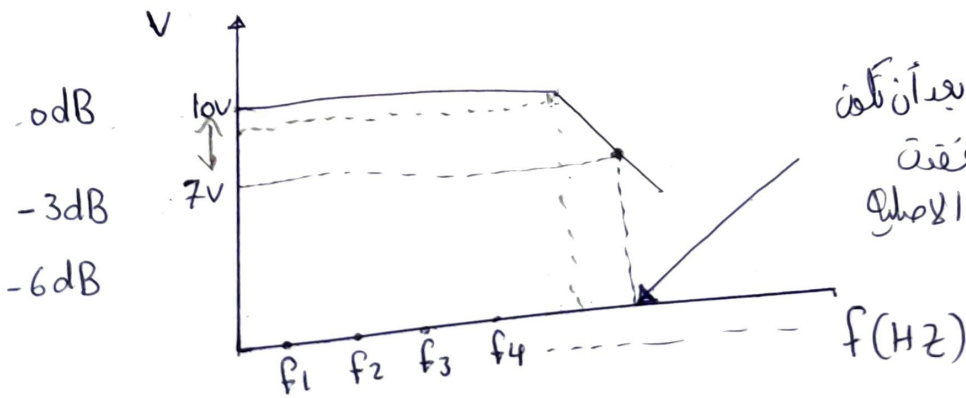

التردد بعد أن تكون  
استارة الخرج فقط  
نصف القدرة الاصلية

تردد منخفض  $\rightarrow$  تردد مرتفع

$$dB = 20 \log\left(\frac{V_o}{V_i}\right)$$


$$6 \text{ dB} = 10 \log\left(\frac{P_{out}}{P_{in}}\right)$$

$V_i$	$V_{out}$	نسبة التغير / التضخم	المقدار dB	علاوة بالقدرة
10V	20V	2	6dB	14 ضعف
10V	14.1V	1.41	3dB	ضعف
10V	10V	1	0dB	القدرة نفسها
10V	7V	0.7	-3dB	فقد نصف القدرة
10V	5V	0.5	-6dB	ربع القدرة

كل 3dB سيكون هناك كسب أو فقد في القدرة بمقدار الضعف  
أو النصف
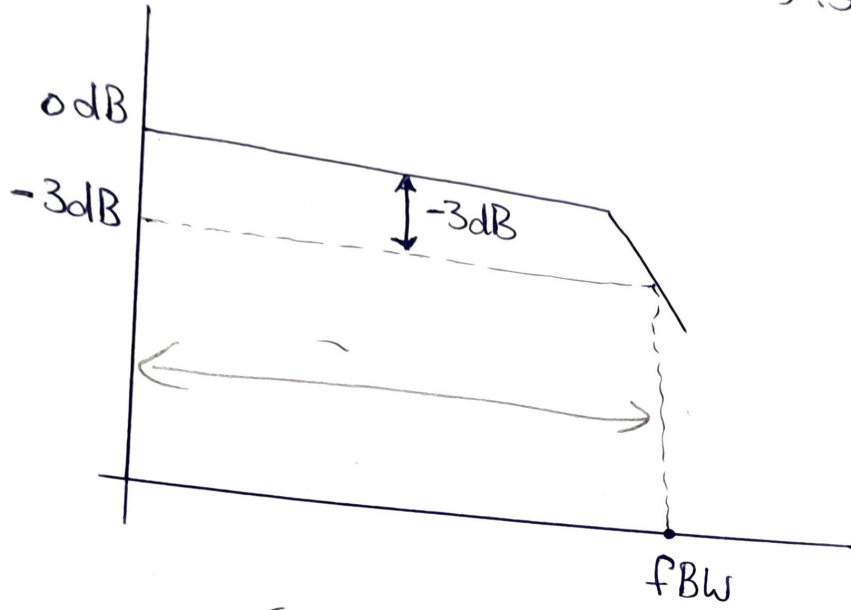
## \* Bandwidth


هو عبارة عن صيغة ترددات أو أكبر تردد يمكن للمكبر أن يعمل عنده بكفاءة




هذا أكبر تردد يمكن أن يتعامل معه المكبر

# \* offset currents and voltages

## 1) offset voltage

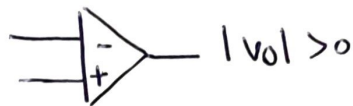

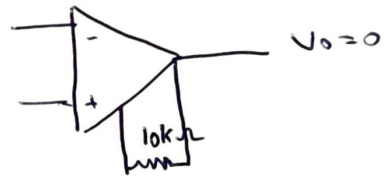
The offset voltage can be reduced by adjusting the ~~10k~~ variable resistance until  $V_o = 0$



## 2) offset current

The bias current  $I_B^+, I_B^- \neq 0$   $V^+ \neq V^- \neq 0$ .

The best value  $R_c = R_f // R_1$

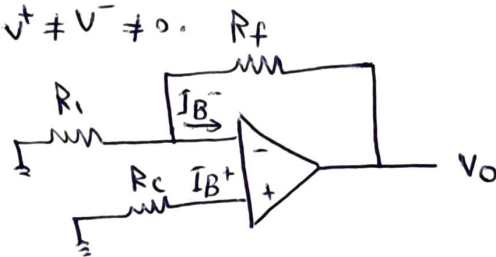

input offset current


$$I_{io} = I_B^+ - I_B^-$$

## Common mode rejection ratio (CMRR)

$A_{OL}$  : open loop gain

$A_{CM}$  : common mode rejection gain

$$CMRR = \left| \frac{A_{OL}}{A_{CM}} \right|$$

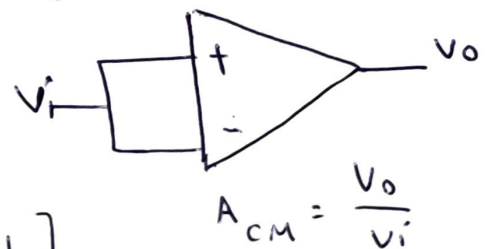

$$CMRR_{dB} = 20 \log \left[ \frac{|A_{OL}|}{|A_{CM}|} \right]$$

The best op amp has very high CMRR

# \* Common-mode Rejection Ratio [CMRR]

$$V_o = A_v (V_2 - V_1) = \left(1 + \frac{2R}{R_G}\right) (V_2 - V_1)$$

Common mode voltage :-

$$V_1 = V_2 = V_c \Rightarrow V_o = 0$$

Common mode Gain  $A_c = 0$

- Differential voltage : if  $V_1 \neq V_2 \Rightarrow V_o = A_v (V_2 - V_1)$

- Differential Gain of the Amplifier :  $A_d = A_v$

- Common mode Rejection Ratio (CMRR) :

$$CMRR = \frac{A_d}{A_c} \rightarrow \text{differential gain}$$


CMRR  $\rightarrow$  لا تفرق بين  $A_c \rightarrow$  لو هادي صفر

تكون  $\infty$   
يعني مش كويس

عادة CMRR تكون اقل من 100 ومن بعض الاصلان تكون 10000 في حال

high quality biopotential amp.
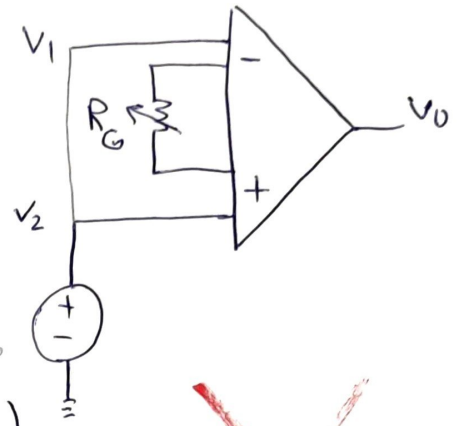
$$CMRR (dB) = 20 \log_{10} \frac{A_d}{A_c}$$




# \* Integrator op-Amp

Important op Amp Circuits that use energy-storage elements include integrator and differentiators. These op Amp circuits often involve resistors and capacitors; inductors (coils) tend to be more bulky and expensive.

(ti) التكاملية
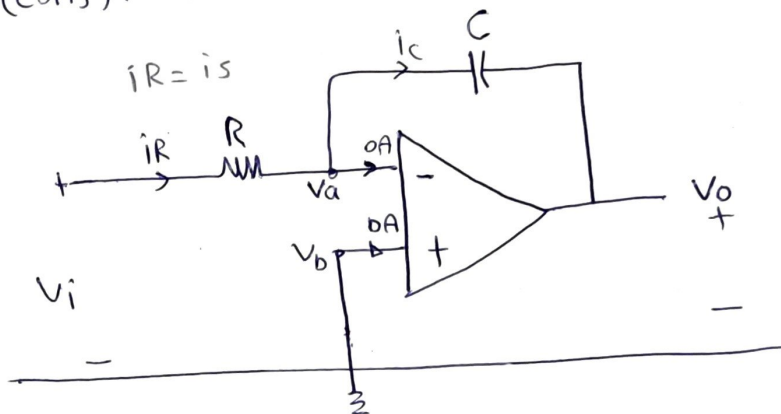
$$V_o(t) = -\left(\frac{1}{RC}\right) \int_0^t v_i dt$$



→ التكاملية

$$i_R = i_c$$

Ideal op-Amp

$$\frac{v_i - v_a}{R} = C \frac{dv_c}{dt}$$

$$= C \frac{d(v_a - v_o)}{dt}$$

$$v_a = v_b = 0$$

$$\therefore \frac{v_i}{R} = -C \frac{dv_o}{dt}$$

$$dv_o = -\frac{1}{RC} v_i dt$$

تكاليف الطرفين

$$\int_0^t dv_o = -\frac{1}{RC} \int_0^t v_i dt$$

$$v_o(t) \Big|_0^t = -\frac{1}{RC} \int_0^t v_i dt$$


$$v_o(t) - v_o(0) = -\frac{1}{RC} \int_0^t v_i dt$$



Ex:-1) The integrator has  $R = 100 \text{ k}\Omega$ ,  $C = 20 \mu\text{f}$ . Determine the output voltage when a dc voltage of  $10 \text{ mV}$  is applied at  $t = 0$ . Assume that the op amp is initially nulled.

Solution :-

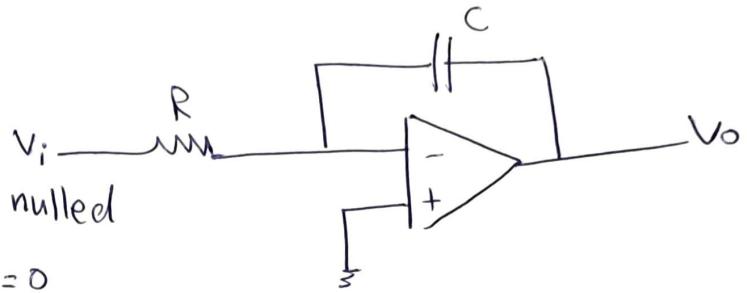$\therefore$  The op amp initially nulled  
 $\therefore V_0(0) = 0$




$$V_0(t) - V_0(0) = -\frac{1}{RC} \int_0^t V_i dt$$

$$V_0(t) = \frac{-1}{100 \times 10^3 \times 20 \times 10^{-6}} \int_0^t 10 \times 10^{-3} dt$$

$$= -5t \text{ mV}$$

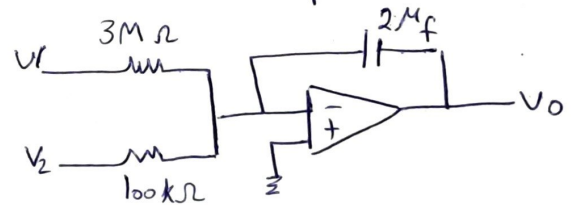2) if  $V_1 = 10 \cos 2t \text{ mV}$  and  $V_2 = 0.5t \text{ mV}$ , find  $V_0$  in the op Amp circuit. Assume that the voltage across the capacitor is initially zero.



$$V_0(t) = -\frac{1}{R_1 C} \int_0^t V_1 dt - \frac{1}{R_2 C} \int_0^t V_2 dt$$

$$V_0(t) = -\frac{1}{3 \times 10^6 \times 2 \times 10^{-6}} \int_0^t 10 \cos 2t dt - \frac{1}{100 \times 10^3 \times 2 \times 10^{-6}} \int_0^t 0.5t dt$$

$$= -\frac{1}{6} \times \frac{10}{2} \sin(2t) \Big|_0^t - \frac{1}{0.2} \times \frac{0.5}{2} t^2 \Big|_0^t$$

$$= -\frac{5}{6} \sin 2t - \frac{5}{4} t^2 \text{ mV}$$

Solution z

$$V_c = V_a - V_o$$

$$\hat{i}_1 + \hat{i}_2 = \hat{i}_c$$

$$\frac{V_1 - V_a}{R_1} + \frac{V_2 - V_a}{R_2} = C \frac{d(V_1 - V_o)}{dt}$$

$$dV_o = -\frac{V_1}{R_1 C} dt - \frac{V_2}{R_2 C} dt$$

$$\int_0^t dV_o = -\frac{1}{R_1 C} \int_0^t V_1 dt - \frac{1}{R_2 C} \int_0^t V_2 dt$$

$$= V_o \Big|_0^t = -\frac{1}{R_1 C} \int_0^t V_1 dt - \frac{1}{R_2 C} \int_0^t V_2 dt$$

$$V_o(t) - V_o(0) = -\frac{1}{R_1 C} \int_0^t V_1 dt - \frac{1}{R_2 C} \int_0^t V_2 dt$$

# Integrator :-

Ex :-

a) Draw the output of ideal integrator show

When :- i-  $V_i = 5\text{mV (dc)}$

ii-  $V_i = 0.5 \sin 100t \text{ (v)}$

iii-  $V_i = 0.5 \sin 1000t \text{ (v)}$

b) Find the best value of  $R_c$ .

Sol :-

$$i) V_o = \frac{1}{RC} \int_0^t v_i dt$$

$$V_o = \frac{1}{1000 \times 0.01 \mu} \int_0^t 5 \times 10^{-3} dt$$

$$V_o = -1000 (5 \times 10^{-3}) t = -5t \text{ (v)}$$




$$ii) V_o = -1000 \int_0^t 0.5 \sin 100t dt$$

$$= -1000 \left[ \frac{-0.5 \cos 100t}{100} \right] = 5 \cos 100t.$$

$$\omega = 2\pi f = 100$$

$$\frac{2\pi}{T} = 100 = 2\pi f$$



$$T = \frac{2\pi}{100}$$

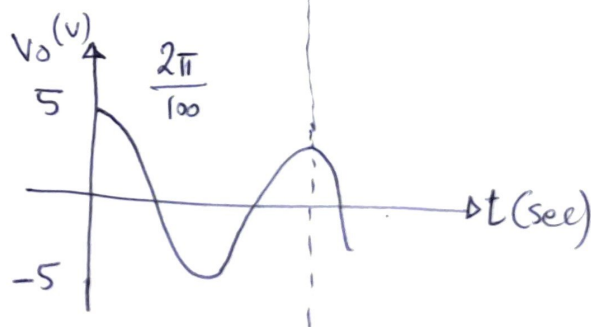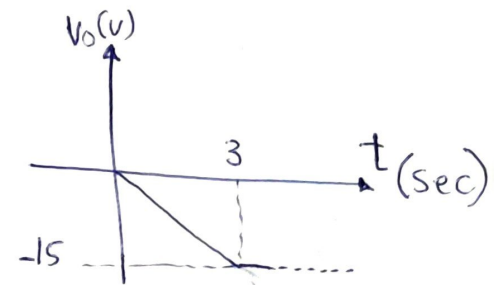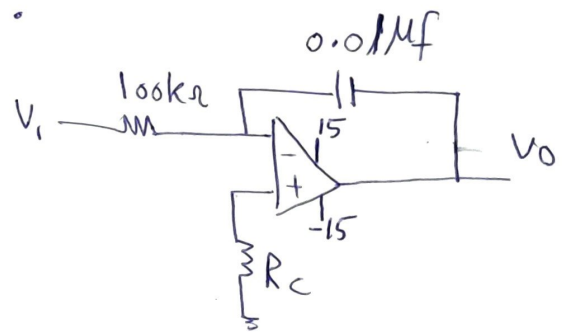


$$V_o = -1000 \int_0^t 0.5 \sin 1000t \, dt$$

$$= -1000 \left[ \frac{-0.5 \cos 1000t}{1000} \right] = 0.5 \cos 1000t \text{ (v)}$$


$$T = \frac{2\pi}{1000}$$

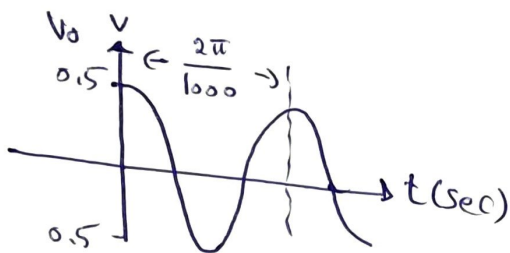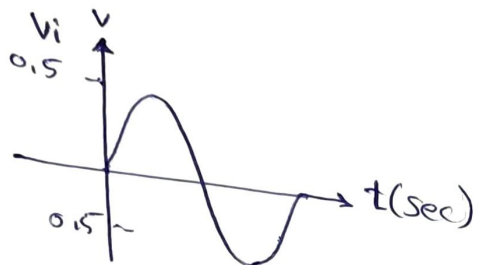

b)  $R_c = R_1 = 100 \text{ k}\Omega$

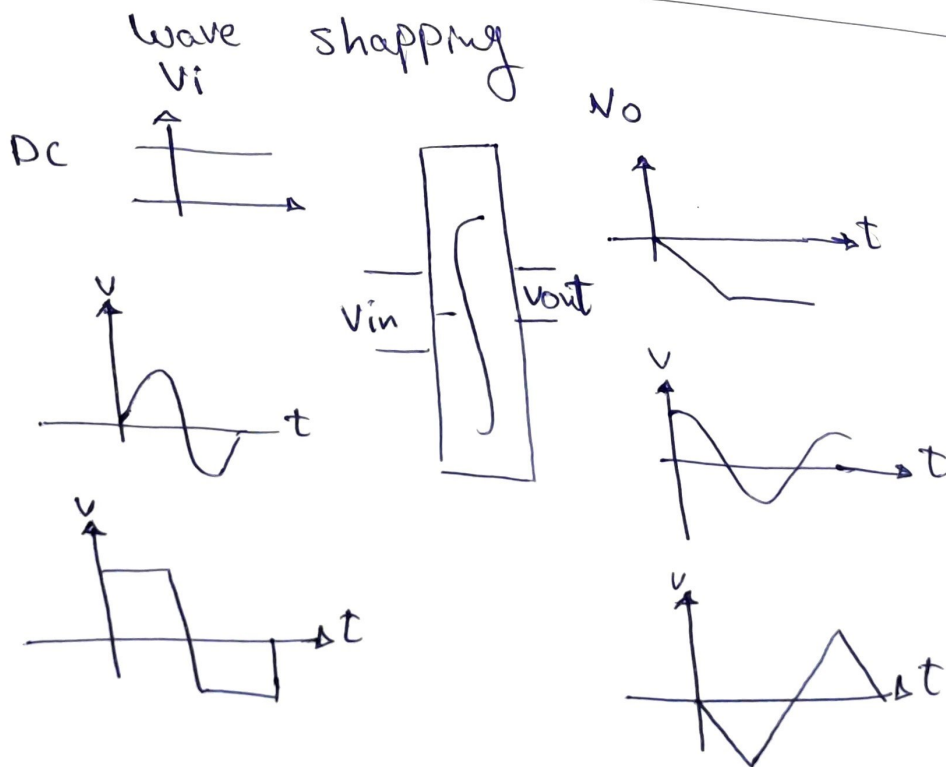

# Practical Integrator

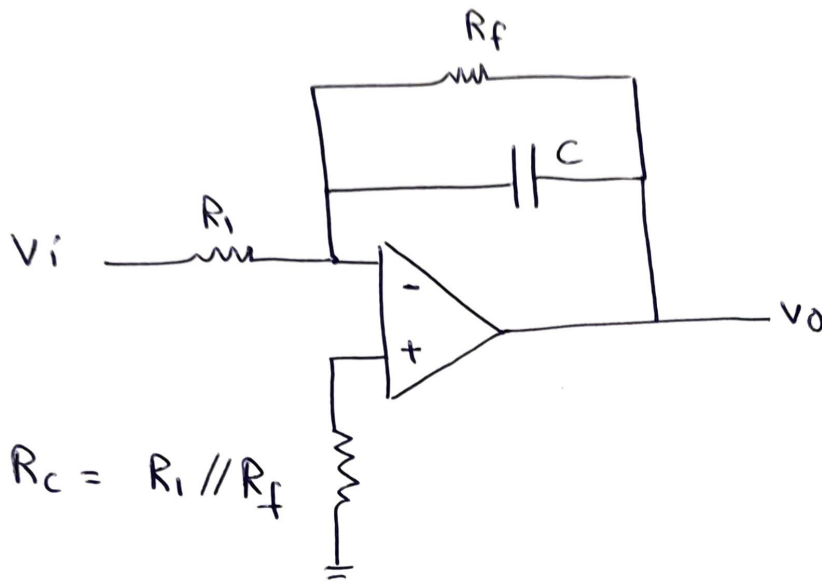


- 1)  $-\frac{R_f}{R_1} v_i$  (dc) at low frequency  $f \leq f_c$
- 2)  $-\frac{1}{R_1 C} \int v_i dt$  (ac)  $f \geq 10f_c$

$$X_C = \frac{1}{2\pi f C} \ll R_f$$


$$f \gg \frac{1}{2\pi R_f C}, \text{ let } f_c = \frac{1}{2\pi R_f C}$$

$$f \gg f_c \Rightarrow f \gg 10f_c$$

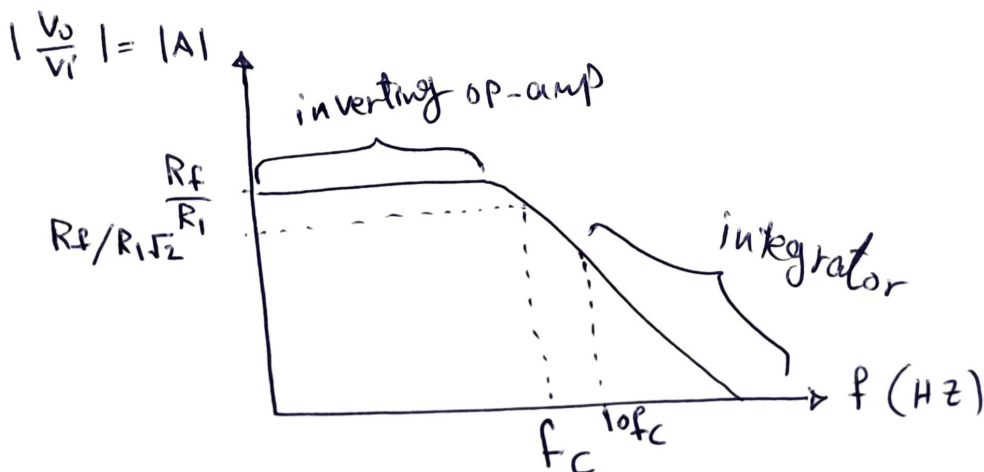

$$\text{gain} \propto \frac{1}{f}$$

$$\text{gain} = \left| \frac{V_o}{V_i} \right| = \frac{1}{\omega R_1 C}$$

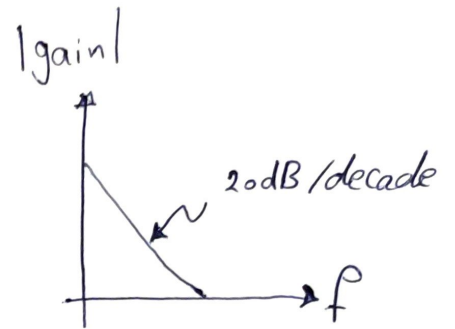

$$V_i = A \sin \omega t \Rightarrow V_o = \frac{-1}{R_1 C} \int A \sin \omega t \cdot dt$$

$$= \frac{-1}{R_1 C} \left[ \frac{-A \cos \omega t}{\omega} \right]$$

$$\left| \text{gain} \right| = \left| \frac{V_o}{V_i} \right| = \frac{-\frac{1}{R_1 C} \left[ \frac{-A \cos \omega t}{\omega} \right]}{A \sin \omega t}$$

$$\therefore |gain| = \frac{1}{R_1 C \omega}$$

Exo

a) Design a practical integrator that

1. Integrates signals with frequencies down to 100 Hz, and
2. Produces a peak output of 0.1V when the input is a 10V peak sine wave having frequency 10 kHz.

b) Find the output when the input is 50mV dc.

c) draw the frequency response of the designed circuit.

Sol:-

$$f \gg 10 f_c$$

$$100 \text{ Hz} = 10 f_c$$

$$\Rightarrow f_c = \frac{100 \text{ Hz}}{10} = 10 \text{ Hz} = \frac{1}{2\pi R_f C}$$

$$\text{let } C = 10 \text{ nF}$$


$$\Rightarrow R_f = 1.59 \text{ M}\Omega$$

$$V_{ip} = 10 \text{ V}, f = 10 \text{ kHz} \Rightarrow V_{op} = 0.1 \text{ V}$$

$$\text{Gain} = \frac{1}{\omega R_f C} = \left| \frac{V_o}{V_i} \right| = \frac{0.1 \text{ V}}{10 \text{ V}}$$


$$R_i = \frac{10}{2\pi \times 10^4 \times 10 \times 10^{-9} \times 0.1}$$

$$R_i = 159 \text{ k}\Omega$$

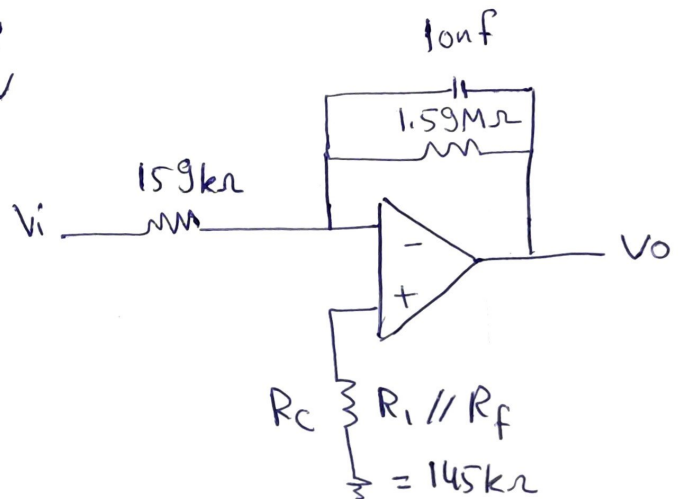


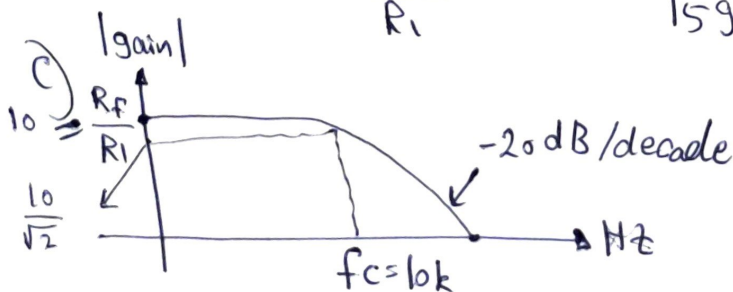b)  $V_i = 50 \text{ mV (dc)}$

$$V_o = -\frac{R_f}{R_i} V_i = -\frac{1.59 \text{ M}\Omega}{159 \text{ k}\Omega} (50 \text{ mV}) = -0.5 \text{ V}$$



# Ideal differentiator :-

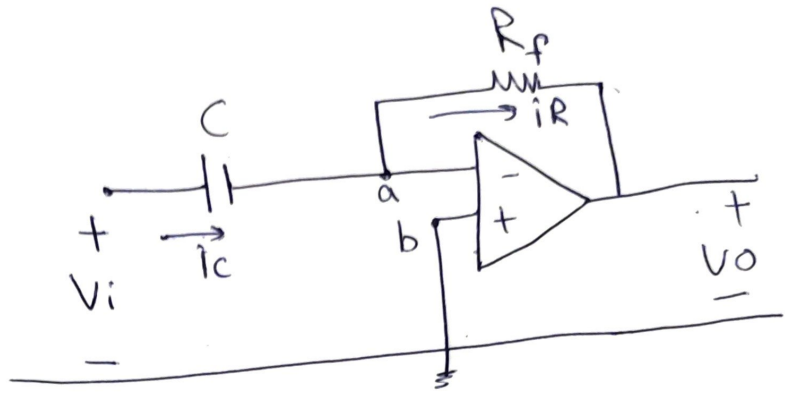

$$V_c = V_i - V_a$$

$$i_c = i_R$$

$$C \frac{dV_c}{dt} = \frac{V_a - V_o}{R} = V_c = V_i - V_a$$

$$\therefore C \frac{d(V_i - V_a)}{dt} = \frac{V_a - V_o}{R}$$


$V_a = V_b = 0$  for ideal op-amp

$$C \frac{dV_i}{dt} = -\frac{V_o}{R}$$

$$-\frac{V_o}{R} = C \frac{dV_i}{dt} \quad (\text{نضرب الطرفين في } -R)$$

$$V_o = -RC \frac{dV_i}{dt}$$

$$\text{gain} = \left| \frac{V_o}{V_i} \right| = \omega C R_f = 2\pi f C R_f$$

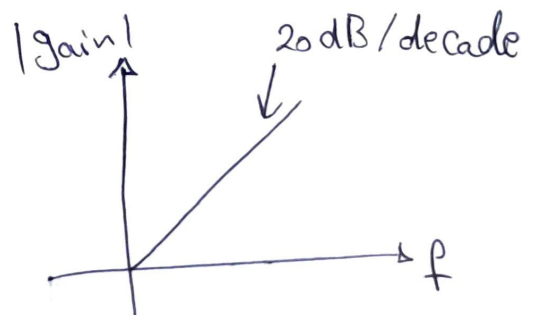



differentiator:-


Example:-

for the circuit shown draw the output where,

1)  $v_i = 0.2 \sin 10^2 t$  [v]

2)  $v_i = 0.2 \sin 10^3 t$  [v]

find the value of  $R_c$ .

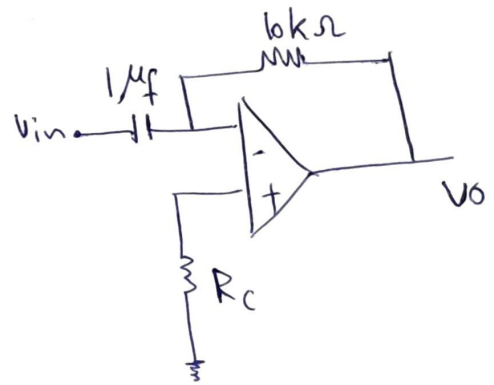


Sol:-

$$V_o = -R_f C \frac{dV_i}{dt}$$

1) 
$$V_o = -10 \times 10^3 \times 10^{-6} \left( \frac{d(0.2 \sin 10^2 t)}{dt} \right)$$

$$V_o = -10 \times 10^3 \times 10^{-6} \times 10^2 \times 0.2 \cos 10^2 t \text{ (v)}$$

$$= -0.2 \cos 10^2 t \text{ (v)}$$

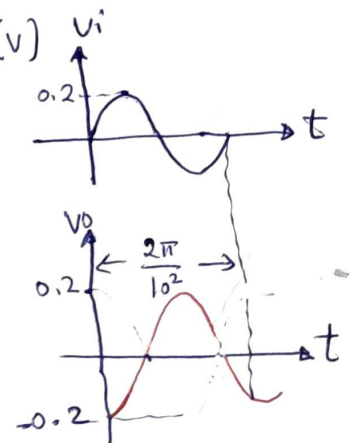


$$\omega = 2\pi f = 10^2$$

$$f = \frac{10^2}{2\pi}$$

$$T = \frac{1}{f} = \frac{2\pi}{10^2}$$

2) 
$$V_o = -10 \times 10^3 \times 10^{-6} \times 10^3 \times 0.2 \cos 10^3 t \text{ [v]}$$

$$= -2 \cos 10^3 t \text{ [v]}$$

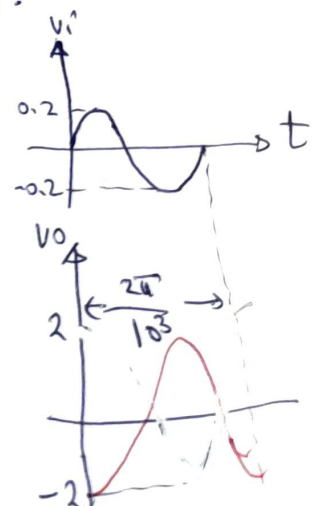

$$R_c = R_f = 10k\Omega$$


#

Exo:-


The differentiator in fig (1) has  $R = 100\text{k}\Omega$  and  $C = 0.1\mu\text{f}$   
Given that  $v_i = 3t$  V, determine the output  $v_o$ .

$$v_o = -Rc \frac{dv_i}{dt}$$
$$= -100 \times 10^3 \times 0.1 \times 10^{-6} \frac{d}{dt} 3t$$
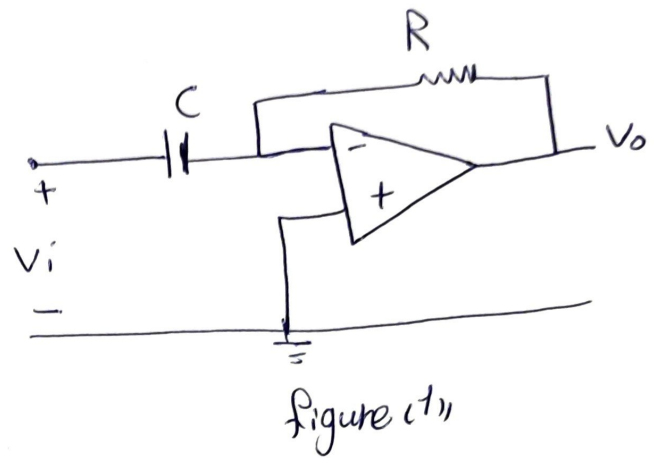
$$= -0.01 \times 3 = -0.03 \text{ V} = -30 \text{ mV}$$



find  $V_o(t)$

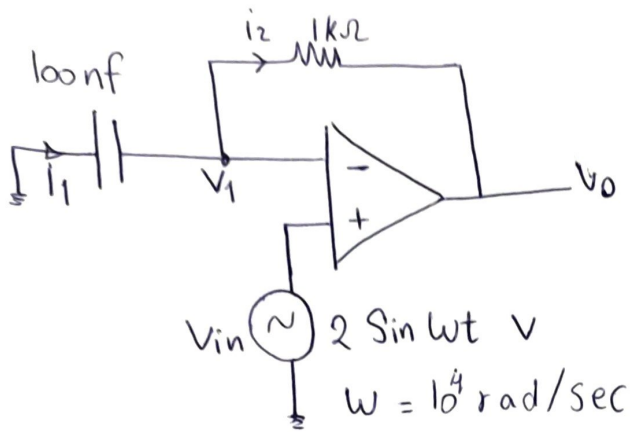

Solution:-  $i_1 = i_2$

$$V_c = 0 - V_1$$

$$C \cdot \frac{dV_c}{dt} = \frac{V_1 - V_o}{R}$$

$$100 \times 10^{-9} \left( \frac{d(0 - V_1)}{dt} \right) = \frac{2 \sin wt - V_o}{1000 \Omega}$$

$$100 \times 10^{-9} \cdot \frac{d(-2 \sin wt)}{dt} = \frac{2 \sin wt - V_o}{1000}$$

$$100 \times 10^{-9} (-2w \cos wt) = \frac{2 \sin wt - V_o}{1000}$$

$$\cancel{1000} \times \cancel{100} \times \cancel{10^{-9}} (-2 \times 10^4 \cos wt) = 2 \sin wt - V_o$$



$$-2 \cos wt = 2 \sin wt - V_o$$

$$V_o = 2 \sin wt + 2 \cos wt$$

$$= 2 [\sin wt + \cos wt]$$

#


# \* practical differentiator :-

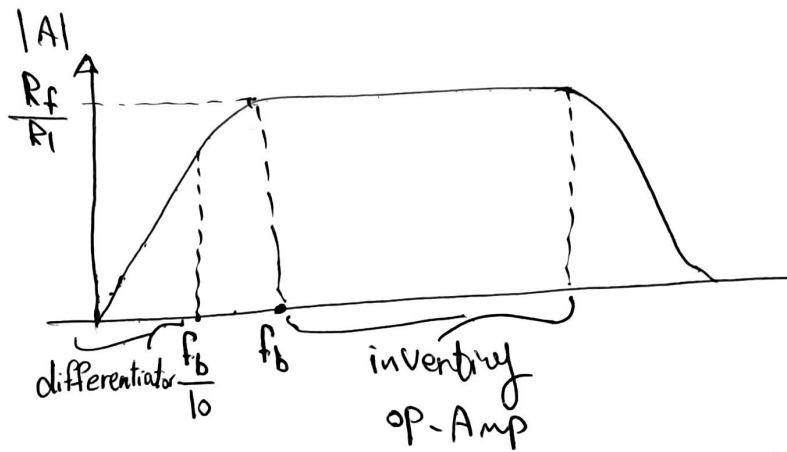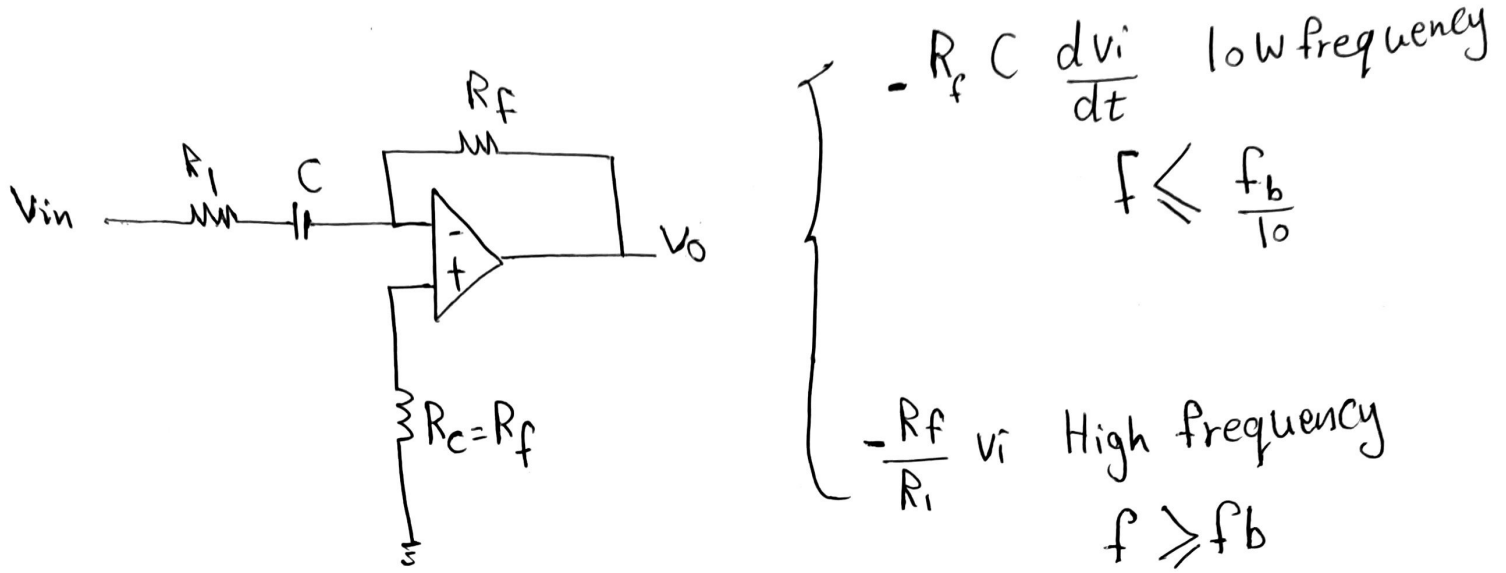

$$\frac{1}{2\pi f C} = X_C > R_1$$

$$f \ll \frac{1}{2\pi R_1 C} \quad \text{let } f_b = \frac{1}{2\pi R_1 C}$$
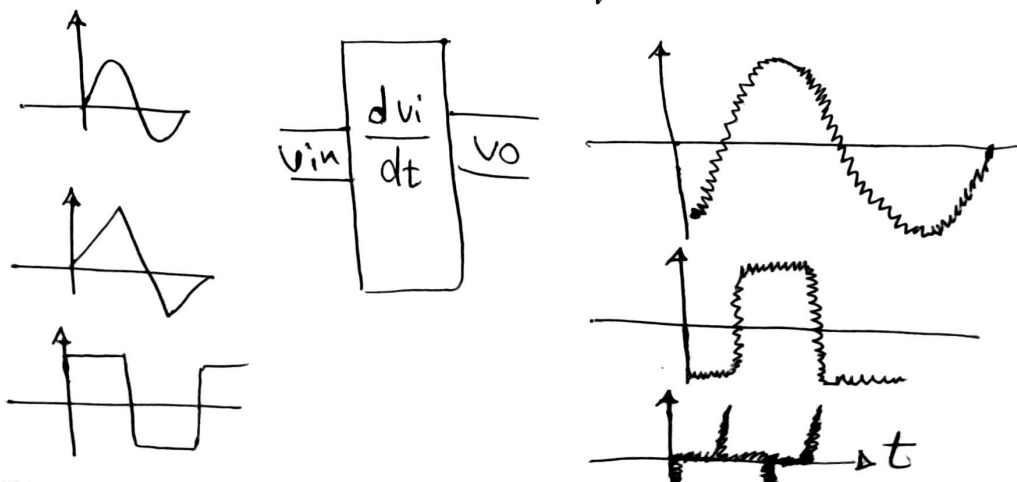
$$f \ll f_b \quad , \quad f \ll \frac{f_b}{10}$$



Example:-

a) Design a practical differentiator that will differentiate signals with frequencies up to 200 Hz. The gain at 10 Hz for sine wave should be 0.1.

b) Draw the frequency response of the designed differentiator if the op-amp used has a unity gain frequency of 1 MHz.

c) Draw  $V_o$  where: i)  $V_i = 0.1 \sin 2\pi \times 10^4 t$  (V)

ii)  $V_i = 0.2 \sin 2\pi \times 10^2 t$  (V)

Sol:-


$$\frac{f_b}{f_0} = 200 \Rightarrow f_b = 2000 \text{ Hz} = 2 \text{ kHz}$$

at 10 Hz  $A = 0.1$  Sin Wave

$$f_b = \frac{1}{2\pi R_1 C} = 2000$$

let  $C = 0.1 \mu\text{F}$

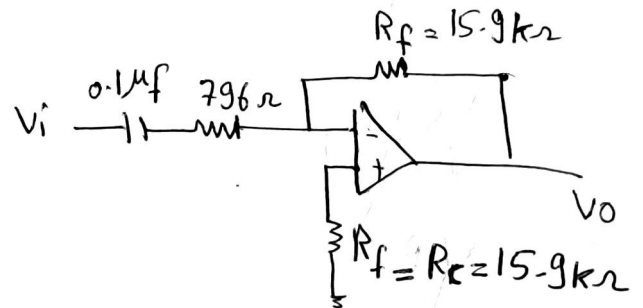
$$R_1 = \frac{1}{2\pi \times 0.1 \times 10^{-6} \times 2000} = 796 \Omega$$



$$\text{gain} = \omega R_f C \Rightarrow \text{at } 10 \text{ Hz} = 0.1$$

$$0.1 = 2\pi \times 10 \times R_f \times 0.1 \times 10^{-6}$$
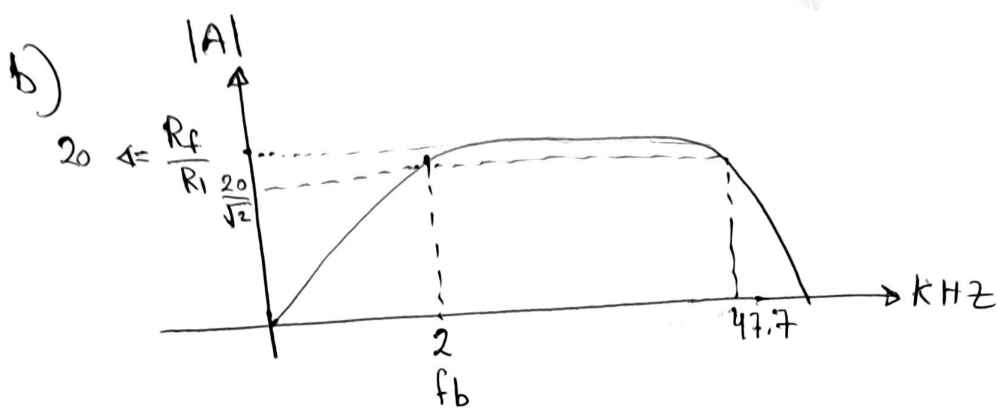
$$R_f = \frac{0.1}{2\pi \times 10 \times 0.1 \times 10^{-6}} = 15.9 \text{ k}\Omega$$



$$\frac{R_f}{R_i} = \frac{15.9 \text{ k}\Omega}{796 \Omega} \approx 20$$

$$B W_{CL} = \beta f_t = \frac{R_i}{R_i + R_f} (f_t) = \frac{796}{796 + 15.9} (1 \times 10^6)$$



$$= 47.7 \text{ kHz}$$

c) i)  $f = 10^4 > f_b$  = inverting amplifier

$$V_o = \frac{-R_f}{R_i} (v_i)$$

$$= -20 (0.1 \sin 2\pi 10^4 t \text{ (v)})$$

$$= -2 \sin 2\pi 10^4 t \text{ [V]}$$

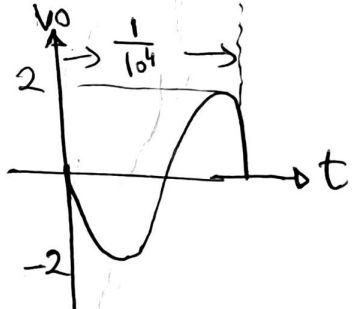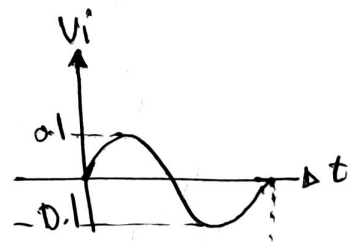

ii)  $v_i = 0.2 \sin 2\pi \times 10^2 t \text{ [V]}$


$f = 10^2 = 100 < \frac{f_b}{10} \Rightarrow$  differentiator

$$V_o = -R_f C \frac{dv_{in}}{dt}$$

$$= -15.9 \text{ k} \times 0.1 \mu \times [0.2 \times 2\pi \times 100 \cos 2\pi 10^2 t \text{ } v_i]$$

$$= -0.2 \cos 2\pi 10^2 t \text{ [V]}$$

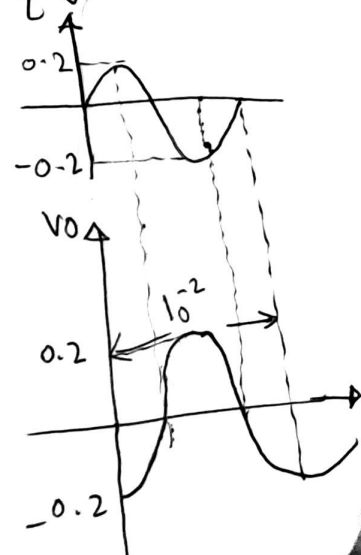
$$T = \frac{1}{f} = \frac{1}{10^2} = 10^{-2}$$



# Passive and Active filters:


## Low pass filter :-

يسمح بمرور الترددات الصغيرة

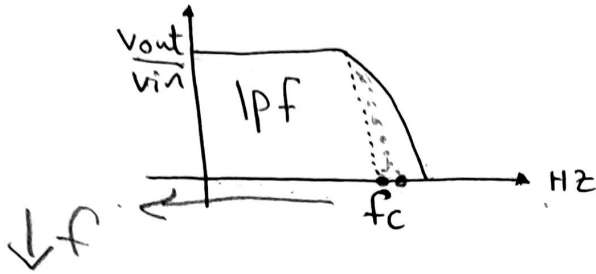

$f_c \Rightarrow$  Critical frequency  
التردد الحرج

1)

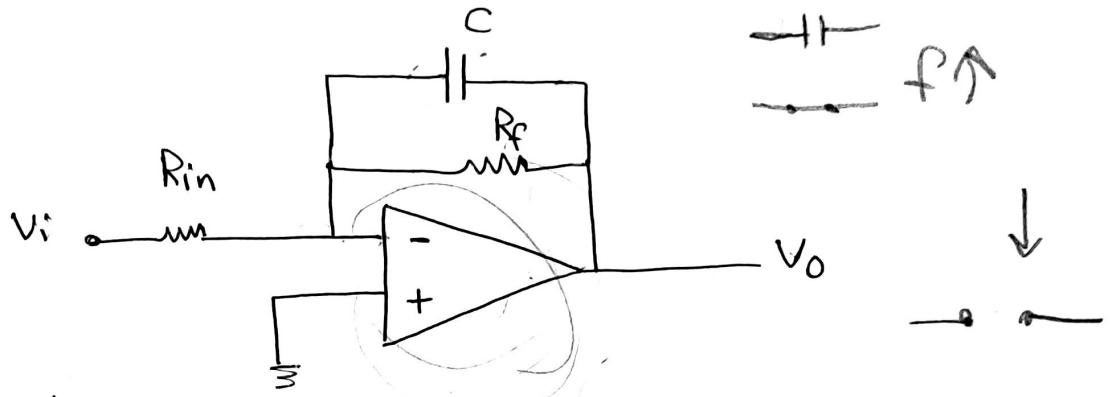


$$f_c = \frac{1}{2\pi R_f C}$$

$$X_c = \frac{1}{2\pi f_c C}$$

$$\text{Gain} = \frac{-R_f \parallel X_c}{R_{in}}$$


2)

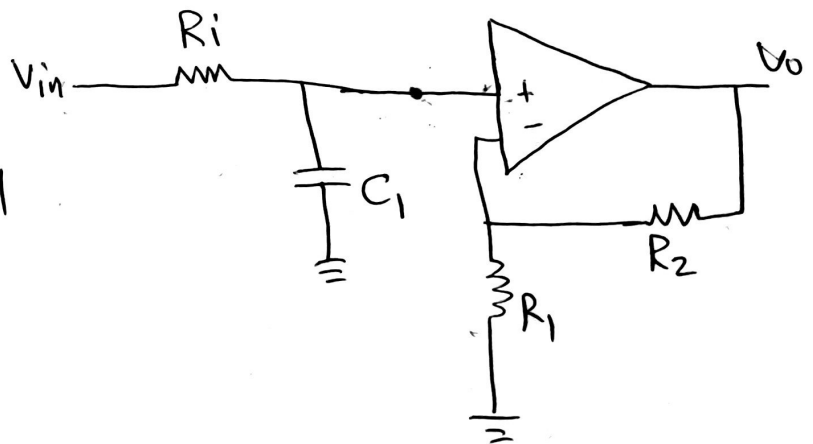

$$A_v = \frac{R_2}{R_1} + 1$$


$$f_c = \frac{1}{2\pi R_{in} C_1}$$

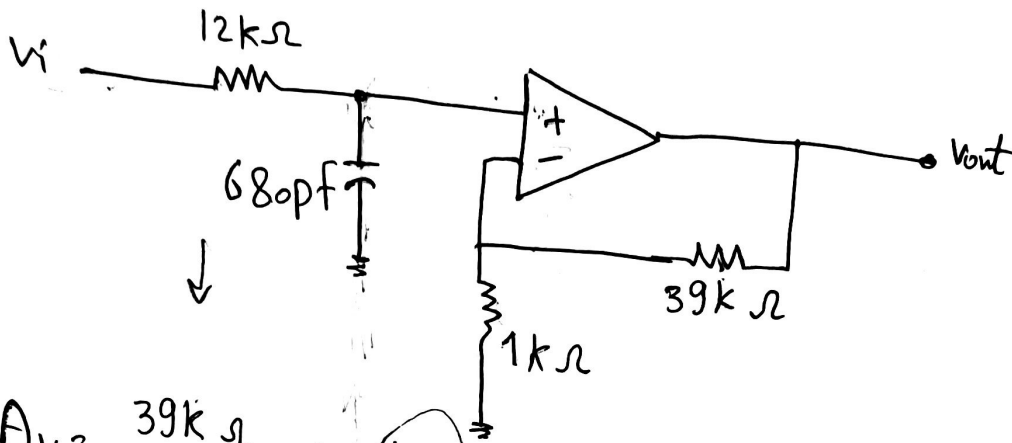اصف كسب الجهد في الشكل  
 اصف تردد القطع وارسم الاستجابة الترددية




$$A_v = \frac{39k\Omega}{1k\Omega} + 1 = 40$$
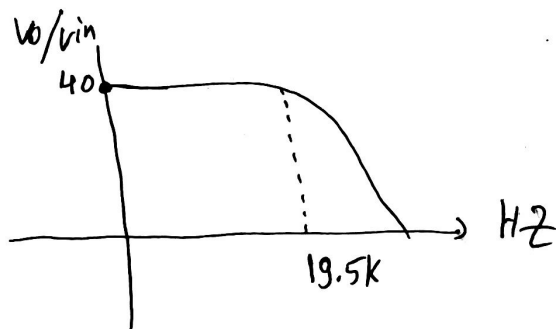
$$f_c = \frac{1}{2\pi \cdot (12k\Omega) \cdot (680pF)} = 19.5 kHz$$






## 2) High pass filter (HPF)

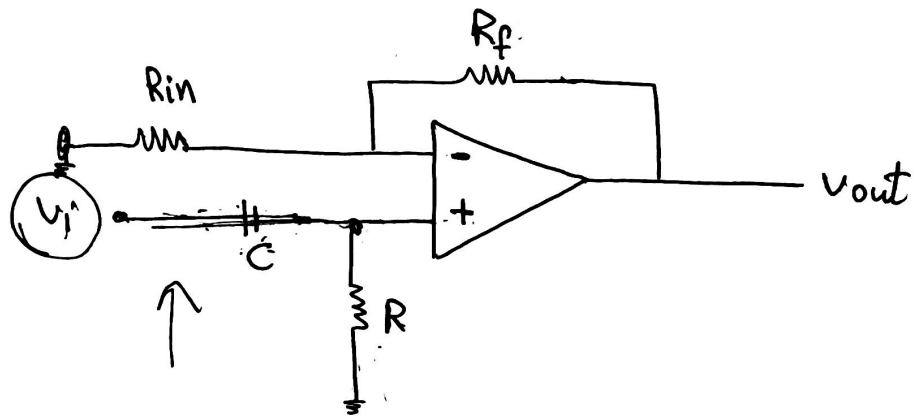

$$\text{Gain} = 1 + \frac{R_f}{R_{in}}$$

$$V_o = V_i \left( 1 + \frac{R_f}{R_{in}} \right)$$

$$f_c = \frac{1}{2\pi RC}$$

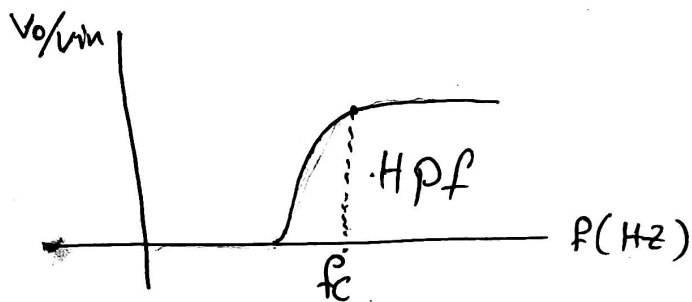

Exo-


- 1) Calculate the cutoff frequency of a LPF for  $R_1 = 1.2 \text{ k}\Omega$  &  $C_1 = 0.02 \mu\text{F}$

Solution:-



$$f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi(1.2 \times 10^3)(0.02 \times 10^{-6})} = 6.63 \text{ kHz}$$

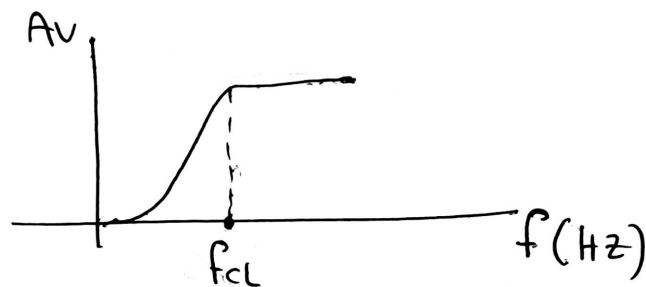- 2) Calculate the  $f_c$  of a HPF for  $R_1 = 20 \text{ k}\Omega$  and  $C_1 = 0.02 \mu\text{F}$

$$f_{cl} = \frac{1}{2(3.14)(20 \times 10^3)(0.02 \times 10^{-6})} =$$



# \* Bandpass filter :-

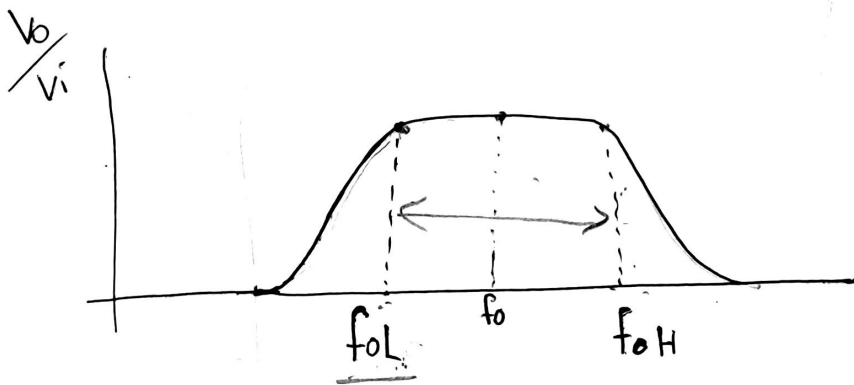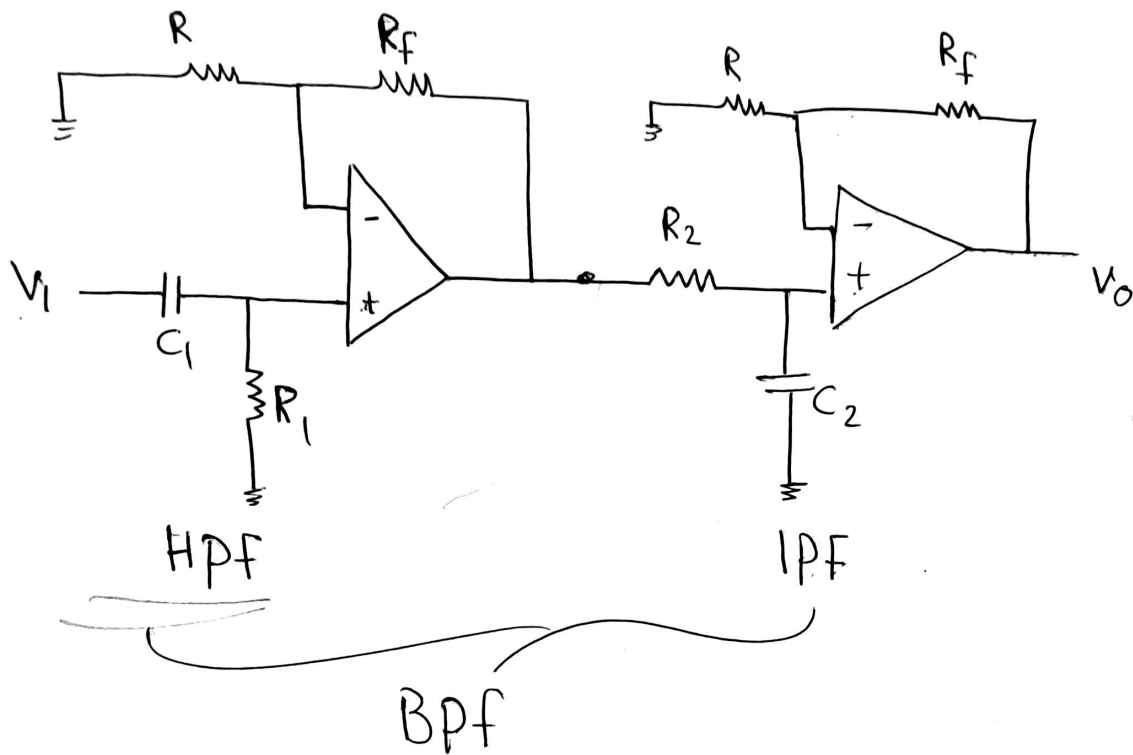

تعداد ترددان عالی  $f_{0L} = \frac{1}{2\pi R_1 C_1}$

$$f_0 = \sqrt{f_{0L} * f_{0H}}$$

تعداد ترددان سفلی  $f_{0H} = \frac{1}{2\pi R_2 C_2}$


$$BW = f_{0H} - f_{0L}$$

if  $f_{0L} < f_{0H}$   
 $f_{0H} < f_{0L}$

Bandpass filter  
 Bandstop filter

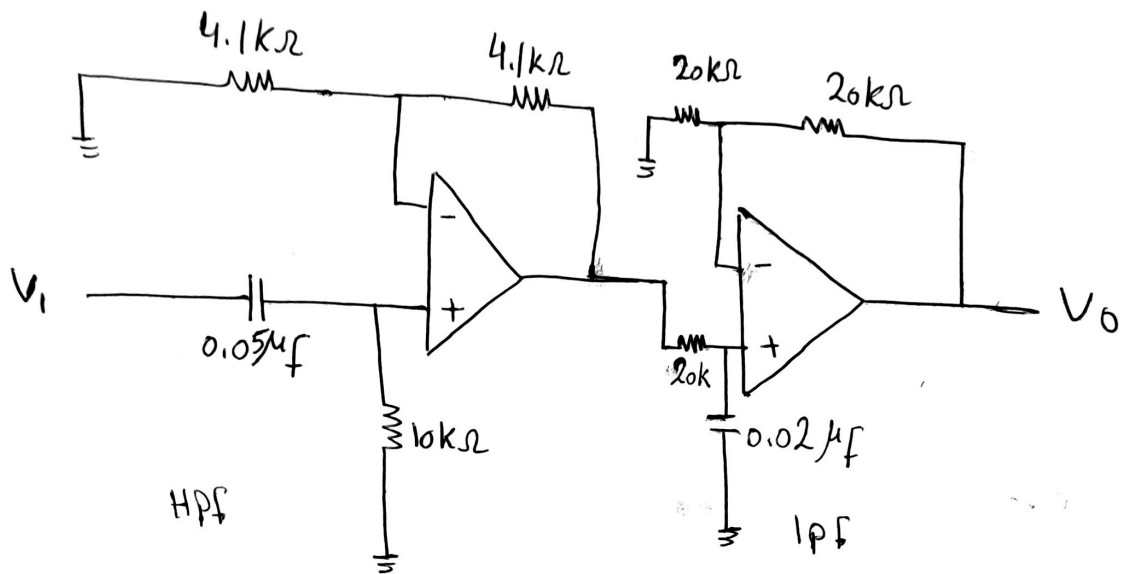3)

Calculate the lower and upper cutoff frequencies of the bandpass filter circuit




$$f_{oL} = \frac{1}{2\pi R_1 C_1}$$



$$= \frac{1}{2(3.14)(10 \times 10^3)(0.05 \times 10^{-6})} = 3.18 \text{ k Hz}$$

$$f_{oH} = \frac{1}{2\pi R_2 C_2}$$
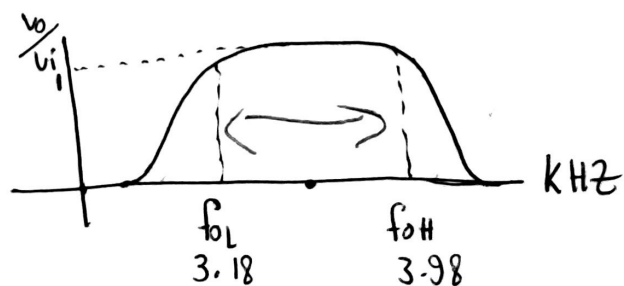
$$= \frac{1}{2(3.14)(20 \times 10^3)(0.02 \times 10^{-6})} = 3.98 \text{ k Hz}$$





Band stop filter = Band reject filter

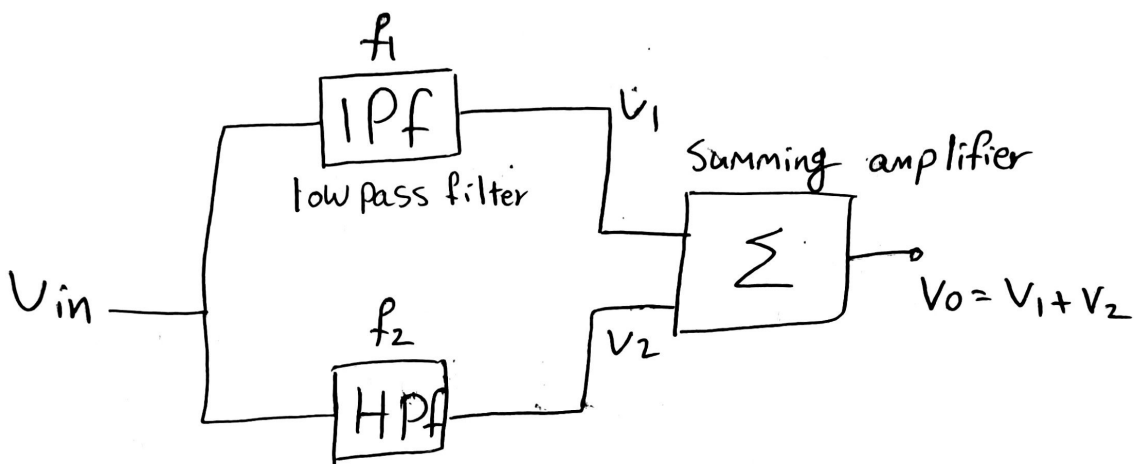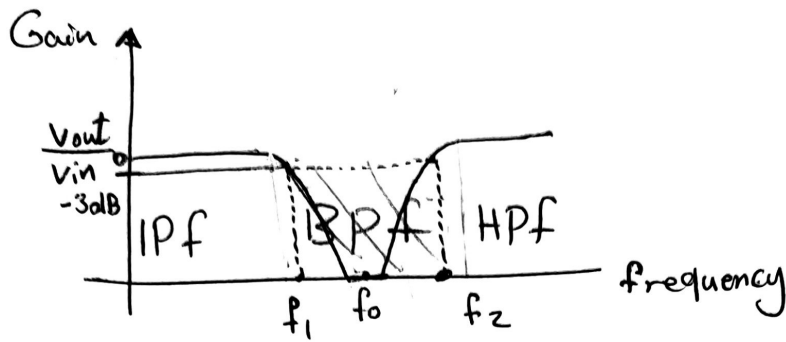

التردد المركزي  $f_0 = \sqrt{f_1 f_2}$



عرض النطاق  $BW = f_2 - f_1$

\* Second order IPF :-

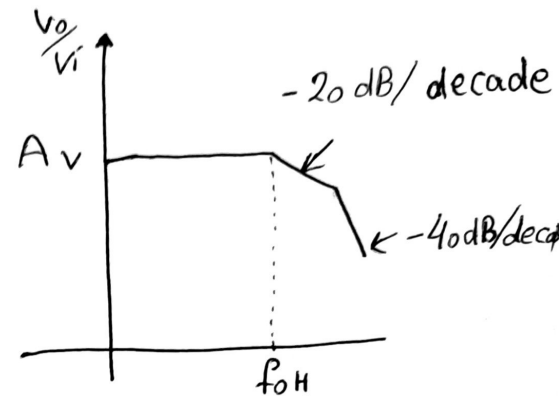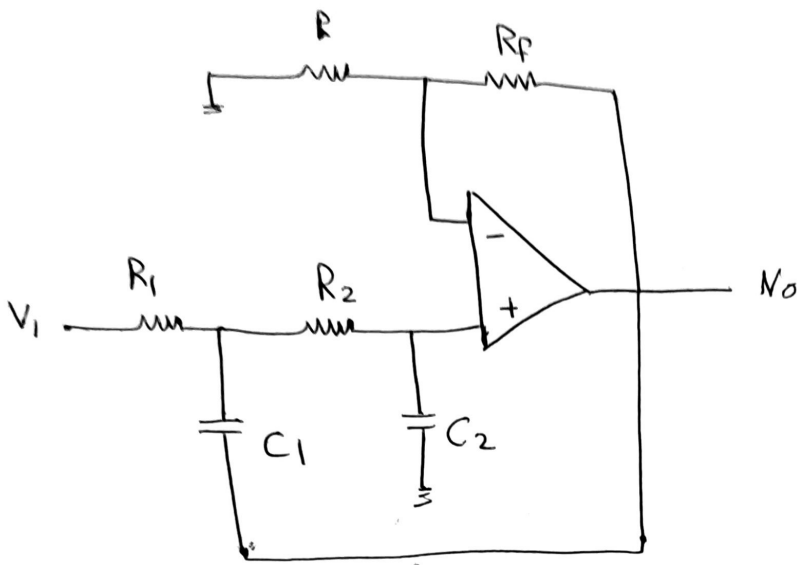


\* The circuit voltage gain and cutoff frequency are the same for the second order circuit as for the first order filter circuit except that the filter response drops at a fast rate a second order filter circuit.

\* second order HPF :-

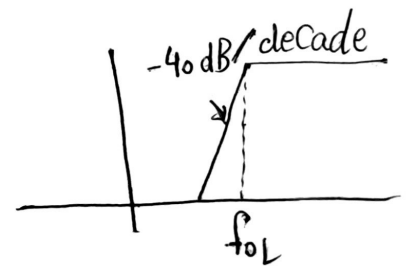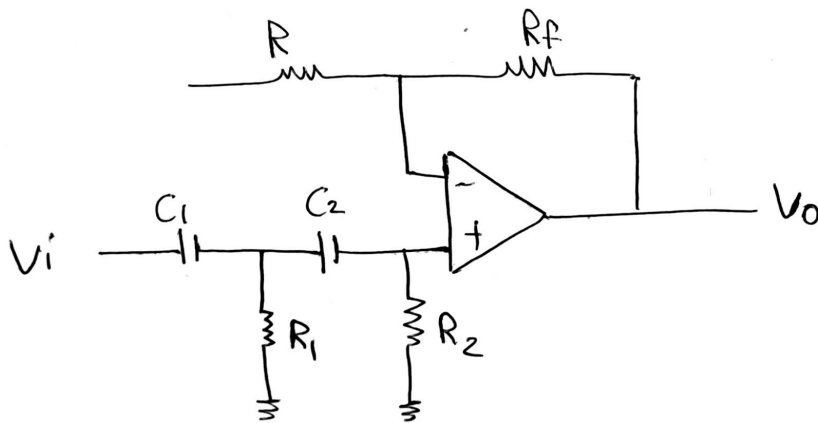

Ex :-

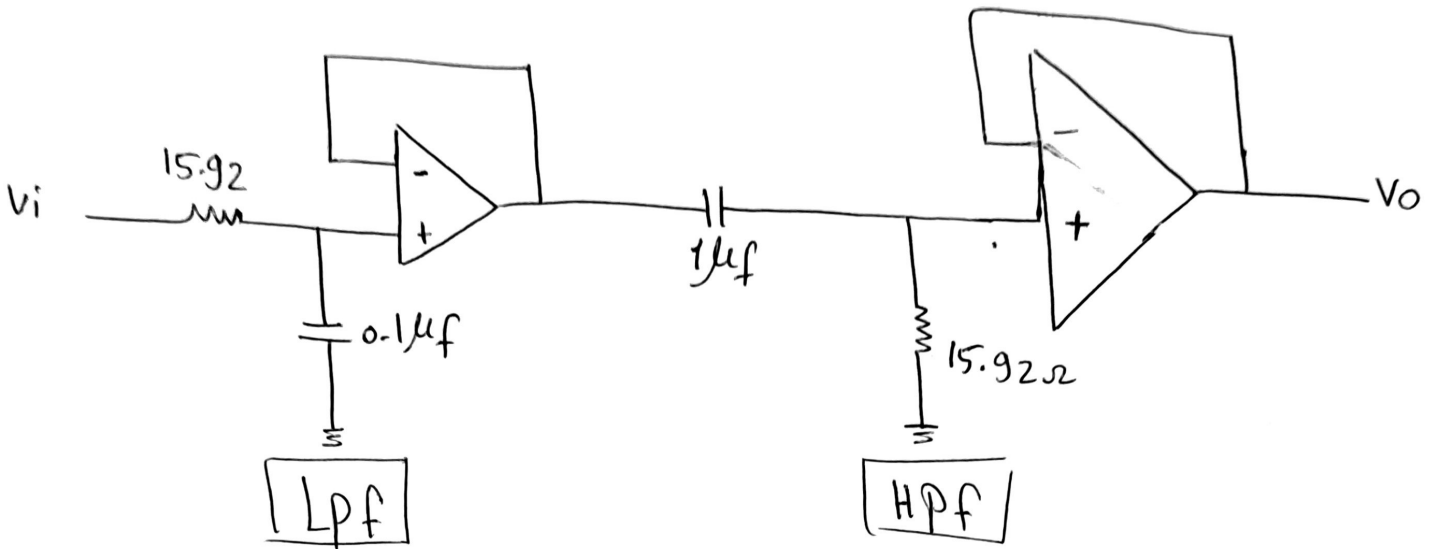

for the circuit shown :-


- What the function of this circuit
- Draw the frequency response
- find the Gain at 100 Hz

Solution :-


تقریر تردد ان عالی  $f_{OL} = \frac{1}{2(3.14)(1 \times 10^{-6})(15.9)} = 10 \text{ kHz}$

تقریر تردد ان منفرجه  $f_{OH} = \frac{1}{2(3.14)(0.1 \times 10^{-6})(15.92)} = 100 \text{ kHz}$

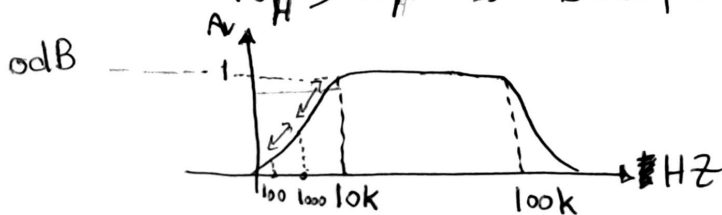$\therefore f_{OH} > f_{OL} = \text{Bandpass filter}$



Gain = -40 dB/decade

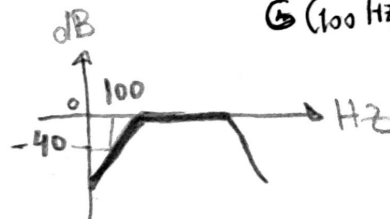

$$\begin{aligned} \text{dB} &= 20 \log \left( \frac{V_o}{V_i} \right) \\ &= 20 \log(1) \\ &= 0 \end{aligned}$$

$$G(100 \text{ Hz}) = 0 - 40 \text{ dB} = -40 \text{ dB}$$